

May 30, 2006

COMPUTER ENGINEERING DEPARTMENT

COE 202

FUNDAMENTALS OF COMPUTER ENGINEERING

Final Exam

Second Semester (052)

Time: 7:30-10:30 AM


Student Name : _____

Student ID. : _____


| Question | Max Points | Score |
|--------------|------------|-------|
| Q1 | 20 | |
| Q2 | 20 | |
| Q3 | 15 | |
| Q4 | 10 | |
| Q5 | 10 | |
| Q6 | 10 | |
| Q7 | 15 | |
| Total | 100 | |

Dr. Aiman El-Maleh

 (Q1) Consider the circuit shown below that has two inputs A, B, and two outputs X, Y:



 (i) Draw the timing diagram for the outputs X and Y given the waveforms for the inputs A and B shown below. Assume that Y is initially having the value 0.




(ii) Does this circuit implement a latch or a flip-flop, and what type? Justify your answer. Indicate what A, B, X, and Y represent.

(iii) Show the design of a **positive-edge-triggered T flip-flop** using SR latches.

(iv) Show the design of a **positive-edge-triggered JK flip-flop** using a positive-edge-triggered T flip-flop.

[20 Points]

 (Q2) It is required to design a sequential circuit that receives a serial input X , and produces a serial output Z , equivalent to $3 \cdot X$, i.e., $Z = 3 \cdot X$. The state diagram for this circuit is shown below:



Implement the sequential circuit using JK-FFs and the smallest number of gates possible assuming the state assignment: $S0=00$, $S1=01$, and $S2=10$. Show the state table and minimize your equations using K-map method.

[15 Points]

(Q3) A sequential circuit has two D flip-flops A and B, two inputs X and Y, and one output Z. The flip-flop input equations and output function are as follows:

$$D_A = B X + A Y'$$

$$D_B = A' X + B' Y$$

$$Z = X A B$$

- (i)** Show the implementation of this circuit using a ROM and D-FFs. Determine the size of the ROM that will be used and show the ROM table.
- (ii)** Obtain the state diagram for this circuit.

[10 Points]

(Q4) Implement the following two functions with a PLA:

$$F_1(A, B, C, D) = \sum m(1, 2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_2(A, B, C, D) = \sum m(0, 1, 4, 5, 9, 10, 13, 14)$$

Minimize the number of product terms used in the PLA. Show the internal logic of the PLA that will be used to implement these two functions.

[10 Points]

(Q5) A single-input, single-output sequential circuit is to be designed that recognizes the input sequence 01101 applied to its input any time it occurs in the input stream starting from a reset state. If the sequence is detected the output will be 1, otherwise it will be 0. Show the state diagram for this circuit assuming detection of **overlapping** sequences assuming a **Mealy model**. As an example, the input stream 01101101101 will produce the output stream 00001001001.

[10 Points]

(Q6) It is required to design a sequential circuit that has one serial input stream X and produces a serial output stream computing the **2's complement** of X . Obtain the state diagram for this circuit assuming a **Moore model**.

[15 Points]

(Q7) It is required to design a **synchronous 3-bit up-down counter** using positive-edge-triggered D-FFs. The counter has two inputs E and M. If $E=0$, the counter remains in the same state, regardless of the value of M. When $E=1$ and $M=1$, the counter counts up, and when $E=1$ and $M=0$, the counter counts down. Show the logic required to make the counter have **Synchronous Reset, RESET**. When $RESET=1$, the counter is reset to 0.