

Name:

Id#

COE 200, Term 993
Fundamentals of Computer Engineering
Quiz# 3

Date: Tuesday, July 11

Q.1. Implement the following Boolean function $F(A, B, C, D) = \sum m(0, 3, 13, 14)$ using only:

- (i) Four 2x4 decoders and three 2-input OR gates.
- (ii) Four 2x1 multiplexers and two inverters.

Q.2. It is required to design a Combinational circuit that compares two n-bit numbers, $A=A_{n-1}-A_0$ and $B=B_{n-1}-B_0$, to see if A is **greater** than B or not. Design a circuit that has three inputs and one output, that can be used for each of the n bits, such that the circuit is connected in cascade by carry-like signals. One of the inputs to each circuit is a carry input, and the single output is a carry output. If the final output from the last circuit is 1, then this indicates that A is greater than B, otherwise A is less than or equal to B. Using this circuit, show the design of a 4-bit greater than comparator.