

Name:

Id#

**COE 200, Term 023
Fundamentals of Computer Engineering**

Quiz# 5

Date: Saturday, August 2, 2003

Q.1. Implement the following Boolean function $F(A, B, C, D) = A' C' + B C' + A' D + B D$ using only:

- (i) Four 2x4 decoders and four 3-input OR gates.
- (ii) Three 2x1 multiplexers.