

Name:

Id#

COE 202, Term 052
Fundamentals of Computer Engineering

Quiz# 5 (Take Home)

Due date: Monday, April 17, 2006

Q.1. Assume the delay of a gate is equal to the number of its inputs, i.e. the delay of a 2-input gate is 2, and the delay of a 3-input gate is 3. Using Logic works do the following:

- a. Model a full-adder.
- b. Use the full adder model and construction from it an 8-bit Ripple Carry Adder.
- c. Determine the worst case delay in your 8-bit Ripple Carry Adder by simulation.
- d. Model a 4-bit Carry Look Ahead adder.
- e. Simulate the following values to verify that your adder works properly: $3+4$, $-1-7$, $3+1$, $2+5$, $3+3$.
- f. Determine the longest delay in the 4-bit Carry Look Ahead adder by simulation.
- g. Construct an 8-bit adder by connection two 4-bit Carry Look Ahead adders together.
- h. Determine by simulation the longest delay in the 8-bit adder in (g).

Q.2. It is required to design a BCD adder to perform addition in BCD representation.

- a. Model a single-digit BCD adder.
- b. Using the single digit BCD adder, build a 3-digit BCD adder.
- c. Verify the correct functionality of the 3-digit BCD adder by simulating the following operations: $999 + 1$, $999+222$, $100+999$, $279+465$

Q.3. [1% Bonus]

- a. Model a 4-bit multiplier.
- b. Verify the correct functionality of the 4-digit multiplier by simulating the following operations: $15 * 1$, $15*0$, $5*5$, $2*8$, $8*7$, $15*15$.