

Name: KEY

Id#


COE 202, Term 052  
Fundamentals of Computer Engineering

Quiz# 6

Date: Saturday, April 29, 2006

Q.1. Implement the following Boolean function  $F(A,B,C) = A B C + A B' C' + A' B C' + A' B' C$  with the minimum possible gates using only:

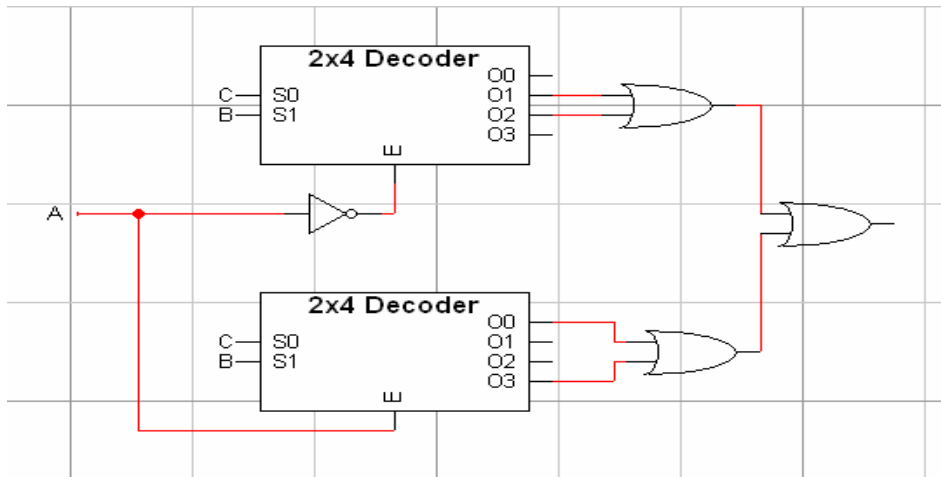(i) 2x4 decoders (with or without enable), 2-input OR gates and inverters.



(ii) 2x1 multiplexers and inverters.

$$F(A,B,C) = A [ B C + B' C' ] + A' [ B C' + B' C ]$$

Note that  $B C + B' C' = [ B C' + B' C ]'$

