

Introduction to Verilog

COE 203

Digital Logic Laboratory

Dr. Aiman El-Maleh

College of Computer Sciences and Engineering
King Fahd University of Petroleum and Minerals

Outline

- ❖ Introduction
- ❖ Why use HDL?
- ❖ Definition of Module
- ❖ Gate Level Modeling
- ❖ Verilog Primitives
- ❖ A Full Adder
- ❖ 4-bit Adder
- ❖ Continuous Assignments
- ❖ Behavioral Description of an Adder
- ❖ Verilog Operators

Introduction

- ❖ Verilog is one of the hardware description languages (HDL) available in the industry for hardware designing.
- ❖ It allows designers to design at Behavior Level, Register Transfer Level (RTL), Gate level and at switch level.
- ❖ Parallel not serial (Not like C language).
- ❖ Verilog can describe everything from single gate to full computer system.

Why use HDL ?


- ❖ Digital systems are highly complex; millions of transistors.
- ❖ For large digital systems, gate-level design is very difficult to achieve in a short time.
- ❖ Verilog allows hardware designers to express their designs with behavioral constructs, deferring the details of implementation to a later stage in the final design.
- ❖ Computer-aided design tools aid in the design process.




- © Intel P4 Processor
- Introduced in 2000
- 40 Million Transistors
- 1.5GHz Clock

Definition of Module

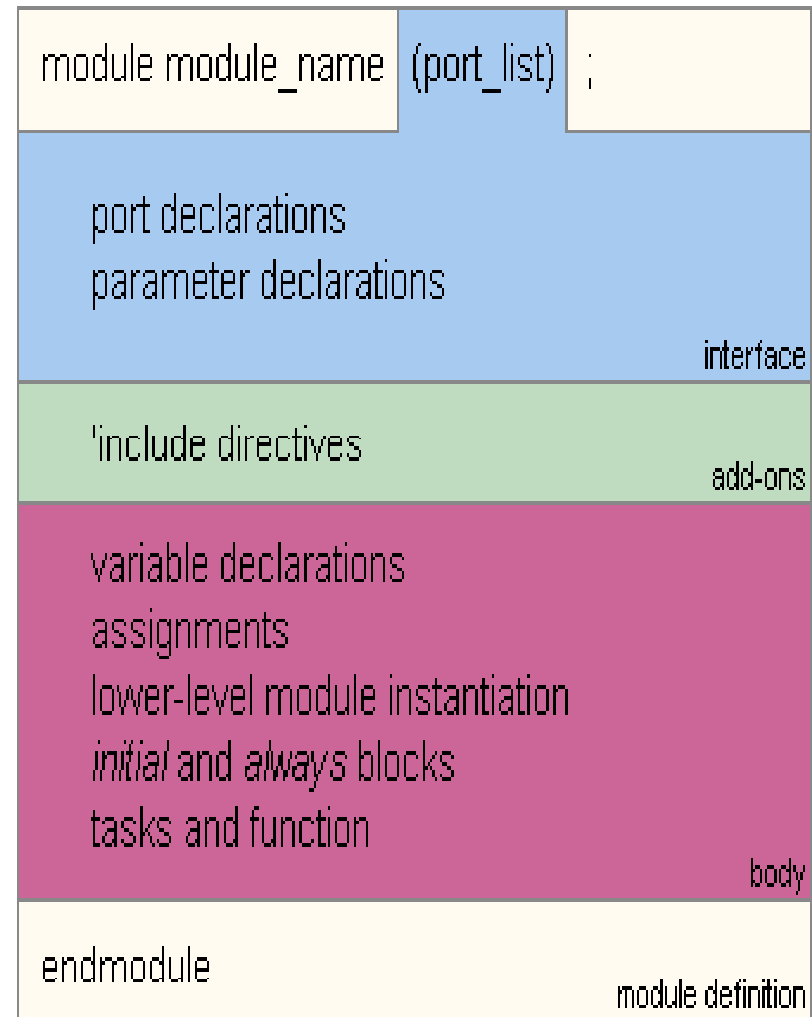- ❖ The **<module name>** is an identifier that uniquely names the module.
- ❖ The **<port list>** is a list of input, inout and output ports which are used to connect to other modules.
- ❖ Interface: port and parameter declaration
- ❖ Body: Internal part of module
- ❖ Add-ons (optional)




The Module Interface ...

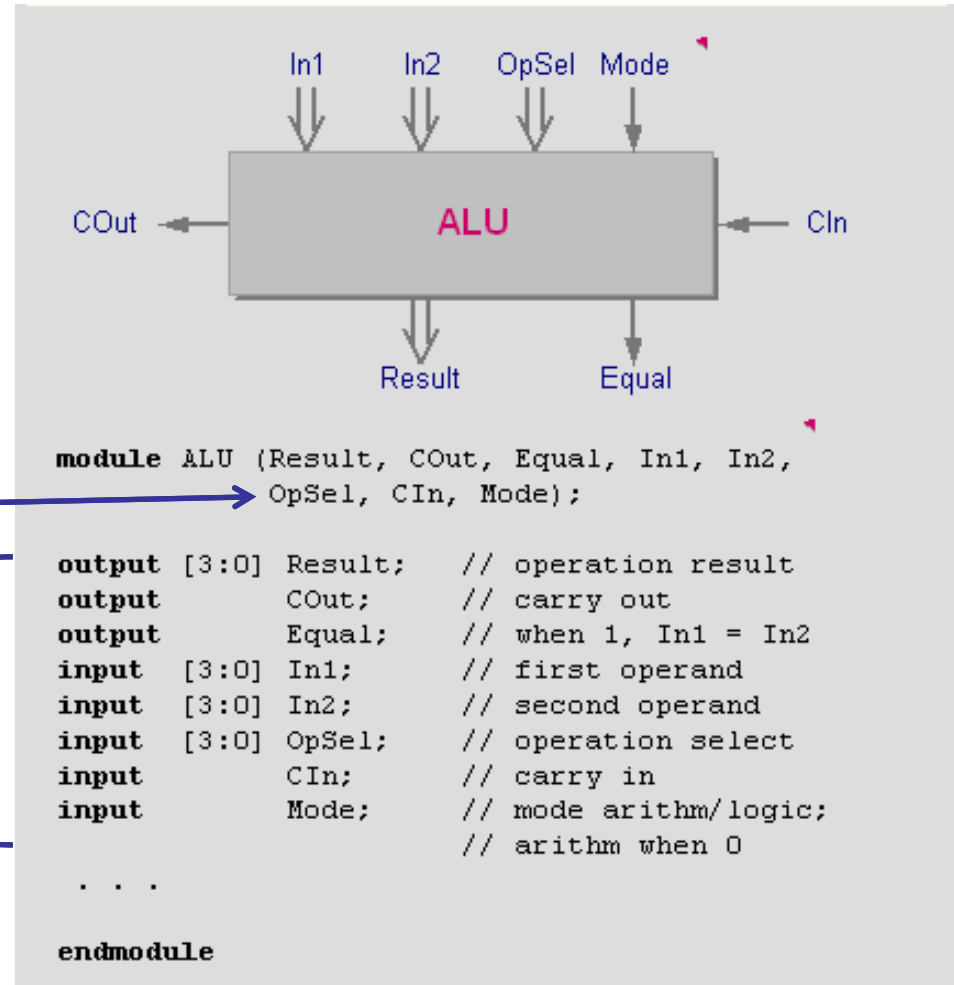

Port List

Port Declaration


... The Module Interface

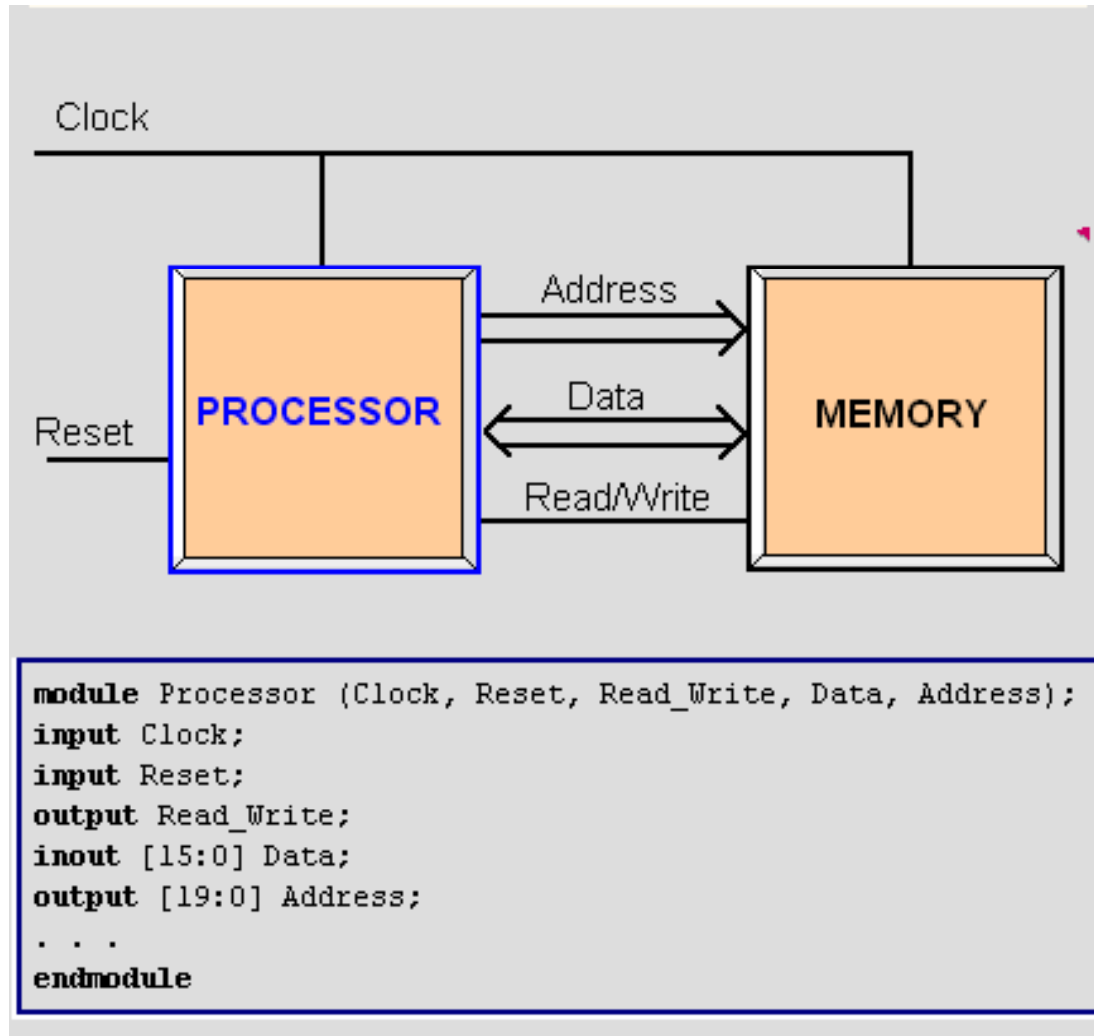

Gate Level Modeling

❖ Net-list description

❖ built-in primitives gates

 

```
module my_gate(OUT1, IN1, IN2);
```

```
    output OUT1;
```

```
    input IN1, IN2;
```

```
    wire X;
```

```
    and (X, IN1, IN2);
```

```
    not (OUT1, X);
```

```
endmodule
```

Internal Signal

Any internal net must be defined as wire

Verilog Primitives

❖ Basic logic gates only

❖ and

❖ or

❖ not

❖ buf

❖ xor





❖ nand

❖ nor


❖ xnor

❖ bufif1, bufif0


❖ notif1, notif0

    


Primitive Pins Are Expandable

 

`nand (y, in1, in2) ;`

 


`nand (y, in1, in2, in3) ;`

 

`nand (y, in1, in2, in3, in4) ;`

A Half Adder
 
```
module hadd (S, C, X, Y);  
  input X, Y;  
  output S, C;  
  
  xor (S, X, Y);  
  and (C, X, Y);  
endmodule
```



A Full Adder

```
module fadd (co, s, a, b, c);
```

```
  input a, b ,c ;
```

```
  output co, s ;
```

```
  wire n1, n2, n3;
```

```
    xor (n1, a, b) ;
```


```
    xor (s, n1, c) ;
```

```
    nand (n2, a, b) ;
```

```
    nand (n3,n1, c) ;
```


```
    nand (co, n3,n2) ;
```

```
endmodule
```

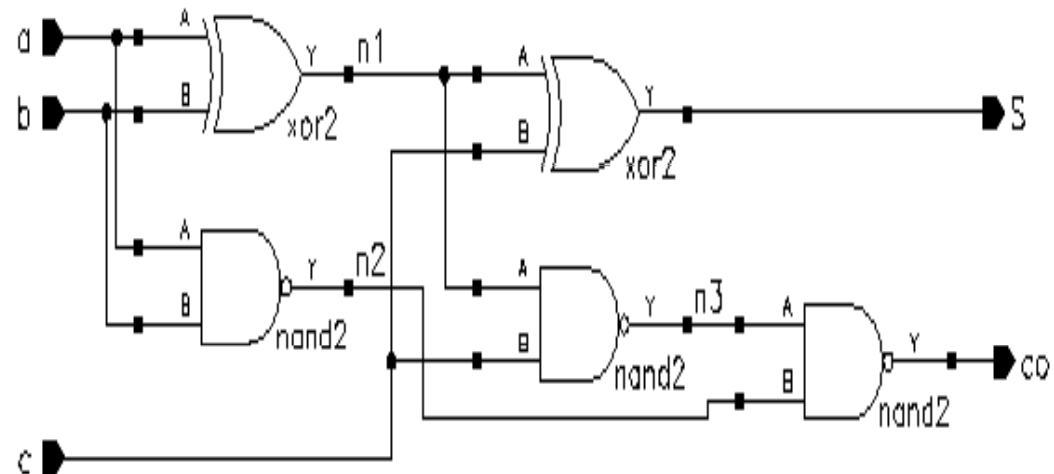

Instantiation of Modules
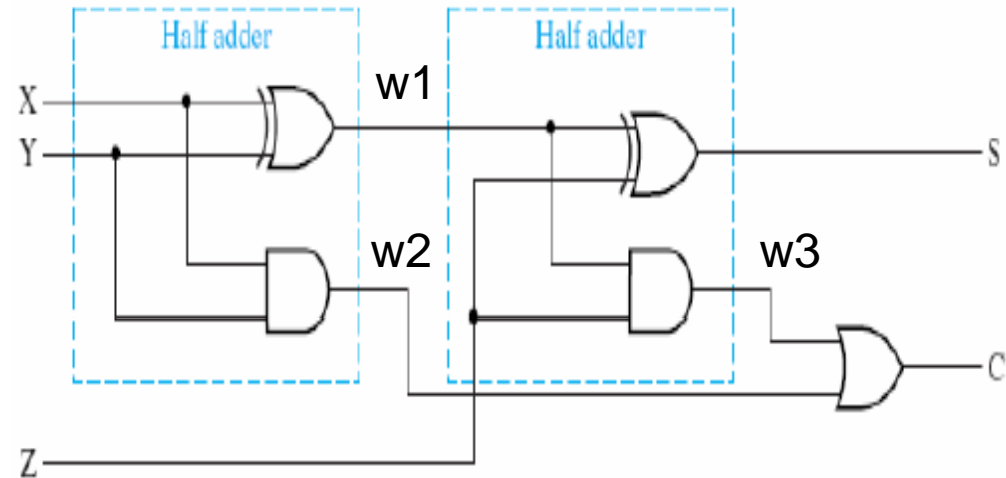
```
module fadd (S, C, X, Y, Z);  
  input X, Y, Z;  
  output S, C;  
  wire w1, w2, w3;  
  
  hadd M1 (w1, w2, X, Y);  
  hadd M2 (S, w3, w1, Z);  
  or (C, w2, w3);  
  
endmodule
```



- ❖ Here we instantiate **hadd** twice. i.e., placing two **hadd** circuits and connecting them.
- ❖ This full adder is built from two half adders and an OR gate.

4-bit Adder

```
module add4 (s,cout,ci,a,b);
```

```
  input [3:0] a,b ;    // port declarations
```

```
  input ci ;
```

```
  output [3:0] s ;    // vector
```

```
  output cout ;
```

```
  wire [2:0] co ;
```


```
    fadd a0 (co[0], s[0], a[0], b[0], ci) ;
```

```
    fadd a1 (co[1], s[1], a[1], b[1], co[0]) ;
```

```
    fadd a2 (co[2], s[2], a[2], b[2], co[1]) ;
```

```
    fadd a3 (cout, s[3], a[3], b[3], co[2]) ;
```

```
endmodule
```

 

Continuous Assignments

- ❖ Describe combinational logic
- ❖ Operands + operators
- ❖ Drive values to a net
 - ✧ `assign out = a&b ;` // and gate
 - ✧ `assign eq = (a==b) ;` // comparator
 - ✧ `wire #10 inv = ~in ;` // inverter with delay
 - ✧ `wire [7:0] c = a+b ;` // 8-bit adder
- ❖ Avoid logic loops
 - ✧ `assign a = b + a ;`
 - ✧ asynchronous design

Simple XOR Gate

```
module my_xor( C, A, B );  
    output C;  
    input A, B;  
  
    assign C = (A ^ B);  
endmodule
```

Operation	Operator
~	Bitwise NOT
&	Bitwise AND
	Bitwise OR
^	Bitwise XOR

Full Adder


```
module fadd (S, Cout, A, B, Cin);
```

```
output S, Cout;
```

```
input A, B, Cin;
```

```
assign S = A ^ (B ^ Cin);
```

```
assign Cout = (A & B)  
              | (A & Cin)  
              | (B & Cin) ;
```

 

```
endmodule
```

Behavioral Description of an Adder

```
module adder4 ( S, Cout, A, B, Cin);
```

```
input [3:0] A, B;
```

```
input Cin;
```

```
output [3:0] S;
```

```
output Cout;
```

```
assign { Cout, S } = A + B + Cin;
```

```
// note: Verilog treats wires as 'unsigned' numbers
```

```
endmodule
```

4-bit operands,
5-bit result

{ Cout, S } is a 5 bit bus:

Cout S[3] S[2] S[1] S[0]

Behavioral Description of an Adder

```
module adder (cout, sum, a, b, cin);  
    parameter width = 2;  
    input cin;  
    input [width:0]    a, b;  
    output [width:0]   sum;  
    output cout;  
    assign {cout, sum} = a + b + cin;  
endmodule
```

Verilog Operators

{ }	concatenation
+ - * /	arithmetic
%	modulus
> >= < <=	relational
!	logical NOT
&&	logical AND
	logical OR
==	logical equality
!=	logical inequality
? :	conditional

~	bit-wise NOT
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
^~ ~^	bit-wise XNOR
&	reduction AND
	reduction OR
~&	reduction NAND
~	reduction NOR
^	reduction XOR
~^ ^~	reduction XNOR
<<	shift left
>>	shift right