 


COE 360, Principles of VLSI Design, Term 71
HW# 2

Q.1. Consider the transistor-level implementation of the 2-input gate shown below. Assume that the threshold voltages of the nMOS and pMOS transistors are $V_{tn}=1v$ and $V_{tp}=-1v$.




- (a) Determine the function implemented by the gate.
- (b) Is there any problem with the given implementation? If there is a problem, then suggest a modification to the implementation to overcome the problem.
- (c) Reimplement the gate function using only transmission gates and inverters.

Q.2. Implement the following in CMOS using the smallest possible number of transistors assuming the availability of inverted inputs:


- (a) $Y = A' C' + A' D + A C + A D$
- (b) $Y = A' B' C + A' B D + A B' E + A B F$
- (c) $Y = A B' C' + A' B C' + A B C + A' B' C$

Q.3. Express the functions implemented by the following gates:

(a)

 


(ii)

 

Q.4. Design a falling-edge D-flip flop using CMOS gates.

 Q.5. Consider an nMOS transistor with a threshold voltage $V_m=1v$, $L=1u$, and $W=2u$, as shown below.



(i) Using spice, draw the voltage-current graph by changing V_{gs} from 1v to 5v, and V_{ds} from 0v to 5v.

(ii) Redraw the voltage-current graph by changing W to 20u. What are your observations?