
 
 
 
 
 


HW#3

 Q.1. Assuming nMOS enhancement transistor threshold voltage V_{tn} of 1.0 V, depletion transistor threshold voltage V_{td} of -2.0 V, and pMOS enhancement transistor threshold voltage V_{tp} of -1.0 V, write down the voltages of the indicated nodes below. Assume that the body effect is negligible.



Q2 (i) Depletion-type nmos transistor


$$\mu C_{ox} = 200 \mu\text{A}/\text{V}^2, \quad V_{td} = -2 \text{ V}, \quad V = 0.6 \text{ V}, \quad 2\phi_b = 0.6 \text{ V}$$

$V_{sb} \neq 0 \Rightarrow$ there is body bias

$$V_t = V_{t0} + \gamma \left[\sqrt{2\phi_b + |V_{sb}|} - \sqrt{2\phi_b} \right]$$

$$= -2 + \frac{1}{2} \left[\sqrt{0.6 + 3.4} - \sqrt{0.6} \right]$$

$$= -1.387 \text{ V}$$

 

$$V_{gs} = 0 > -1.387 \text{ V}, \quad V_{gd} = -1.6 < -1.387 \text{ V}$$

\Rightarrow transistor will be in saturation when

$$V_{out} = 3.4 \text{ V}$$

$$I_D = \frac{\beta}{2} [V_{gs} - V_t]^2$$

$$\Rightarrow \beta = \frac{2 I_D}{[V_{gs} - V_t]^2} = \frac{2 \times 0.5 \times 10^{-3} \text{ mA}}{[0 + 1.387]^2}$$

$$= 519.59 \frac{\text{mA}}{\text{V}^2}$$

$$\beta = \mu C_{ox} \frac{W}{L} \Rightarrow \frac{W}{L} = \frac{\beta}{\mu C_{ox}} = \frac{519.59}{200}$$

$$= 2.598$$

$$\text{Since } L = 1 \mu\text{m} \Rightarrow W = 2.598 \mu\text{m}$$

However, since the minimum grid size is

$$0.25 \mu\text{m} \Rightarrow W = \underline{\underline{2.75 \mu\text{m}}}$$

(ii) PMOS transistor

$V_{sb} = 0 \Rightarrow$ No bias effect

$$V_{tp} = -1 \text{ V}$$

$$\mu C_{ox} = 40 \text{ } \mu\text{A}/\text{V}^2, \gamma = 0.5 \text{ V}^{1/2}, 2\phi_b = 0.6 \text{ V}$$

$$V_{gs} = -5 \text{ V} < -1 \text{ V}, V_{ds} = -1.6 \text{ V}$$

$V_{gd} = -3.4 \text{ V} < -1 \Rightarrow$ transistor will be linear

when $V_{out} = 3.4$

$$I_D = \frac{\beta}{2} [2(V_{gs} - V_t)V_{ds} - V_{ds}^2]$$

$$\Rightarrow \beta = \frac{2 I_D}{[2(V_{gs} - V_t)V_{ds} - V_{ds}^2]}$$

$$= \frac{2 \times 0.5 \times 10^{-3} \text{ } \mu\text{A}}{[2(-5 + 1)(-1.6) - (-1.6)^2]}$$


$$= 97.66 \frac{\mu\text{A}}{\text{V}^2}$$

$$\frac{W}{L} = \frac{\beta}{\mu C_{ox}} = \frac{97.66}{40} = 2.44$$

Since $L = 1 \mu \Rightarrow W = 2.44 \mu$

However, since the minimum grid size is 0.25

$\Rightarrow W = 2.5 \mu$

 

Q3

1. $V_{gs} = V_{ds} = 9V \Rightarrow V_{gd} = 0 < V_{th}$

\Rightarrow transistor is in saturation

$$I_D = \frac{\beta}{2} [V_{gs} - V_t]^2$$

$$\Rightarrow 2 \text{ mA} = \frac{\beta}{2} [9 - V_t]^2 \Rightarrow \beta = \frac{4 \text{ mA}}{[9 - V_t]^2}$$

2. $V_{gs} = V_{ds} = 5V \Rightarrow V_{gd} = 0 < V_{th}$

\Rightarrow transistor is in saturation

$$\Rightarrow 0.5 \text{ mA} = \frac{\beta}{2} [5 - V_t]^2 \Rightarrow \beta = \frac{1 \text{ mA}}{[5 - V_t]^2}$$

Equating the equations in (1) & (2)

$$\Rightarrow \frac{4 \text{ mA}}{[9 - V_t]^2} = \frac{1 \text{ mA}}{[5 - V_t]^2}$$

$$\Rightarrow \frac{2}{9 - V_t} = \frac{1}{5 - V_t}$$

$$\Rightarrow 9 - V_t = 10 - 2V_t \Rightarrow \boxed{V_t = 1V}$$

$$\text{Thus, } \beta = \frac{1 \text{ mA}}{[5 - V_t]^2} = \frac{1 \text{ mA}}{16} = \underline{\underline{62.5 \frac{\mu\text{A}}{\text{V}^2}}}$$