

HW#5

Q1 Average DC power dissipation = $\frac{V_{DD}}{2} \frac{(V_{DD} - V_{OL})}{R_L}$

$$\Rightarrow 100 \mu W = \frac{5}{2} \frac{(5 - V_{OL})}{120 \text{ k}\Omega} \Rightarrow V_{OL} = 0.2 \text{ V}$$

When $V_{out} = V_{OL}$, $V_{in} = V_{OH} = V_{DD}$

$V_{gd} = V_{DD} - V_{OL} > V_t \Rightarrow$ transistor is linear

By KCL: $\frac{V_{DD} - V_{OL}}{R_L} = \frac{\beta}{2} [2(V_{DD} - V_t)V_{OL} - V_{OL}^2]$


$$\begin{aligned} \Rightarrow \beta R_L &= \frac{2(V_{DD} - V_{OL})}{[2(V_{DD} - V_t)V_{OL} - V_{OL}^2]} \\ &= \frac{2(5 - 0.2)}{[2(5 - 0.8)0.2 - (0.2)^2]} \\ &= \frac{9.6}{[1.68 - 0.04]} = 5.854 \end{aligned}$$

For a resistive-load inverter,

$$V_{IL} = V_t + \frac{1}{R_L \beta} = 0.8 + \frac{1}{5.854} = \underline{0.971 \text{ V}}$$

$$\begin{aligned} \text{and } V_{out}(V_{IL}) &= V_{DD} - \frac{1}{2R_L \beta} = 5 - \frac{1}{2(5.854)} \\ &= \underline{4.91 \text{ V}} \end{aligned}$$

Q2 (i)

 

For a depletion-load inverter,


$$V_{OL} = V_{OH} - V_{T_0} - \sqrt{(V_{OH} - V_{T_0})^2 - \frac{\beta_{load}}{\beta_{driver}} |V_{T_{load}}(V_{OL})|^2}$$

The worst or highest V_{OL} is obtained when $C = H$ and $E = H$, while all other inputs are low. This is because this combination produces the highest pull-down resistance or the smallest equivalent β_{driver} . This in turn produces the highest V_{OL} .

Let us first find the inverter-equivalent circuit for this combination.

$$\left(\frac{W}{L}\right)_{equiv} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_C} + \frac{1}{\left(\frac{W}{L}\right)_E}} = \frac{1}{\frac{1}{3} + \frac{1}{5}} = \frac{1}{\frac{8}{15}} = \frac{15}{8}$$
 
$$\frac{\beta_{load}}{\beta_{driver}} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_{load}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{driver}} = \frac{V_3}{15/8} = \frac{8}{45} = 0.18$$



To compute V_{OL} , we first assume

$$V_{T_{load}}(V_{OL}) = -2.5$$

$$\Rightarrow V_{OL} = 5 - 1 - \sqrt{(5-1)^2 - \frac{8}{45} (2.5)^2} = 0.14 \text{ V}$$

Next, we compute the value of $V_{T_{load}}$ as a function of V_{OL} .

$$\begin{aligned}
 V_{T,load}(V_{OL} = 0.14) &= V_{T0,load} + \gamma \left[\sqrt{2\phi_b + V_{OL}} - \sqrt{2\phi_b} \right] \\
 &= -2.5 + 0.4 \left[\sqrt{0.6 + 0.14} - \sqrt{0.6} \right] \\
 &= -2.47 \text{ V}
 \end{aligned}$$

Then, we recompute V_{OL} with the updated value of $V_{T,load}$

$$V_{OL} = 4 - \sqrt{16 - \frac{8}{45} (2.47)^2} \approx \underline{0.14 \text{ V}}$$

So, we stop here.

The best or lowest V_{OL} is achieved when all inputs are high. This combination produces the lowest pull-down resistance or the largest equivalent β driver.

First, let us find the inverter equivalent circuit for this combination.

$$\begin{aligned}
 \left(\frac{W}{L}\right)_{equiv} &= \left(\frac{W}{L}\right)_A + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_D}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_C} + \frac{1}{\left(\frac{W}{L}\right)_E}} \\
 &= 2 + \frac{1}{\frac{1}{4} + \frac{1}{8}} + \frac{1}{\frac{1}{3} + \frac{1}{5}} \\
 &= 2 + \frac{24}{16} + \frac{15}{8} = 6.275
 \end{aligned}$$

$$\frac{\beta_{load}}{\beta_{driver}} = \frac{V_3}{6.275} = 0.053$$

Since V_{OL} will be very small, we can assume that the body bias effect is negligible.

$$V_{OL} = 4 - \sqrt{16 - 0.05 (2.5)^2} = \underline{0.04 \text{ V}}$$

(ii) We need to design the circuit to achieve a worst case $V_{OL} = 0.1 \text{ V}$.

Since the output value is small, we can neglect the body-bias effect.

$$0.1 = 4 - \sqrt{16 - \frac{\beta_{load}}{\beta_{driver}} (2.5)^2}$$

$$\Rightarrow 3.9 = \sqrt{16 - \frac{\beta_{load}}{\beta_{driver}} (2.5)^2}$$


$$\Rightarrow 15.21 = 16 - \frac{\beta_{load}}{\beta_{driver}} (6.25) \Rightarrow \frac{\beta_{load}}{\beta_{driver}} = 0.126$$

Thus, $\left(\frac{W}{L}\right)_{driver} = \left(\frac{W}{L}\right)_{load} \times \frac{1}{0.126} = \underline{2.64}$

If we assume that all $\frac{W}{L}$ for all the nmos transistors are equivalent, then the worst case is when two transistors in series are on


$$\Rightarrow \left(\frac{W}{L}\right)_{equiv} = \frac{1}{2} \left(\frac{W}{L}\right) \Rightarrow \left(\frac{W}{L}\right) = 2 \left(\frac{W}{L}\right)_{equiv}$$

$$= 2 \times 2.64 = 5.28$$

 

or we can have the following design, which achieves the same V_{OL} for all single paths from output to ground.

 * Note that the second design has less area.



Q3 CMOS Inverter

(i) $V_{th} = 2.5 \text{ V}$, $V_{DD} = 5 \text{ V}$

since $V_{th} = \frac{V_{DD}}{2}$ and

$$V_{th} = |V_{tp}| \Rightarrow \frac{\beta_n}{\beta_p} = 1$$

$$\Rightarrow \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p} = 1$$

$$\Rightarrow \left(\frac{W}{L}\right)_p = \left(\frac{W}{L}\right)_n \times \frac{\mu_n C_{ox}}{\mu_p C_{ox}} = \left(\frac{W}{L}\right)_n \times \frac{100}{40} = 2.5 \left(\frac{W}{L}\right)_n$$

$$\Rightarrow \left(\frac{W}{L}\right)_n = 0.4 \left(\frac{W}{L}\right)_p$$


since $\left(\frac{W}{L}\right)_p$ is given as 2 $\Rightarrow \left(\frac{W}{L}\right)_n = 0.8$

(ii) For a symmetric inverter, $NMH = NML = V_{IL}$

$$V_{IL} = \frac{1}{8} (3 V_{DD} + 2 V_{tn})$$

$$= \frac{1}{8} (15 + 2) = 2.125 \text{ V}$$


Thus, $NMH = NML = 2.125 \text{ V}$

 

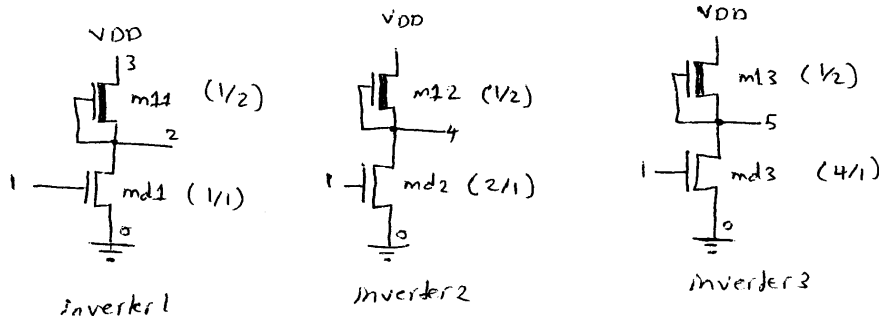Q4


* Depletion-Load Inverter Circuit

```
VDD 3 0 DC 5
md1 2 1 0 0 emode W=1u L=1u
m11 3 2 2 0 dmode W=1u L=2u
md2 4 1 0 0 emode W=2u L=1u
m12 3 4 4 0 dmode W=1u L=2u
md3 5 1 0 0 emode W=4u L=1u
m13 3 5 5 0 dmode W=1u L=2u
VS 1 0 DC
.model emode nmos (vto=1.0 gamma=0.4 phi=0.6 kp=100u)
.model dmode nmos (vto=-2.5 gamma=0.4 phi=0.6 kp=100u)
.DC VS 0 5 0.1
.print dc v(2) v(4) v(5)
.end
```



Inverter	β_{driven}	β_{load}
1	v(2)	2
2	v(4)	4
3	v(5)	8

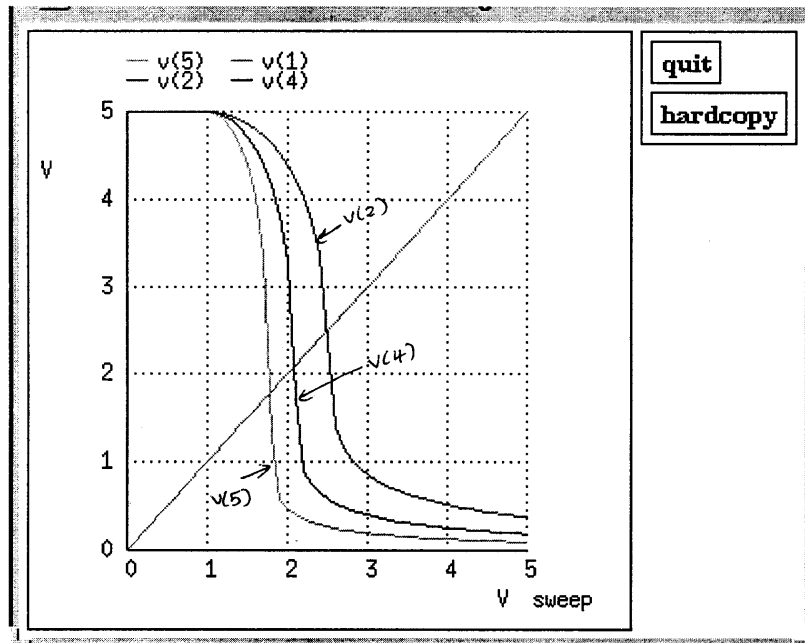
we can observe from the voltage transfer characteristic graphs that for a depletion-load inverter, it is necessary to have a large $\beta_{\text{driver}}/\beta_{\text{load}}$ ratio. The larger this ratio is the lower the value of V_{OL} . Note also that this reduces the values of V_{IL} , V_{IH} and V_{th} . NMH will increase but NML might be the same.




Q5

* CMOS Inverter Circuit


```
VDD 3 0 DC 5
md1 2 1 0 0 MN W=1u L=1u
ml1 2 1 3 3 MP W=2u L=1u
md2 4 1 0 0 MN W=2u L=1u
ml2 4 1 3 3 MP W=2u L=1u
md3 5 1 0 0 MN W=4u L=1u
ml3 5 1 3 3 MP W=2u L=1u
VS 1 0 DC
.model MN nmos (vto=1.0 gamma=0.4 phi=0.6 kp=100u)
.model MP pmos (vto=-1.0 gamma=0.4 phi=0.6 kp=40u)
.DC VS 0 5 0.1
.print dc v(2) v(4) v(5), I(vdd)
.end
```

 

inverter 1

 


inverter 2

 

inverter 3

Inverter		β_n / β_p
1	v(2)	1.25
2	v(4)	2.5
3	v(5)	5

A key parameter in the design of CMOS inverters is the inverter threshold voltage. All CMOS inverters have a $V_{OL} = 0$ and $V_{OH} = V_{DD}$. We can see here that as β_n/β_p is close to 1, V_{th} is close to $V_{DD}/2$ since $V_{th} = (V_{thp})$. The larger the ratio of $\frac{\beta_n}{\beta_p}$, the smaller the value of V_{th} . In CMOS inverters, we can be close to the behavior of an ideal inverter using a small $(w/L)_n/(w/L)_p$ ratio, nearly equal to $\sqrt{2.5}$ for a symmetric inverter, i.e. $(\frac{w}{L})_p \approx 2.5 (\frac{w}{L})_n$.

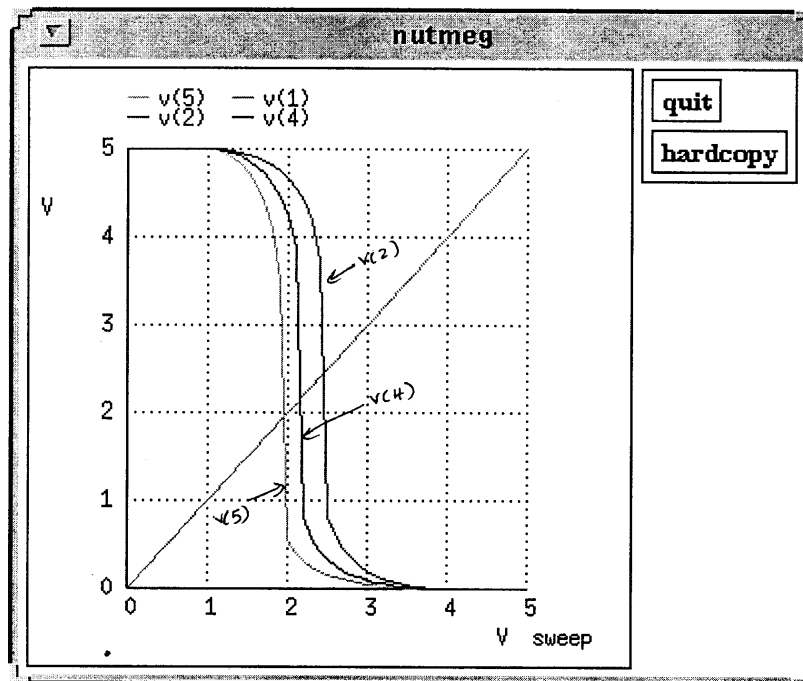

For nmos inverters, larger ratio $\beta_{driver}/\beta_{load}$ is required which implies $(\frac{w}{L})_{driver}$ has to be larger than $(\frac{w}{L})_{load}$.

Q6 (i) For the first shape:

$$\begin{aligned} R &= 1 R_s + 0.66 R_s + 0.66 R_s + 4 R_s \\ &\quad + 0.66 R_s + 0.66 R_s + 1 R_s \\ &= 8.64 R_s \end{aligned}$$

Material	Resistance
Polysilicon	$8.64 \times 20 = 172.8 \Omega$
n-diffusion	$8.64 \times 40 = 345.6 \Omega$
p-diffusion	$8.64 \times 150 = 1296 \Omega$
metal	$8.64 \times 0.05 = 0.432 \Omega$

For the second shape:

$$\begin{aligned} R &= 1 R_s + \frac{2}{3} R_s + \frac{1.5}{5} R_s + \frac{2.5}{2} R_s \\ &= 3.22 R_s \quad (\text{Note that for simplicity, corners are ignored}). \end{aligned}$$

Material	Resistance
Polysilicon	$3.22 \times 20 = 64.4 \Omega$
n-diffusion	$3.22 \times 40 = 128.8 \Omega$
p-diffusion	$3.22 \times 150 = 483 \Omega$
metal	$3.22 \times 0.05 = 0.161 \Omega$

(ii) * The channel resistance of the p-transistor equals the resistance of two resistors in series R_1 and R_2 . R_1 equals to $\frac{3}{2} R_s$. R_2 is a parallel combination of three resistors, two of which have nonuniform current flow.

$$\frac{1}{R_2} = \frac{1}{R_s} + \frac{1}{2(0.66)R_s} + \frac{1}{2(0.66)R_s}$$

$$\frac{1}{R_2} = \frac{1 + 0.76 + 0.76}{R_s} = \frac{2.52}{R_s}$$

$$\Rightarrow R_2 = 0.398 R_s$$

$$\begin{aligned} \Rightarrow R_p &= R_1 + R_2 = 1.5 R_s + 0.398 R_s \\ &= 1.898 R_s \\ &= 1.898 \times 15 \times 10^3 \\ &= \underline{\underline{28.47 \text{ k}\Omega}} \end{aligned}$$

* The channel resistance of the n-transistor consists of three resistances in parallel.

$$\frac{1}{R_n} = \frac{1}{\frac{1}{4} R_s} + \frac{1}{(0.66)R_s} + \frac{1}{\frac{1}{2} R_s}$$

$$= \frac{4 + 1.52 + 2}{R_s} = \frac{7.52}{R_s}$$

$$\begin{aligned} \Rightarrow R_n &= \frac{1}{7.52} R_s = \frac{1}{7.52} \times 6 \times 10^3 \\ &= \underline{\underline{0.798 \text{ k}\Omega}} \end{aligned}$$