


**COE 360 Principles of VLSI Design**  
**Dr. Aiman El-Maleh**

**Lecture#12**

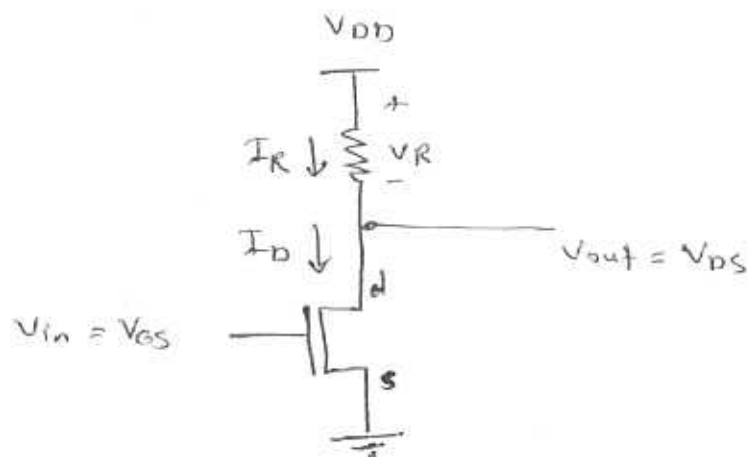**Resistive-Load Inverter**

Resistive - Load Inverter

Consider the structure of the resistive-load inverter shown below.



\* When  $V_{in} < V_t$ , the transistor is in cutoff and does not conduct any drain current. Since the voltage drop across the load resistor is equal to zero, the output voltage =  $V_{DD}$ .

\* As the input voltage is increased beyond  $V_t$  (i.e.  $V_{in} \geq V_t$ ), the driver transistor starts conducting a nonzero drain current. The transistor will be initially in saturation since  $V_{out} = V_{DS}$  will be slightly under  $V_{DD}$  and  $V_{in} = V_{GS}$  close to  $V_t$  i.e.  $V_{GS} - V_t < V_{DS}$  or  $V_{gd} = V_{GS} - V_{DS} < V_t$ .

$$\text{Thus, } I_R = \frac{\beta_n}{2} (V_{in} - V_t)^2$$

\* With increasing input voltage, the drain current of the driver also increases, and the output voltage  $V_{out}$  starts to drop. Eventually, for input voltages larger than  $V_{out} + V_t$  (i.e.  $V_{gs} > V_{ds} + V_t = V_{gs} - V_{ds} > V_t$ ) the transistor enters the linear region.


Thus, the current  $I_R = I_D$  is given as:

$$I_R = \frac{\beta_n}{2} [2(V_{in} - V_t) \cdot V_{out} - V_{out}^2]$$

The various operating regions of the driver transistor and the corresponding input-output conditions are summarized below:

Input Voltage Range	Operating Mode
$V_{in} < V_t$	Cutoff
$V_t \leq V_{in} \leq V_{out} + V_t$	Saturation
$V_{in} > V_{out} + V_t$	linear

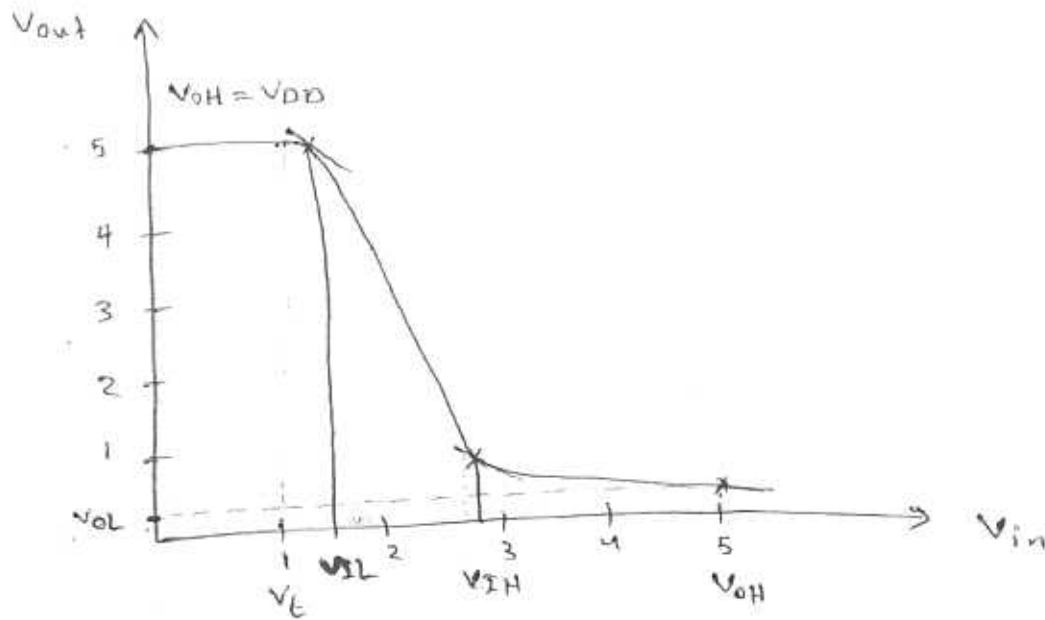The voltage transfer characteristic (VTC) of a typical resistive-load inverter circuit indicating the operating modes of the transistor and the critical voltage points is shown below:



Now, let us calculate the five critical voltage points which determine the steady state input-output behavior of the inverter.

\* Calculation of VOH

The output voltage  $V_{out}$  is given by

$$V_{out} = V_{DD} - R_L I_R$$

When the input voltage  $V_{in}$  is low i.e., smaller than  $V_t$ , the driver transistor is cutoff. Since the drain current of the driver transistor is equal to the load current,  $I_R = I_D = 0$ . Thus, the output voltage  $V_{OH} = V_{DD}$ .

### \* Calculation of $V_{OL}$

To calculate the output low voltage  $V_{OL}$ , we assume that the input voltage is equal to  $V_{OH}$ , i.e.  $V_{in} = V_{OH} = V_{DD}$ .

Since  $V_{in} - V_t > V_{out}$ , the driver transistor operates in the linear region. Thus, the load current  $I_R$  is

$$I_R = I_D = \frac{\beta_n}{2} [2(V_{DD} - V_t)V_{OL} - V_{OL}^2]$$

Note also that  $I_R = \frac{V_{DD} - V_{out}}{R_L}$

Thus,  $\frac{V_{DD} - V_{OL}}{R_L} = \frac{\beta_n}{2} [2(V_{DD} - V_t)V_{OL} - V_{OL}^2]$

This equation yields a simple quadratic in  $V_{OL}$ , which is solved to find the value of the output low voltage.

$$V_{OL}^2 - 2 \left[ V_{DD} - V_T + \frac{1}{\beta_n R_L} \right] V_{OL} + \frac{2}{\beta_n R_L} V_{DD} = 0$$

Note:  $ax^2 + bx + c = 0$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$V_{OL} = V_{DD} - V_T + \frac{1}{\beta_n R_L} - \sqrt{\left( V_{DD} - V_T + \frac{1}{\beta_n R_L} \right)^2 - \frac{2V_{DD}}{\beta_n R_L}}$$

### \* Calculation of $V_{IL}$

By definition,  $V_{IL}$  is the smaller of the two input voltage values at which the slope of the VTC becomes equal to -1  
i.e.  $dV_{out} / dV_{in} = -1$

When  $V_{in} = V_{IL}$ , the output voltage  $V_{out}$  is slightly smaller than  $V_{OH}$ .

Consequently,  $V_{out} > V_{in} - V_T$ , and the transistor operates in saturation.

Thus,

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{\beta_n}{2} (V_{in} - V_T)^2$$

To satisfy the derivative condition, we differentiate both sides of the equation with respect to  $V_{in}$

$$-\frac{1}{R_L} \cdot \frac{dV_{out}}{dV_{in}} = \beta_n (V_{in} - V_t)$$

Then, we substitute  $\frac{dV_{out}}{dV_{in}} = -1$

$$\Rightarrow -\frac{1}{R_L} \cdot (-1) = \beta_n (V_{IL} - V_t)$$

$$\Rightarrow \boxed{V_{IL} = V_t + \frac{1}{\beta_n R_L}}$$

The value of the output voltage when the input is equal to  $V_{IL}$  can also be found by substituting  $V_{IL}$  in the original equation

$$V_{out} (V_{in} = V_{IL}) = V_{DD} - \frac{\beta_n R_L}{2} \left[ V_t + \frac{1}{\beta_n R_L} - V_t \right]^2$$

$$\boxed{V_{out} = V_{DD} - \frac{1}{2\beta_n R_L}}$$

## \* Calculation of $V_{IH}$

$V_{IH}$  is the larger of the two voltage points at which the slope = -1. When the input voltage  $V_{in} = V_{IH}$ ,  $V_{out}$  is slightly larger than the output low voltage  $V_{OL}$ . Hence,  $V_{out} < V_{in} - V_t$ , and the driver transistor operates in the linear region. Thus,

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{\beta_n}{2} \left[ 2(V_{in} - V_t) V_{out} - V_{out}^2 \right]$$

Differentiating both sides with respect to  $V_{in}$ , we obtain

$$-\frac{1}{R_L} \cdot \frac{dV_{out}}{dV_{in}} = \frac{\beta_n}{2} \left[ 2(V_{in} - V_t) \frac{dV_{out}}{dV_{in}} + 2V_{out} - 2V_{out} \cdot \frac{dV_{out}}{dV_{in}} \right]$$

Now substituting  $\frac{dV_{out}}{dV_{in}} = -1$  at  $V_{in} = V_{IH}$

$$-\frac{1}{R_L} \cdot (-1) = \beta_n \left[ (V_{IH} - V_t) \cdot (-1) + 2V_{out} \right]$$

$$\Rightarrow \boxed{V_{IH} = V_t + 2V_{out} - \frac{1}{\beta_n R_L}}$$



Next, we can find  $V_{out}$  when  $V_{in} = V_{IH}$  by substituting  $V_{IH}$  in the original equation

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{\beta_n}{2} \left[ 2 \left( V_t + 2V_{out} - \frac{1}{\beta_n R_L} - V_t \right) V_{out} - V_{out}^2 \right]$$

The positive solution of this second-order equation gives

$$V_{out} (V_{in} = V_{IH}) = \sqrt{\frac{2}{3} \frac{V_{DD}}{\beta_n R_L}}$$

The four critical voltage points  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$ ,  $V_{IH}$  can now be used to determine the noise margins,  $NML$  and  $NMH$  of the resistive-load inverter.

\* Calculation of the inverter threshold voltage

$V_{th}$ :

The inverter threshold voltage  $V_{th}$ , which is considered as the transition voltage is defined as the point on VTC where  $V_{in} = V_{out}$ . Note that under this condition, the transistor will be in saturation since  $V_{in} - V_t < V_{out}$ .


Thus, substituting  $V_{out} = V_{in}$  in the following equation:

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{\beta_n}{2} [V_{in} - V_t]^2$$

$$\Rightarrow \frac{V_{DD} - V_{out}}{R_L} = \frac{\beta_n}{2} [V_{out} - V_t]^2$$

Solving this equation for  $V_{out}$  gives  $V_{th}$ .

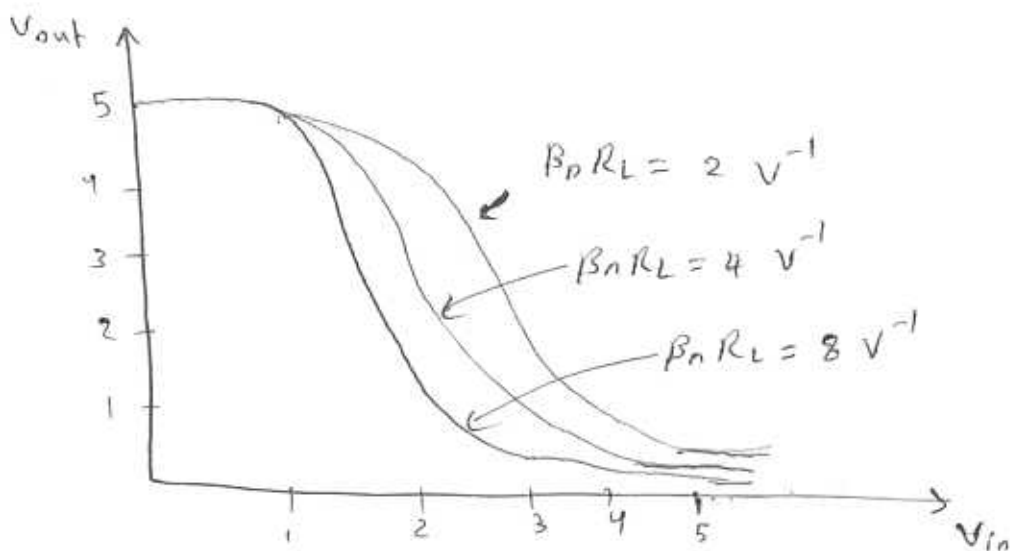\* As can be seen from the previous analysis that the term  $\beta_n R_L$  plays an important role in determining the shape of the voltage transfer characteristic.  $V_{OH}$  is determined by the power supply voltage  $V_{DD}$ . Among the other three critical voltage points,  $V_{OL}$  receives primary attention while  $V_{IL}$  and  $V_{IH}$  are usually treated as secondary design variables.



The larger the  $\beta_n R_L$  values, the smaller the output low voltage and the shape of the VTC approaches that of the ideal inverter, with very large transition slope.

### \* Power Consumption

The average DC power consumption of the resistive load inverter is found by considering two cases  $V_{in} = V_{OL}$  (low) and  $V_{in} = V_{OH}$  (high)

$$P_{DC} = \frac{V_{DD}}{2} [I_{DC}(V_{in} = \text{low}) + I_{DC}(V_{in} = \text{high})]$$

When  $V_{in} = V_{OL}$ , the transistor is cutoff and  $I_D = I_R = 0$ , and power dissipation is zero.

When  $V_{in} = V_{OH}$ , the transistor is on and the current drawn from the power supply is given as

$$I_D = I_R = \frac{V_{DD} - V_{OL}}{R_L}$$

$$\text{Thus, } P_{DC} (\text{average}) = \frac{V_{DD}}{2} \cdot \frac{(V_{DD} - V_{OL})}{R_L}$$

### Example

Consider the following inverter design problem:  
Given  $V_{DD} = 5V$ ,  $\mu_n C_{ox} = 30 \mu A/V^2$ , and  $V_t = 1V$ . Design a resistive-load inverter with  $V_{OL} = 0.2V$ . Specifically, determine the  $(W/L)$  ratio of the transistor and the value of the load resistor  $R_L$  that achieve the required  $V_{OL}$ .

### Solution

Note that the transistor operates in the linear region when the output voltage is equal to  $V_{OL}$  and the input voltage is equal to  $V_{OH} = V_{DD}$ .

Thus,

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \left[ 2(V_{OH} - V_t) \cdot V_{OL} - V_{OL}^2 \right]$$

Assuming  $V_{OL} = 0.2$ ,

$$\Rightarrow \frac{5 - 0.2}{R_L} = \frac{30 \times 10^{-6}}{2} \cdot \frac{W}{L} \left( (2)(4) \cdot (0.2) - (0.2)^2 \right)$$

$$\Rightarrow \frac{W}{L} \cdot R_L = 2.05 \times 10^5 \Omega$$

The selection of the pair of values to use for  $(\frac{W}{L})$  and  $R_L$  in the final design depends on tradeoff between the power consumption of the circuit and the silicon area.

### Example

Consider a resistive load inverter with  $V_{DD} = 5V$ ,  $\mu_n C_{ox} = 20 \mu A/V^2$ ,  $V_t = 0.8V$ ,  $R_L = 200 k\Omega$ , and  $W/L = 2$ . Calculate the critical voltages ( $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$ ,  $V_{IH}$ ) and the noise margins of the circuit.

### Solution

$$V_{OH} = V_{DD} = 5V$$

$$\beta_n = \mu_n C_{ox} \frac{W}{L} = 40 \mu A/V^2$$

$$\beta_n R_L = 8 V^{-1}$$

$$\begin{aligned} V_{OL} &= V_{DD} - V_t + \frac{1}{\beta_n R_L} - \sqrt{\left(V_{DD} - V_t + \frac{1}{\beta_n R_L}\right)^2 - \frac{2V_{DD}}{\beta_n R_L}} \\ &= 5 - 0.8 + \frac{1}{8} - \sqrt{\left(5 - 0.8 + \frac{1}{8}\right)^2 - \frac{2 \times 5}{8}} \\ &= 0.147V \end{aligned}$$

$$V_{IL} = V_t + \frac{1}{\beta_n R_L} = 0.8 + \frac{1}{8} = 0.925V$$

$$\begin{aligned} V_{IH} &= V_t + \sqrt{\frac{8}{3} \frac{V_{DD}}{\beta_n R_L}} - \frac{1}{\beta_n R_L} \\ &= 0.8 + \sqrt{\frac{8}{3} \cdot \frac{5}{8}} - \frac{1}{8} = 1.97V \end{aligned}$$

$$NML = V_{IL} - V_{OL} = 0.93 - 0.15 = 0.78V$$

$$NMA = V_{OH} - V_{IH} = 5.0 - 1.97 = 3.03V$$

Note that  $NML$  is quite low here. A good  $NML$  should be at least 25%  $V_{DD} = 1.25V$ .