

COE 360 Principles of VLSI Design
Dr. Aiman El-Maleh

Lecture#16


Inverter-Equivalent Circuits

COE 360 : Lecture #16Inverter - Equivalent Circuits

Let us first consider the depletion-load NAND gate shown below.

$$I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[2(V_{GS,A} - V_T) V_{DS,A} - V_{DS,A}^2 \right]$$
 
$$I_{D,B} = \frac{1}{2} \left(\frac{W}{L} \right)_B \mu_n C_{ox} \left[2(V_{GS,B} - V_T) V_{DS,B} - V_{DS,B}^2 \right]$$



It is assumed here that $V_{T,A} = V_{T,B} = V_T$,
and that $(\mu_n C_{ox})_A = (\mu_n C_{ox})_B$.

Note that $V_{GS,A} = V_{GS,B} - V_{DS,B}$, and

that $V_{DS,A} = V_{out} - V_{DS,B}$

$$I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[2(V_{GS,B} - V_{DS,B} - V_T) (V_{out} - V_{DS,B}) - (V_{out} - V_{DS,B})^2 \right]$$

$$\Rightarrow I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[2 (V_{GS,B} - V_T) (V_{out} - V_{DS,B}) - 2 (V_{DS,B}) (V_{out} - V_{DS,B}) - (V_{out} - V_{DS,B})^2 \right]$$

$$\Rightarrow I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[2 (V_{GS,B} - V_T) V_{out} - 2 (V_{GS,B} - V_T) V_{DS,B} - 2 V_{DS,B} V_{out} + 2 V_{DS,B}^2 - V_{out}^2 + 2 V_{out} V_{DS,B} - V_{DS,B}^2 \right]$$

$$\Rightarrow I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[2 (V_{GS,B} - V_T) V_{out} - V_{out}^2 - [2 (V_{GS,B} - V_T) V_{DS,B} - V_{DS,B}^2] \right]$$

$$\Rightarrow I_{D,A} = \frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox} \left[\frac{I_{D,eq}}{\frac{1}{2} \left(\frac{W}{L} \right)_{eq} \mu_n C_{ox}} - \frac{I_{D,B}}{\frac{1}{2} \left(\frac{W}{L} \right)_B \mu_n C_{ox}} \right]$$

$$\Rightarrow \frac{I_{D,A}}{\frac{1}{2} \left(\frac{W}{L} \right)_A \mu_n C_{ox}} = \frac{I_{D,eq}}{\frac{1}{2} \left(\frac{W}{L} \right)_{eq} \mu_n C_{ox}} - \frac{I_{D,B}}{\frac{1}{2} \left(\frac{W}{L} \right)_B \mu_n C_{ox}}$$


$$\Rightarrow \frac{I_{D,eq}}{\frac{1}{2} \left(\frac{W}{L}\right)_{eq} \mu_n C_{ox}} = \frac{I_{D,A}}{\frac{1}{2} \left(\frac{W}{L}\right)_A \mu_n C_{ox}} + \frac{I_{D,B}}{\frac{1}{2} \left(\frac{W}{L}\right)_B \mu_n C_{ox}}$$

Note that $I_{D,A} = I_{D,B} = I_{D,eq}$


$$\Rightarrow \frac{1}{\left(\frac{W}{L}\right)_{eq}} = \frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_B}$$

$$\Rightarrow \left(\frac{W}{L}\right)_{eq} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_B}}$$

 Thus, the inverter equivalent to the 2-input NAND gate assuming both inputs have the same value is shown below




For example,

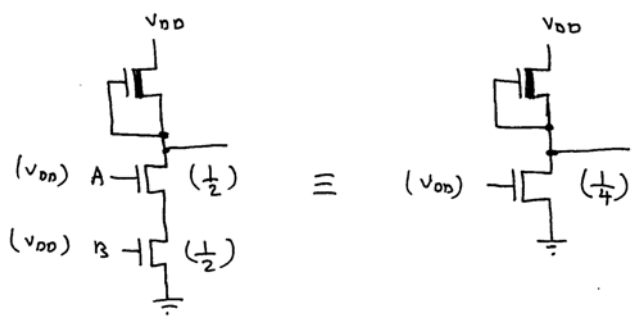

For a generalized n -input NAND gates, which consists of n series connected driver transistors, the $(\frac{W}{L})$ ratio of the equivalent driver transistor

is
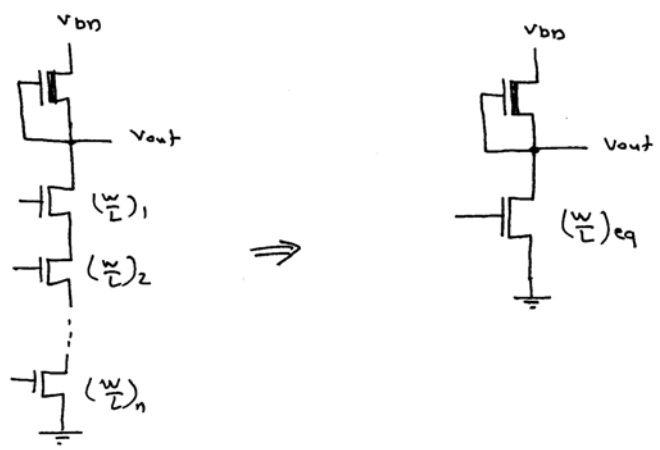
$$\left(\frac{W}{L}\right)_{\text{equivalent}} = \frac{1}{\sum_{k(1:n)} \frac{1}{\left(\frac{W}{L}\right)_k}}$$



Note that we have neglected the substrate-bias effect, and assumed that the threshold voltages of all transistors equals to V_t .

If the series-connected transistors are identical i.e., $(\frac{W}{L})_1 = (\frac{W}{L})_2 = \dots = (\frac{W}{L})_n$, the width-to-length ratio of the equivalent transistor becomes

$$(\frac{W}{L})_{\text{equivalent}} = \frac{1}{n} (\frac{W}{L})$$


- NOR gates

Let us consider the 2-input NOR gate shown below.

Note that $I_D = I_{D,A} + I_{D,B}$

$$I_{D,A} = \frac{1}{2} (\frac{W}{L})_A \mu_n C_{ox} [2(V_{GS,A} - V_t) V_{DS,A} - V_{DS,A}^2]$$
 
$$I_{D,B} = \frac{1}{2} (\frac{W}{L})_B \mu_n C_{ox} [2(V_{GS,B} - V_t) V_{DS,B} - V_{DS,B}^2]$$



Note that $V_{GS,A} = V_{GS,B} = V_{GS}$ and that

$$V_{DS,A} = V_{DS,B} = V_{out}$$

$$\Rightarrow \frac{1}{2} \left(\frac{W}{L}\right)_{eq} \mu_n C_{ox} \left[2(V_{GS} - V_t) V_{out} - V_{out}^2 \right]$$


$$= \frac{1}{2} \left(\frac{W}{L}\right)_A \mu_n C_{ox} \left[2(V_{GS} - V_t) V_{out} - V_{out}^2 \right]$$

$$+ \frac{1}{2} \left(\frac{W}{L}\right)_B \mu_n C_{ox} \left[2(V_{GS} - V_t) V_{out} - V_{out}^2 \right]$$


$$= \frac{1}{2} \left[\left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_B \right] \mu_n C_{ox} \left[2(V_{GS} - V_t) V_{out} - V_{out}^2 \right]$$

$$\Rightarrow \left(\frac{W}{L}\right)_{eq} = \left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_B$$

For example,

 

\equiv

 


Thus, an n-input NOR gate can be reduced to an equivalent inverter with the following $(\frac{W}{L})$ ratio:

$$\left(\frac{W}{L}\right)_{\text{equivalent}} = \sum_{k(\text{on})} \left(\frac{W}{L}\right)_k$$

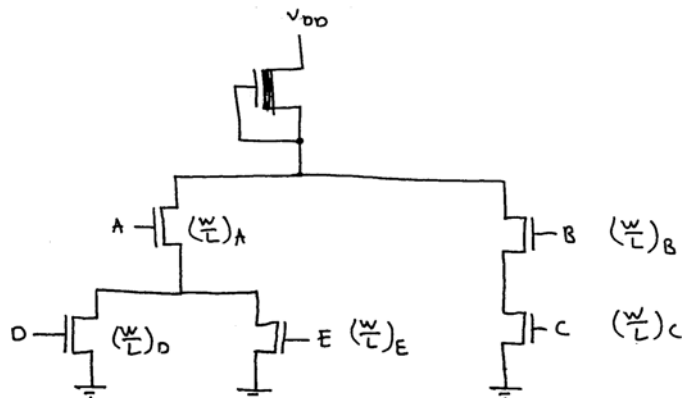Example

Find the inverter-equivalent of the following circuit assuming all inputs are logic-high.




The equivalent inverter shown below has the following $(\frac{W}{L})_{eq}$ ratio.

$$\left(\frac{W}{L}\right)_{eq} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_C}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E}}$$

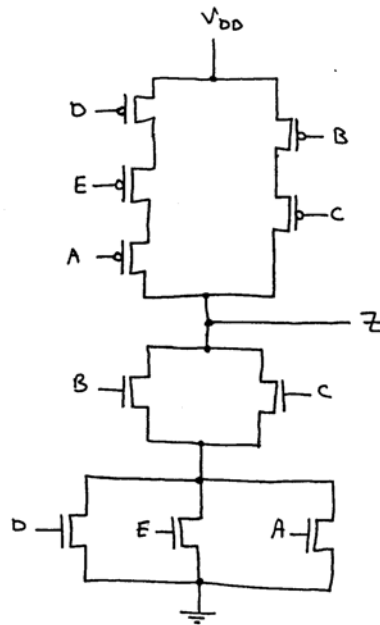Example

Find an equivalent CMOS inverter circuit for the following circuit for simultaneous switching of all inputs, assuming that $\left(\frac{W}{L}\right)_p = 15$ for all pMOS transistors and $\left(\frac{W}{L}\right)_n = 10$ for all nMOS transistors.



$$\begin{aligned} \left(\frac{W}{L}\right)_{n,eq} &= \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E + \left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_B + \left(\frac{W}{L}\right)_C}} \\ &= \frac{1}{\frac{1}{30} + \frac{1}{20}} = 12 \end{aligned}$$

$$\begin{aligned} \left(\frac{W}{L}\right)_{p,eq} &= \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_D} + \frac{1}{\left(\frac{W}{L}\right)_E} + \frac{1}{\left(\frac{W}{L}\right)_A}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_C}} \\ &= \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15}} + \frac{1}{\frac{1}{15} + \frac{1}{15}} = 12.5 \end{aligned}$$

Thus, the equivalent CMOS inverter is shown below:

