 
 


**COE 360 Principles of VLSI Design**  
**Dr. Aiman El-Maleh**

**Lecture#4**


**Logic Design using CMOS**

1. NMOS transistor basic structure
2. PMOS transistor basic structure
3. Transmission gate
4. Nand gate
5. Nor gate
6. CMOS gates

- n-transistor (nMOS):


- An MOS (metal-oxide-silicon) structure is created by superimposing several layers of conducting, insulating, and transistor forming materials.
- CMOS technology provides two types of transistors, an n-type transistor (nMOS) and a p-type transistor (pMOS).

- p-transistor (pMOS)

 

- gate is a control input - it affects the flow of current between the source and drain.
- In an nmos transistor, the source is the one with lower voltage (source of negative charges).
- In a pmos transistor, the source is the one with higher voltage (source of positive charges).

 - An nmos transistor produces a good 0 but a poor 1




- \* An nmos transistor conducts if the potential difference between the gate and the source  $V_{gs} > V_T$  (threshold voltage) ( $V_T > 0$ )
- \* Source is like the substrate i.e. the node with potential  $V_{SS}$ .
- \* If  $V_g = V_{SS}$  (low), then regardless of the values on  $V_{in}$  &  $V_{out}$ , the transistor will be off since  $V_{gs} < V_T$ . Thus,  $V_{out}$  will be floating and has a high impedance value  $Z$ .
- \* If  $V_g = V_{DD}$ ,  $V_{in} = V_{SS}$ , and  $V_{out} = V_{DD}$ , the transistor will be on since  $V_{gs} = V_{DD} > V_T$  until all the charge on  $V_{out}$  is eliminated and  $V_{out} = V_{SS}$ . Thus, we get a good 0.
- \* If  $V_g = V_{DD}$ ,  $V_{in} = V_{DD}$ , and  $V_{out} = V_{SS}$ , then  $V_{out}$  will be the source and  $V_{in}$  the drain, and current will flow from  $V_{in}$  to  $V_{out}$  and the capacitance will start charging.

the transistor will continue conducting as long as  $V_{gs}$ , the potential difference between the gate and  $V_{out} > V_T$ . At the point where  $V_{out} = V_{DD} - V_T$ ,  $V_{gs}$  becomes equal to  $V_T$  and the transistor ceases conduction.

Thus, the maximum value that  $V_{out}$  can get is  $V_{DD} - V_T$ , which is a poor 1.

 - A pmos transistor produces a good 1 but a poor 0.




- \* A pmos transistor conducts if the potential difference between the gate and the source  $V_{gs} < +V_T$ . ( $V_T < 0$ )
- \* Source is the terminal connected to  $V_{DD}$
- \* If  $V_g = V_{DD}$  (high), then regardless of the values on  $V_{in}$  &  $V_{out}$ , the transistor will be off since  $V_{gs} > +V_T$ . Thus,  $V_{out}$  will be floating and has a high impedance value  $Z$ .

\* If  $V_g = V_{ss}$  (low), and  $V_{in} = V_{DD}$ , the transistor will be on since the potential difference between the gate and  $V_{in}$  (source) =  $-V_{DD} < +V_T$ . Thus, current flows and charges the capacitor towards  $V_{DD}$ , and we get a good 1.

+ If  $V_g = V_{ss}$ , and  $V_{in} = V_{ss}$ , and  $V_{out} = V_{DD}$ ,  $V_{out}$  in this case will be the source and  $V_{in}$  the drain. Since  $V_{gs} = -V_{DD} < +V_T$  the transistor will be on and the load capacitor discharges until  $V_{out} = V_T$ , at which point the transistor ceases conducting since  $V_{gs} = +V_T$ . Thus, the p-transistor produces a poor 0 equal to  $V_T$ .

 
- To obtain both a good 0 and a good 1, we combine an n-transistor and a p-transistor in parallel as shown below:



This switch is called a complementary switch or C-switch, transmission gate or pass gate.


- \* If  $V_g = V_{ss}$ , both the n and p transistors will be off.
- \* If  $V_g = V_{DD}$ ,  $V_{in} = V_{ss}$ , and  $V_{out} = V_{DD}$  both transistors will be on, and the load capacitance on  $V_{out}$  will discharge. However, when  $V_{out} = V_T$ , the p-transistor stops conducting while the n-mos transistor continues conducting until  $V_{out} = V_{ss}$ . So, we get a good 0.
- \* If  $V_g = V_{DD}$ ,  $V_{in} = V_{DD}$ , and  $V_{out} = V_{ss}$  both transistors will be on, and the load capacitance on  $V_{out}$  will charge. However, when  $V_{out} = V_{DD} - V_T$ , the n-trans. stops conducting while the p-transistor continues conduction and we get  $V_{out} = V_{DD}$ . So, we get a good 1.

- NAND gate:

 


$$V_{out} = (A \cdot B)'$$

nmos

 

$$V_{out} = \bar{A} + \bar{B} = (A \cdot B)'$$

pmos

 


$$V_{out} = (A \cdot B)'$$

cmos




- NOR gate:

 


$$V_{out} = (A + B)'$$

nmos

 

$$V_{out} = \overline{A \cdot B} = (A + B)'$$


pmos

 

$$V_{out} = (A + B)'$$

cmos

- CMOS gates:

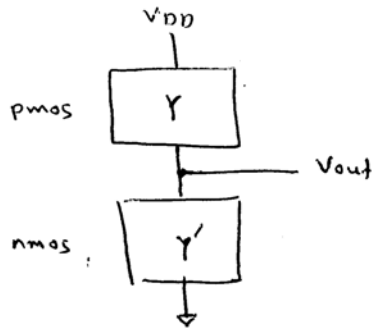

To implement a function  $Y$  in CMOS, implement in the lower part  $\bar{Y}$  using nmos and in the upper part  $Y$  using pmos.

Example: Implement  $Y = (A \cdot B + C \cdot D)'$

$$\bar{Y} = AB + CD, \quad Y = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})$$

