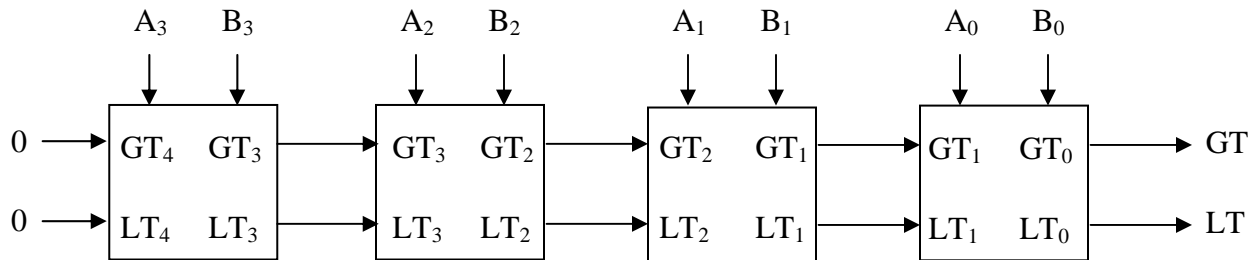


**COE 360, Principles of VLSI Design, Term 991  
Course Project**

**4-bit Comparator**

Due date: Saturday, December 11


It is required to design a 4-bit comparator using CMOS technology. The comparator gets two 4-bit numbers  $A=A_3A_2A_1A_0$  and  $B=B_3B_2B_1B_0$ , and produces two outputs GT and LT. If  $A>B$ , then the output signal GT is set to 1, and if  $A<B$ , then the output signal LT is set to 1, otherwise both signals will be set to 0, which indicates that the two numbers are equal (i.e.  $A=B$ ). The 4-bit comparator circuit can be designed in a modular way as shown below.



**Figure 1 4-bit comparator - block diagram**

The truth table and general arrangement for a binary 1-bit comparator bit-slice is shown below where  $A_i$  and  $B_i$  are the two bits to be compared,  $GT_{i+1}$  and  $LT_{i+1}$  are the inputs from outputs of the previous stage and  $GT_i$  and  $LT_i$  are the outputs of the current stage. If  $A_i > B_i$ , then  $GT_i = 1$ , and if  $A_i < B_i$ , then  $LT_i = 1$ . Both  $GT_i$  and  $LT_i$  will be equal to 0 if  $A_i = B_i$ .

Inputs				Outputs	
$A_i$	$B_i$	$GT_{i+1}$	$LT_{i+1}$	$GT_i$	$LT_i$
X	X	1	0	1	0
X	X	0	1	0	1
0	0	0	0	0	0
0	1	0	0	0	1
1	0	0	0	1	0
1	1	0	0	0	0

 

**Figure 2 Comparator cell behavior**

**To complete the project, you need to do the following steps:**

1. Design the gate-level and the transistor-level schematic of the basic cell of 1-bit comparator.
2. Draw the stick diagram layout of the basic cell of 1-bit comparator.
3. Using MAGIC, draw the initial layout of the basic cell of 1-bit comparator having all nMOS transistors with a (W/L) ratio of 1, and all pMOS transistors with a (W/L) ratio of 2. Assume that the minimum feature size is used for all transistors.
4. Extract the transistor-level circuit from the layout of the basic cell, using the command *extract*, convert it into the simulator format, using *ext2sim*, and then simulate it using *irsim* and verify that it is working properly for all input combinations.
5. Extract the SPICE model of the basic comparator cell, using the command *ext2spice*. Then, using SPICE, determine the maximum propagation delay across the cell. You need to use the following models for the **nfet** and **pfet** transistors:  

```
.Model nfet nmos (vto=0.8 lambda=0 gamma=0 cj=1.4e-4 cjsw=4.5e-10
ld=0.1e-6 phi=0.6 tox=100e-9 rsh=3)
.Model pfet pmos (vto=-0.8 lambda=0 gamma=0 cj=5.6e-4 cjsw=7.1e-11
ld=0.1e-6 phi=0.6 tox=100e-9 rsh=3)
```
6. Draw the layout of the 4-bit comparator circuit based on its basic cell using the *array* command. Then, simulate it using *irsim* to verify that it is working properly.
7. Deduce the maximum propagation delay of the 4-bit comparator based on the maximum delay across one cell. Then, extract the SPICE model of the 4-bit comparator and determine the maximum propagation delay across it. Compare your estimated delay to what you found based on spice and comment about it.
11. Using the **power-meter** technique, determine the maximum power dissipated by the basic comparator cell. Then, determine the maximum power dissipated by the 4-bit comparator. Comment on your observations.
12. Optimize the speed of the 4-bit comparator circuit by resizing the transistors width and length to reduce the maximum propagation delay of the initial design by 50%. Change your spice model based on the new transistor sizes and verify it. (Note: You do not need to redraw the layout for this part.)
13. Right a report describing your design. The report should include the following:
  - Gate-level schematic for the basic comparator cell.
  - Transistor-level schematic for the basic comparator cell.
  - Stick-diagram layout for the basic comparator cell.
  - Layout printout for the basic comparator cell and for the 4-bit comparator.

- Irsim simulation printouts indicating that the basic comparator cell and the 4-bit comparator are working properly.
- Spice simulation printouts indicating the maximum propagation delay across the basic comparator cell and the 4-bit comparator for the initial design.
- Spice simulation printouts indicating the maximum propagation delay across the basic comparator cell and the 4-bit comparator for the optimized design.
- Spice simulation printouts indicating the maximum power dissipation, using the power-meter technique, across the basic comparator cell and the 4-bit comparator for the initial design.

**The project is to be conducted by a group of a maximum of three students. Area optimization and neatness of the layout design will be evaluated. Organization and completeness of the report is important.**