

Name:

Id#

COE 360, Term 071

Principles of VLSI Design  
Quiz# 2

Date: Wednesday, Oct. 24, 2007

**Q1.** Implement the following functions using **CMOS** with the smallest number of transistors possible. Note that transmission gates are to be used whenever this leads to a better implementation. Indicate the number of transistors needed for your implementation including the ones needed for inverting the inputs:

(1)  $F = A' B C + A' B' C'$

(2)  $F = A B + A C + B C$

- (3) A falling-edge triggered D-flip flop.