

Name:

Id#

**COE 360, Principles of VLSI Design, Term 002
Pop Quiz# 2**

Date: Tuesday, March 13

Implement the following Boolean function in CMOS using the smallest possible number of transistors assuming the availability of inverted inputs:

$$Y = [(A \cdot B + C) (D + E)]'$$