

Name: Key

Id#

COE 360, Principles of VLSI Design, Term 032
Quiz#2

Date: Sunday, March 14, 2004

Q1. Implement the following functions using CMOS with the smallest number of transistors possible. Indicate the number of transistors needed for your implementation:

(1) $F = ABC + ADC' + ABD$

$$F = ABC + ADC' + ABD$$

$$= A [BC + DC']$$


Let $x = BC + DC'$

$$\Rightarrow F = Ax$$

$$= \overline{[Ax]}$$

Let $y = [Ax]$

$$\Rightarrow F = \overline{y}$$

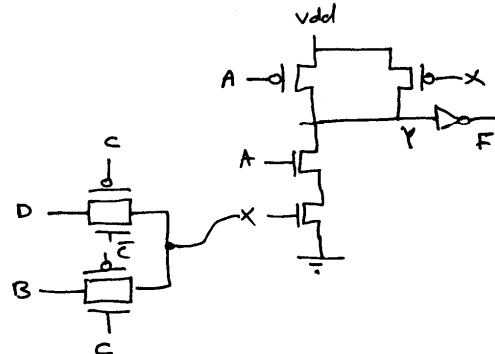


transistors = 6 + 4 + 2 = 12

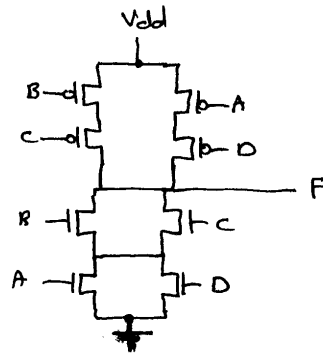(2) $F = [AB + AC + DB + DC]'$



$$F = [A [B+c] + D [B+c]]'$$

$$= [[B+c][A+D]]' = (B \cdot \overline{c}) + (\overline{A} \cdot \overline{D})$$




transistors = 8

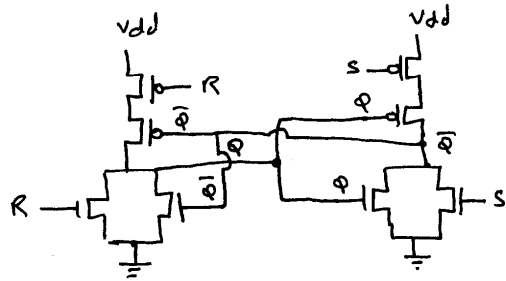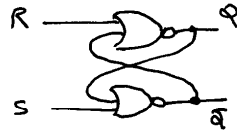- (3) An SR Latch. (Note that the SR latch does not have a clock input)



transistors = $4 + 4 = \underline{\underline{8}}$

- (4) A D-Latch.

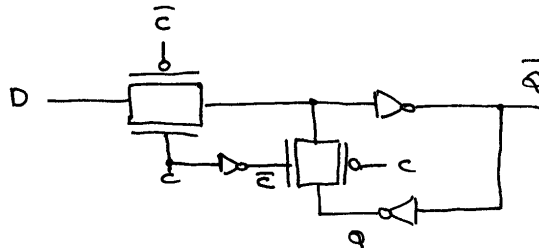

transistors = $\underline{\underline{10}}$