


COE 360, Term 071

Principles of VLSI Design  
Quiz# 2


Date: Wednesday, Oct. 24, 2007

**Q1.** Implement the following functions using CMOS with the smallest number of transistors possible. Note that transmission gates are to be used whenever this leads to a better implementation. Indicate the number of transistors needed for your implementation including the ones needed for inverting the inputs:

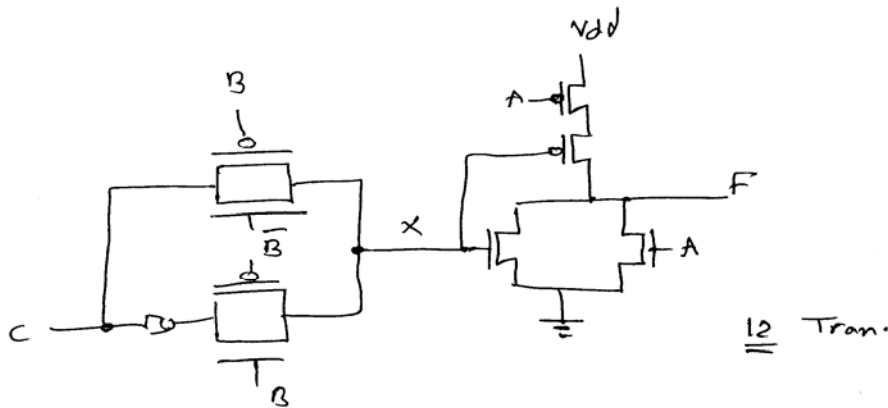(1)  $F = A' B C + A' B' C' = A' (B C + B' C') = [A + (B C' + B' C)]'$



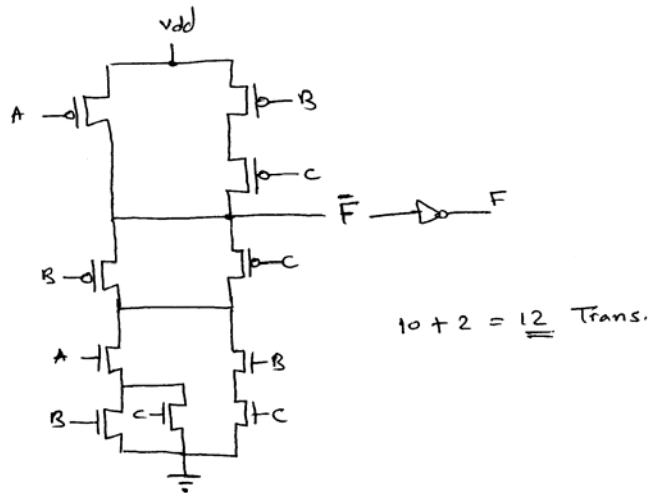(2)  $F = A B + A C + B C = [A (B + C) + B C]'$



(3) A falling-edge triggered D-flip flop.

