

Name:

Id#

COE 360, Principles of VLSI Design, Term 981
Quiz# 5


Date: Tuesday, June 18

(I) In a standard single metal N-Well CMOS fabrication process, the sheet resistance of various layers are given below:


<i>p-channel:</i>	15×10^3	Ω/SQ
<i>n-channel:</i>	6×10^3	Ω/SQ
<i>polysilicon:</i>	20	Ω/SQ
<i>n-diffusion:</i>	40	Ω/SQ
<i>p-diffusion:</i>	150	Ω/SQ
<i>Metal:</i>	0.05	Ω/SQ

Since the current flow in corner squares is not uniform, it is assumed that the value of a corner square is equal to 0.66 the normal square resistance.

 (i) Calculate the resistance of the following shapes for each of the polysilicon, n-diffusion, p-diffusion, and metal material types.



 (ii) Calculate the p-channel resistance of the following transistor.



- (II)** Assume that for a CMOS inverter, the rising and falling times are given as $3.0 C_L/\beta_p$ and $3.0 C_L/\beta_n$, respectively.
- (i) Design the circuit shown below such that the worst falling time is equal to 2ns, assuming that all dimensions of nmos and pmos transistors are equivalent.
- (ii) Compute the best and worst rising times for the circuit.
- (iii)** What will be the dimensions of the pmos transistors to achieve a worst rising time equal to 2ns.
Assume $C_L=0.1\text{pF}$, $\mu_n C_{ox}=100 \text{ uA/V}^2$, $\mu_p C_{ox}=40 \text{ uA/V}^2$, and $L=1\mu\text{m}$.

