

Name: Key

Id#

COE 360, Principles of VLSI Design, Term 043
Quiz# 6


Date: Sunday, August 7

Q1. Design a **Resistive-load Inverter** with $V_{OH}=5V$, $V_{OL}=0.2V$, and Average DC power $250 \mu W$. Assume that $V_{in}=1V$ and $\mu_n C_{ox}=50.5 \mu A/V^2$. Assume that the used technology is $0.5 \mu m$.

By KCL, $I_L = I_D$

When $V_{in} = V_{OH}$, $V_{out} = V_{OL}$

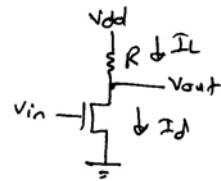$V_{gd} = V_{OH} - V_{OL} = 5 - 0.2 > V_t \Rightarrow$ transistor is in Linear mode.



$$\Rightarrow \frac{V_{dd} - V_{OL}}{R} = \frac{\beta_n}{2} [2(V_{DD} - V_t)V_{OL} - V_{OL}^2]$$

$$\Rightarrow \frac{5 - 0.2}{R} = \frac{\beta_n}{2} [2(5 - 1)0.2 - (0.2)^2]$$

$$\Rightarrow \frac{4.8}{R} = \frac{\beta_n}{2} [1.56]$$

$$\Rightarrow \beta_n = \frac{2 * 4.8}{1.56 R} = \frac{6.154}{R}$$

$$\text{Average DC power} = \frac{V_{dd}}{2} \cdot I = \frac{V_{dd}}{2} \frac{(V_{dd} - V_{OL})}{R}$$

$$\Rightarrow 250 \mu W = \frac{5}{2} \frac{4.8}{R}$$

$$\Rightarrow R = \frac{2.5 * 4.8}{250 \mu} = \underline{\underline{48 \text{ k}\Omega}}$$

$$\Rightarrow \beta_n = \frac{6.154}{48 \text{ k}} = 128.2 \frac{\mu A}{V^2}$$

$$\Rightarrow \mu_n C_{ox} \frac{W}{L} = 128.2 \frac{\mu A}{V^2}$$

$$\Rightarrow \frac{W}{L} = \frac{128.2 \mu}{50.5 \mu} = \underline{\underline{2.539}}$$

$$\Rightarrow L = \underline{\underline{0.5 \mu m}} \quad W = L * 2.539 = \underline{\underline{1.269 \mu m}}$$