

Name: KEY

Id#

COE 360, Term 071

Principles of VLSI Design

Quiz# 6


Due date: Saturday, Dec. 8, 2007

Q1. Design a **Resistive-load Inverter** with  $V_{OH}=5V$ ,  $V_{OL}=0.2V$ , and Average DC power  $250 \mu W$ . Assume that  $V_{tn}=1V$  and  $\mu_n C_{ox}=50.5 \mu A/V^2$ . Assume that the used technology is  $0.5 \mu m$ .

By KCL,  $I_L = I_D$

When  $V_{in} = V_{OH}$ ,  $V_{out} = V_{OL}$

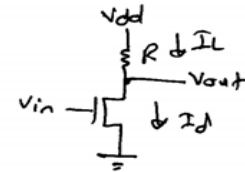$V_{gd} = V_{OH} - V_{OL} = 5 - 0.2 > V_t \Rightarrow$  transistor is in Linear mode.



$$\Rightarrow \frac{V_{dd} - V_{OL}}{R} = \frac{\beta_n}{2} [2(V_{OH} - V_t)V_{OL} - V_{OL}^2]$$

$$\Rightarrow \frac{5 - 0.2}{R} = \frac{\beta_n}{2} [2(5 - 1)0.2 - (0.2)^2]$$

$$\Rightarrow \frac{4.8}{R} = \frac{\beta_n}{2} [1.56]$$

$$\Rightarrow \beta_n = \frac{2 * 4.8}{1.56 R} = \frac{6.154}{R}$$

$$\text{Average DC power} = \frac{V_{dd}}{2} \cdot I = \frac{V_{dd}}{2} \frac{(V_{dd} - V_{OL})}{R}$$

$$\Rightarrow 250 \mu W = \frac{5}{2} \frac{4.8}{R}$$

$$\Rightarrow R = \frac{2.5 * 4.8}{250 \mu} = \underline{\underline{48 \text{ k}\Omega}}$$



$$\Rightarrow \beta_n = \frac{6.154}{48 \text{ k}} = 128.2 \frac{\mu A}{V^2}$$

$$\Rightarrow \mu_n C_{ox} \frac{W}{L} = 128.2 \frac{\mu A}{V^2}$$

$$\Rightarrow \frac{W}{L} = \frac{128.2 \mu}{50.5 \mu} = \underline{\underline{2.539}}$$

$$\Rightarrow L = \underline{\underline{0.5 \mu m}} \quad W = L * 2.539 = \underline{\underline{1.269 \mu m}}$$

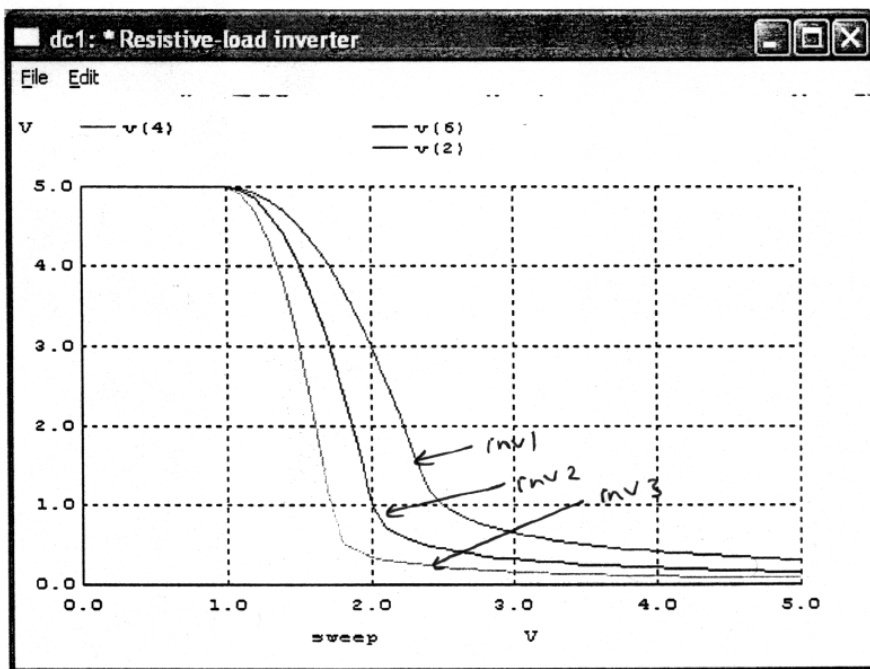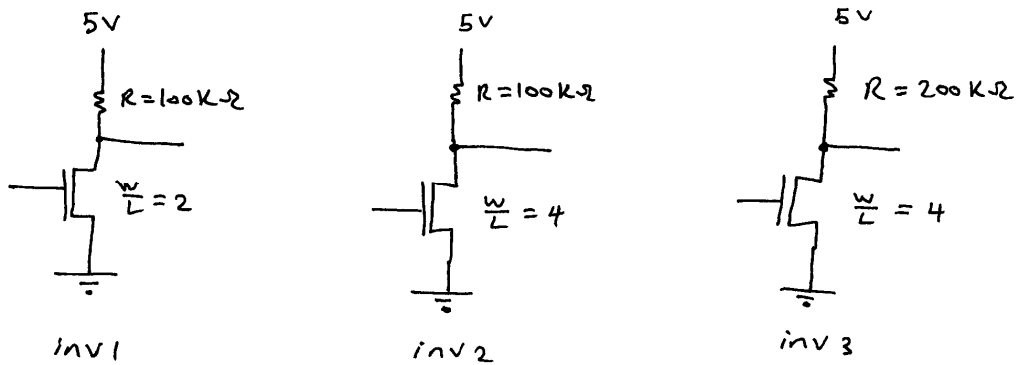**Q2.** Given the following three resistive-load inverters and the three voltage transfer characteristic graphs for the three inverters, select the voltage-transfer characteristic graph that corresponds to each inverter. Show your answer in the given graph. Justify your answer.



$$V_{OL} = \frac{R_d}{R_d + R_L} V_{DD}$$

$$\underline{\text{inv1}} : V_{OL} \approx \frac{\frac{1}{2} V_{DD}}{\frac{1}{2} + 100 \text{ k}\Omega} = \frac{\frac{1}{4} V_{DD}}{\frac{1}{4} + 50 \text{ k}\Omega}$$

$$\underline{\text{inv2}} : V_{OL} \approx \frac{\frac{1}{4} V_{DD}}{\frac{1}{4} + 100 \text{ k}\Omega}$$

$$\underline{\text{inv3}} : V_{OL} \approx \frac{\frac{1}{4} V_{DD}}{\frac{1}{4} + 200 \text{ k}\Omega}$$

$$\Rightarrow V_{OL}(\text{inv3}) < V_{OL}(\text{inv2}) < V_{OL}(\text{inv1})$$