

Name:

Id#

COE 360, Principles of VLSI Design, Term 032
Quiz# 7

Date: Tuesday, May 4

Q1. Given the following three resistive-load inverters and the three voltage transfer characteristic graphs for the three inverters, select the voltage-transfer characteristic graph that corresponds to each inverter. Show your answer in the given graph. Justify your answer.

