

## HW#3 Solution

**Q.1.** It is required to model in VHDL a parametrizable **n-bit Ripple Carry Adder**.

- (i) Describe the entity of the n-bit adder using GNERIC for passing the adder size.

```
entity FA is
  port (a, b, cin : in BIT;
        sum, cout : out BIT);
end FA;

-- description of adder using concurrent signal assignments
architecture behave of FA is
begin
  sum <= (a xor b) xor cin;
  cout <= (a and b) or (cin and a) or (cin and b);
end behave;
=====

entity RCA is
  generic(N : integer := 4);
  port (a : in BIT_vector(N downto 1);
        b : in BIT_vector(N downto 1);
        cin : in BIT;
        sum : out BIT_vector(N downto 1);
        cout : out BIT);
end RCA;
```

- (ii) Model architecture for the n-bit adder using GENERATE statement.


```
-- structural implementation of the N-bit adder
Use work.HW3.all;
architecture structural of RCA is
  FOR ALL : n1 USE ENTITY WORK.FA;
  signal carry : BIT_vector(0 to N);
begin
  carry(0) <= cin;
  cout <= carry(N);

  -- instantiate a single-bit adder N times
  gen: for I in 1 to N generate
```

```

add: n1 port map(
    a => a(I),
    b => b(I),
    cin => carry(I - 1),
    sum => sum(I),
    cout => carry(I));
end generate;
end structural;

```

 

(iii) Define a package called HW3 where you store all used components, functions and procedures inside the package and use the package when needed.

```

-----
--          PACKAGE DECLERATION
-----

```

```

Package HW3 is
Type integers IS ARRAY (0 to 9) OF INTEGER;

```

```

COMPONENT n1 port (a : in BIT;b : in BIT; cin : in BIT;sum : out BIT;cout : out BIT); END
COMPONENT ;

```

```

component RCA
    generic(N : integer);
    port (a : in Bit_vector(N downto 1);
          b : in Bit_vector(N downto 1);
          cin : in Bit;
          sum : out Bit_vector(N downto 1);
          cout : out Bit);
end component;

```

```

Procedure Int2Bin (Int: IN Integer; Bin : OUT BIT_VECTOR);

```

```

Procedure Bin2Int (Bin : IN BIT_VECTOR; Int: OUT Integer);

```

```

Procedure Apply_Data ( Signal Target: OUT Bit_Vector;

```

```

    Constant Period: IN Time) ;

```

```

Constant Values: IN Integers;

```

```

END HW3;
-----

```

```

--          PACKAGE BODY
-----

Package Body HW3 IS

Procedure Int2Bin (Int: IN Integer; Bin : OUT BIT_VECTOR) IS
    Variable Tmp: Integer;
Begin
    Tmp := Int;
    For I IN 1 To (Bin'Length) Loop
        If ( Tmp MOD 2 = 1) Then
            Bin(I) := '1' ;
        Else Bin(I) := '0' ;

            End If;
            Tmp := Tmp / 2;
        End Loop;
    End Int2Bin;

Procedure Bin2Int (Bin : IN BIT_VECTOR; Int: OUT Integer) IS
    Variable Result: Integer;
Begin
    Result := 0;
    For I IN Bin'RANGE Loop
        If Bin(I) = '1' Then
            Result := Result + 2**I;
        End If;
    End Loop;

    Int := Result / 2;
End Bin2Int;

Procedure Apply_Data (
    Signal Target: OUT Bit_Vector ;
    Constant Values: IN Integers;
    Constant Period: IN Time) IS

    Constant n : INTEGER := target'length;
    VARIABLE j: INTEGER;
    VARIABLE tmp, pos : INTEGER :=0;
    Variable Buf: Bit_Vector (N Downto 1);

Begin
    For I IN 0 To (integers'length -1) Loop
        tmp := values (i);
        j:= 1;
        WHILE j <= N LOOP
            IF(tmp MOD 2 = 1) THEN
                buf (j) := '1';
            else buf(j) :='0';
            end if;
            tmp:= tmp /2;
            j:= j +1;
        END LOOP;
        target <= TRANSPORT buf AFTER i * period;
    END LOOP;

End Apply_Data;

```



(v) Write a test bench for testing the n-bit ripple carry adder assuming that the input arguments will be read as integers from an input file and that the output will be stored as integer in an output file. Use TEXTIO package for this purpose. **Hint:** assignments scheduled on signals inside a process take effect after encountering a wait statement. Use the statement **wait for 0 ns** as many times as needed for this purpose.

```
entity testHW32 is
end;
```

```
-----
-- testbench for 4-bit adder
-----
```

```
Use work.HW3.all;
USE STD.TEXTIO.ALL;
```

```
architecture RCA4 of testHW32 is
constant N : integer := 4;
```

```
    signal a   : Bit_vector(N downto 1);
    signal b   : Bit_vector(N downto 1);
    signal cin  : Bit;
    signal sum  : Bit_vector(N downto 1);
    signal cout : Bit;
    FOR a1: RCA USE ENTITY WORK.RCA;
```

```
begin
```

```
    Process
```

```
        File Infile : Text IS IN "example1.txt" ;
        File Outfile: Text IS OUT "Outfile1.txt" ;
        Variable Out_Line, My_Line : Line;
        Variable Int_Val, Int_Value : Integer;
        Variable Buf1: Bit_Vector (N Downto 1);
        Variable Buf2: Bit_Vector (N Downto 1);
        Variable BufCin : Bit_Vector (1 Downto 1);
        Begin
```

```
            While Not (Endfile(Infile)) Loop
```

```
                Readline( Infile, My_Line); -- read a line from the input file
                Read( My_Line, Int_Val);      -- read a value from the line
                Int2Bin (Int_Val, BufCin);
```

```
                cin <= BufCin(1);
                wait for 0 ns;
                wait for 0 ns;
```

```
            --Readline( Infile, My_Line); -- read a line from the input file
            Read( My_Line, Int_Val);      -- read a value from the line
```

```

Int2Bin (Int_Val, Buf1);

a <= Buf1;
wait for 0 ns;
wait for 0 ns;

--Readline( Infile, My_Line); -- read a line from the input file
Read(My_Line, Int_Val);      -- read a value from the line
Int2Bin (Int_Val, Buf2);

b <= Buf2;
wait for 0 ns;
wait for 0 ns;

-- To let the input settle
wait for 100 ns;

Bin2Int (sum , Int_Val);
Write( Out_Line, Int_Val);      -- write the squared value to
the line
Write( Out_Line, cout);        -- write the squared value to the line
WriteLine( Outfile, Out_Line); -- write the line to the output file

        End Loop;
        wait;
    End Process;
a1: RCA generic map (n)
    port map ( a, b, cin, sum, cout);
END RCA4;

```

=====

THE INPUT FILE " example1.txt" :

```

1 0 1
1 5 6
1 6 7
1 8 2
1 10 5
0 11 1
0 9 9
0 3 11
0 15 1
0 14 0

```

THE OUTPUT FILE " Outfile1.txt" :


```

20
120
140
110
01
120
21

```

140  
01  
140

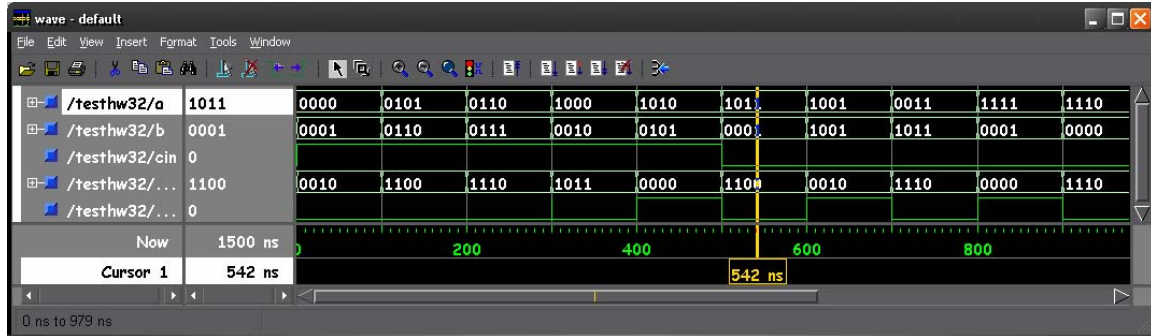The Last digit from each line is the carry out.



**Q.2.** It is required to model in VHDL a parametrizable **n-bit Array Multiplier**.

(i) Describe the entity of the n-bit array multiplier using GENERIC for passing the adder size. Note that while the multiplier inputs are n-bits each, the multiplier output is 2n bits.

```
entity AMul IS
generic (      N : INTEGER := 4);
port (  A, B : IN BIT_VECTOR(N downto 1);
        SUM : OUT BIT_VECTOR(2*N downto 1));
end AMul;
```

(ii) Model architecture for the n-bit array multiplier using GENERATE statement. Use the n-bit ripple carry adder modeled in Q1 in your solution.

```
USE WORK.HW3.ALL;
architecture Mine of AMul is
component RCA
    generic(N : integer);
    port (a,b  : in Bit_vector(N downto 1);
          cin : in Bit;
          sum  : out Bit_vector(N downto 1);
          cout : out Bit);
end component;
```

```
type MULARRAY is array (N+1 downto 1) of BIT_VECTOR((2*N+1) downto 1);
signal ANDING_BITS, FIRST, SECOND : MULARRAY;
```

```
signal TEMP_CIN, TEMP_COUT : BIT_VECTOR ((N+1) downto 1);
constant SIZE : INTEGER := 2*N+1;
```

```
BEGIN
```

```
FIRST_NUMBER_BITS: FOR I IN 1 TO N generate
begin
```

```
    SECOND_NUMBER_BITS: FOR J IN 1 TO N generate
    begin
        ANDING_BITS(I)(J+I-1) <= A(J) and B(I);
    end generate;
end generate;
```

```
-- first row
```

```
FIRST(1) <= ANDING_BITS(1);
```

```
TEMP: FOR I IN 1 TO N generate
```

```
begin
    SECOND(I) <= ANDING_BITS(I+1);
    SUMMING: RCA generic map (SIZE) port map (FIRST(I), SECOND(I),
    TEMP_CIN(I), FIRST(I+1), TEMP_COUT(I));
    TEMP_CIN(I+1) <= TEMP_COUT(I);
end generate;
```

```
sum <= FIRST(N+1)(2*N downto 1);
end mine;
```

(iii) Modify the test bench developed for the adder in Q1(v) to test the n-bit multiplier. Assume that the input arguments will be read as integers from an input file and that the output will be stored as integer in an output file. Use TEXTIO package for this purpose.

```
entity testMul is
end;
```

```
-----
-- testbench for 4-bit adder
-----
```

```
Use work.HW3.all;
USE STD.TEXTIO.ALL;
```

```
architecture mul of testMul is
constant N : integer := 4;
```

```
    signal a : Bit_vector(N downto 1);
    signal b : Bit_vector(N downto 1);
```



```
signal product : Bit_vector(2*N downto 1);
FOR a1: AMul USE ENTITY WORK.AMul;
```

```
begin
```

```
    Process
```

```
        File Infile : Text IS IN "example2.txt" ;
        File Outfile: Text IS OUT "Outfile2.txt" ;
        Variable Out_Line, My_Line : Line;
        Variable Int_Val, Int_Value : Integer;
        Variable Buf1: Bit_Vector (N Downto 1);
        Variable Buf2: Bit_Vector (N Downto 1);
        Begin
```

```
            While Not (Endfile(Infile)) Loop
```

```
                Readline( Infile, My_Line); -- read a line from the input
```

```
file
```

```
                Read( My_Line, Int_Val);          -- read a value from the
```

```
line
```

```
                Int2Bin (Int_Val, Buf1);
```

```
                a <= Buf1;
                wait for 0 ns;
                wait for 0 ns;
```

```
                --Readline( Infile, My_Line); -- read a line from the input
```

```
file
```

```
                Read(My_Line, Int_Val);          -- read a value from the
```

```
line
```

```
                Int2Bin (Int_Val, Buf2);
```

```
                b <= Buf2;
                wait for 0 ns;
                wait for 0 ns;
```

```
                wait for 100 ns;
```

```
                Bin2Int (product , Int_Val);
                Write( Out_Line, Int_Val);          -- write the squared
```

```
value to the line
```

```
                WriteLine( Outfile, Out_Line);    -- write the line to the
```

```
output file
```

```
            End Loop;
            wait;
```

```
        End Process;
```

```

a1: AMul generic map (n)
    port map ( a, b, product);
END mul;

```

THE INPUT FILE " example2.txt" :

```

15 15
9 13
8 4
12 3
6 6
1 1
15 0
11 11
13 12
10 10

```

THE OUTPUT FILE " Outfile2.txt" :

```

225
117
32
36
36
1
0
121
156
100

```

