

Name: KEY

Id#

COE 405, Term 062

Design & Modeling of Digital Systems

Quiz# 2

Date: Monday, March 26, 2007

Q.1. Given the following signal assignments, show all transactions placed on each signal. At each event, show transactions that are appended, overwritten, and expired including those occurring at delta time. Show resulting waveforms on each signal.

Architecture dataflow of signals IS

Signal A, B, C, D: Bit := '0';

Begin

A <= '1' after 10ns, '0' after 13ns, '1' after 17 ns, '0' after 25 ns, '1' after 26 ns;


B <= transport A after 5ns;

C <= A after 5 ns;

D <= Reject 2 ns Inertial A after 5 ns;

End dataflow;

| | | 0ns | 5ns | 10ns | 13ns | 15ns | 17ns | 18ns | 22ns | 25ns | 26ns | 30ns | 31ns |
|---|--------------------|--|--|------------------------------------|---------------------------|---------------------------|----------------------------------|----------------|----------------|-------|----------------|-------|------|
| A | Current Value | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| | Projected Waveform | (1,10) (0,13) (1,17) (0,25) (1,26) | (1,5) (0,8) (1,12) (0,20) (1,21) | (0,3) (1,7) (0,15) (1,16) | (1,4) (0,12) (1,13) | (1,2) (0,10) (1,11) | (0,8) (0,7) (1,9) (1,8) | (0,7) (1,8) | (0,3) (1,4) | (1,1) | φ | φ | φ |
| B | Current Value | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| | Projected Waveform | (0,5) | φ | (1,5) | (1,2) (0,5) | (0,3) | (0,1) (1,5) | (1,4) | φ | (0,5) | (0,4) (1,5) | (1,1) | φ |
| C | Current Value | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| | Projected Waveform | (0,5) | φ | (1,5) | (1,2) (0,5) | (0,3) | (0,1) (1,5) | (1,4) | φ | (0,5) | (0,4) (1,5) | (1,1) | φ |
| D | Current Value | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| | Projected Waveform | (0,5) | φ | (1,5) | (1,2) (0,5) | (0,3) | (0,1) (1,5) | (1,4) | φ | (0,5) | (0,4) (1,5) | (1,1) | φ |

 

Q.2. You are required to model an N-bit 2x1 MUX. The MUX entity declaration is given below:

```
Entity MUXN2x1 is
    Generic(N : Natural :=8);
    PORT (A, B : IN Bit_Vector(N-1 Downto 0);
          S: IN Bit;
          C: OUT Bit_Vector(N-1 Downto 0)
          );
End;
```

(i) Model a single-bit 2x1 MUX using behavioral model.

```
Entity MUX2x1 is
    PORT (A, B, S: IN BIT; C: OUT BIT);
END;
Architecture Behavioral of MUX2x1 is
Begin
    Process(A, B, S)
    Begin
        if (S='0') Then
            C <= A ;
        else
            C <= B;
        end if;
    End Process;

End;
```

- (ii) Using the model developed in (i) for the single-bit 2x1 MUX, develop a structural model for the N-bit 2x1 MUX using **generate** statement.

```
Entity MUXN2x1 is
  Generic(N : Natural :=8);
  PORT (A, B : IN Bit_Vector(N-1 Downto 0);
        S: IN Bit;
        C: OUT Bit_Vector(N-1 Downto 0)
        );
End;
Architecture Structural of MUXN2x1 is
  Component MUX2x1
    PORT (A, B, S: IN BIT; C: OUT BIT);
  ENd component;
  Begin

  MG: For I IN 0 To N-1 Generate
    MG: MUX2x1 port map (A(I), B(I), S, C(I));
  END Generate;

End;
```