
COE 405

Structural Specification of Hardware

Dr. Aiman H. El-Maleh
Computer Engineering Department
King Fahd University of Petroleum & Minerals


Outline

- **Parts Library**
- **Wiring of Primitives**
 - Single-bit comparator
- **Wiring Iterative Networks**
 - 4-bit comparator
 - For...Generate Statement
 - IF...Generate Statement
- **Modeling a Test Bench**
- **Binding Alternative**
- **Top Down Wiring**
 - Sequential Comparator
 - Byte Latch
 - Byte Comparator

2-2


Basic Components & Graphical Notation

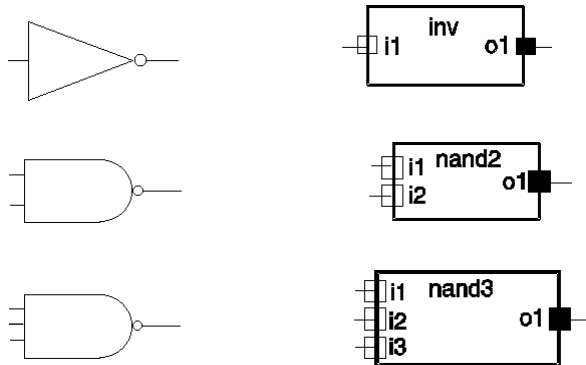- Three basic components are used
- Will use as the basic components of several designs
- A graphical notation helps clarify wiring



2-3





Entity Syntax

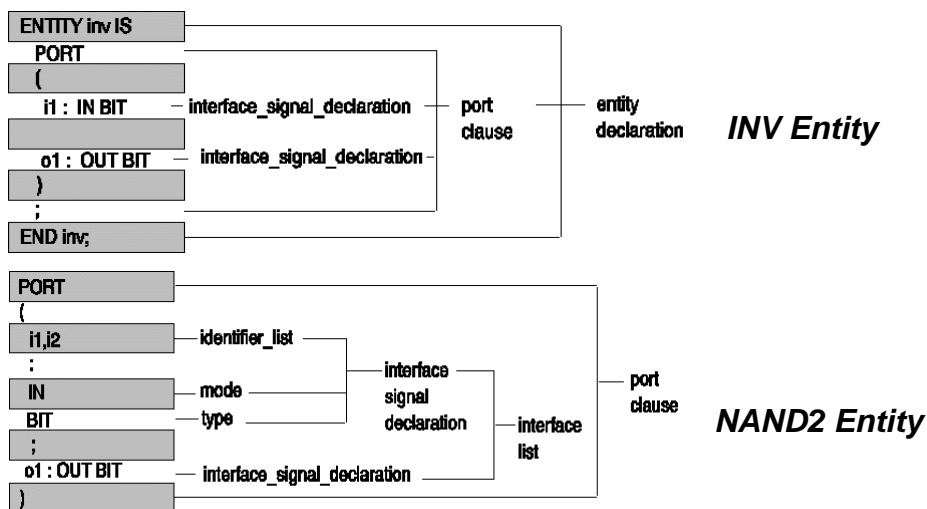

2-4

A Cascadable Single-Bit Comparator

    
- When $a > b$ the a_gt_b becomes 1
- When $a < b$ the a_lt_b becomes 1
- If $a = b$ outputs become the same as corresponding inputs



2-5


Structural Single-Bit Comparator

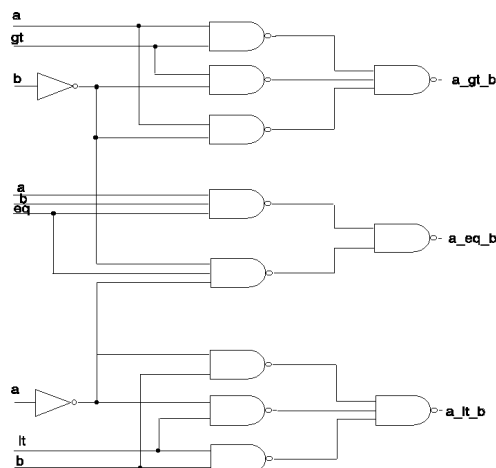- Design uses basic components
- The less-than and greater-than outputs use the same logic



2-6

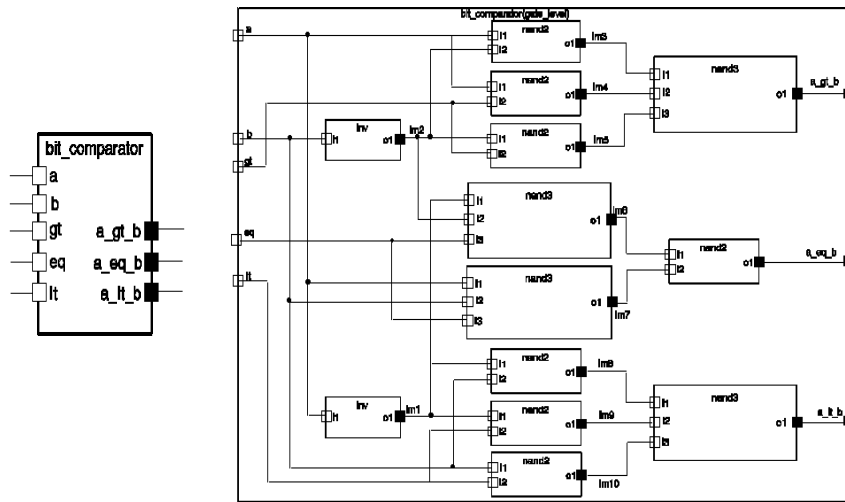Structural Single-Bit Comparator: Aspect Notation



2-7

Structural Model of Single-Bit Comparator ...

ENTITY bit_comparator IS

PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);

END bit_comparator;

ARCHITECTURE gate_level OF bit_comparator IS

--

COMPONENT n1 PORT (i1: IN BIT; o1: OUT BIT); END COMPONENT ;

COMPONENT n2 PORT (i1,i2: IN BIT; o1:OUT BIT); END COMPONENT;

COMPONENT n3 PORT (i1, i2, i3: IN BIT; o1: OUT BIT); END COMPONENT;

-- Component Configuration

FOR ALL : n1 USE ENTITY WORK.inv (single_delay);

FOR ALL : n2 USE ENTITY WORK.nand2 (single_delay);

FOR ALL : n3 USE ENTITY WORK.nand3 (single_delay);

--Intermediate signals

SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;

2-8

... Structural Model of Single-Bit Comparator

```
BEGIN
-- a_gt_b output
  g0 : n1 PORT MAP (a, im1);
  g1 : n1 PORT MAP (b, im2);
  g2 : n2 PORT MAP (a, im2, im3);
  g3 : n2 PORT MAP (a, gt, im4);
  g4 : n2 PORT MAP (im2, gt, im5);
  g5 : n3 PORT MAP (im3, im4, im5, a_gt_b);
-- a_eq_b output
  g6 : n3 PORT MAP (im1, im2, eq, im6);
  g7 : n3 PORT MAP (a, b, eq, im7);
  g8 : n2 PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
  g9 : n2 PORT MAP (im1, b, im8);
  g10 : n2 PORT MAP (im1, lt, im9);
  g11 : n2 PORT MAP (b, lt, im10);
  g12 : n3 PORT MAP (im8, im9, im10, a_lt_b);
END gate_level;
```


2-9

Netlist Description of Single-Bit Comparator

```
ARCHITECTURE netlist OF bit_comparator IS
SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;
BEGIN
-- a_gt_b output
  g0 : ENTITY Work.inv(single_delay) PORT MAP (a, im1);
  g1 : ENTITY Work.inv(single_delay) PORT MAP (b, im2);
  g2 : ENTITY Work.nand2(single_delay) PORT MAP (a, im2, im3);
  g3 : ENTITY Work.nand2(single_delay) PORT MAP (a, gt, im4);
  g4 : ENTITY Work.nand2(single_delay) PORT MAP (im2, gt, im5);
  g5 : ENTITY Work.nand3(single_delay) PORT MAP (im3, im4, im5, a_gt_b);
-- a_eq_b output
  g6 : ENTITY Work.nand3(single_delay) PORT MAP (im1, im2, eq, im6);
  g7 : ENTITY Work.nand3(single_delay) PORT MAP (a, b, eq, im7);
  g8 : ENTITY Work.nand2(single_delay) PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
  g9 : ENTITY Work.nand2(single_delay) PORT MAP (im1, b, im8);
  g10 : ENTITY Work.nand2(single_delay) PORT MAP (im1, lt, im9);
  g11 : ENTITY Work.nand2(single_delay) PORT MAP (b, lt, im10);
  g12 : ENTITY Work.nand3(single_delay) PORT MAP (im8, im9, im10, a_lt_b);
END netlist;
```


2-10

Syntax Details

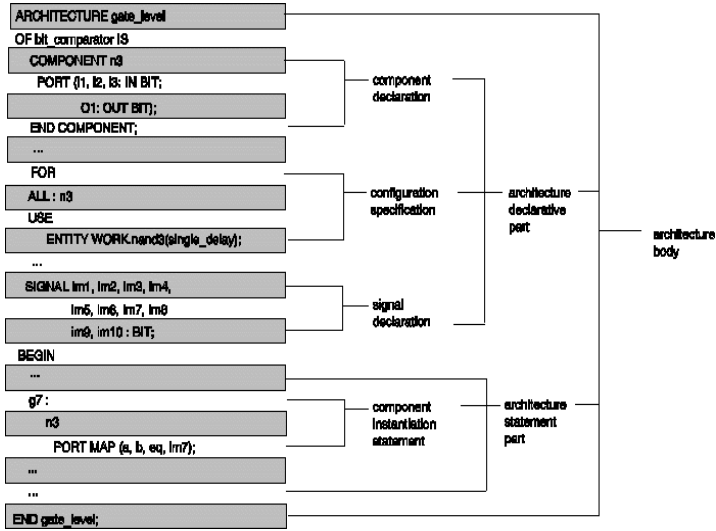

2-11

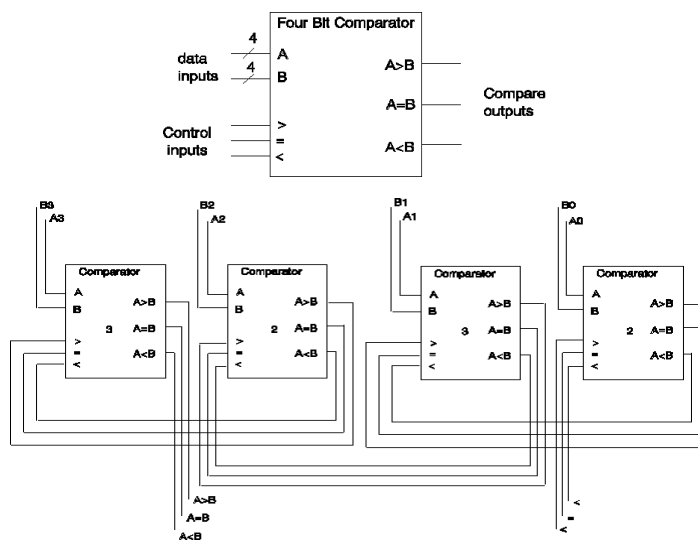
4-Bit Comparator Structural Iterative Wiring



2-12

4-Bit Comparator Aspect Notation

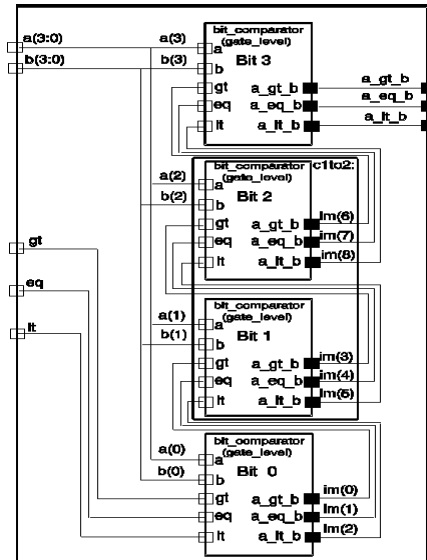- Aspect notation shows VHDL wiring
- VHDL description will use same intermediate signal names



2-13

4-Bit Comparator: “For Generate” Statement ...

```

ENTITY nibble_comparator IS
  PORT (a, b : IN BIT_VECTOR (3 DOWNT0 0); -- a and b data inputs
        gt, eq, lt : IN BIT; -- previous greater, equal & less than
        a_gt_b, a_eq_b, a_lt_b : OUT BIT); -- a > b, a = b, a < b
END nibble_comparator;
--
ARCHITECTURE iterative OF nibble_comparator IS

  COMPONENT comp1
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
  END COMPONENT;
  FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
  SIGNAL im : BIT_VECTOR ( 0 TO 8);
BEGIN

  c0: comp1 PORT MAP (a(0), b(0), gt, eq, lt, im(0), im(1), im(2));

```

2-14

... 4-Bit Comparator: “For Generate” Statement

c1to2: FOR i IN 1 TO 2 GENERATE

c: comp1 PORT MAP (a(i), b(i), im(i*3-3), im(i*3-2), im(i*3-1),
im(i*3+0), im(i*3+1), im(i*3+2));

END GENERATE;


c3: comp1 PORT MAP (a(3), b(3), im(6), im(7), im(8), a_gt_b,
a_eq_b, a_lt_b);

END iterative;

- USE BIT_VECTOR for Ports a & b
- Separate first and last bit-slices from others
- Arrays FOR intermediate signals facilitate iterative wiring
- Can easily expand to an n-bit comparator

2-15

Syntax of Generate Statement

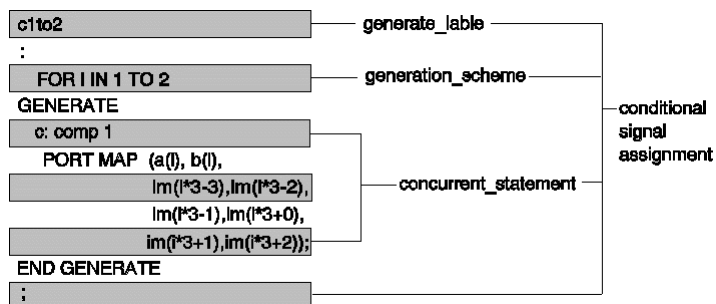

- Generate statement is a concurrent statement
- Generate statement brackets concurrent statements

2-16

4-Bit Comparator: “IF Generate” Statement ...

```
ARCHITECTURE iterative OF nibble_comparator IS
--
  COMPONENT comp1
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
  END COMPONENT;
--
  FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
  CONSTANT n : INTEGER := 4;
  SIGNAL im : BIT_VECTOR ( 0 TO (n-1)*3-1);
--
BEGIN
  c_all: FOR i IN 0 TO n-1 GENERATE

  /: IF i = 0 GENERATE
    least: comp1 PORT MAP (a(i), b(i), gt, eq, lt, im(0), im(1), im(2) );
  END GENERATE;
```

2-17

... 4-Bit Comparator: “IF Generate” Statement

```
--
  m: IF i = n-1 GENERATE
    most: comp1 PORT MAP (a(i), b(i), im(i*3-3), im(i*3-2),
                          im(i*3-1), a_gt_b, a_eq_b, a_lt_b);
  END GENERATE;
--
  r: IF i > 0 AND i < n-1 GENERATE
    rest: comp1 PORT MAP (a(i), b(i), im(i*3-3), im(i*3-2),
                          im(i*3-1), im(i*3+0), im(i*3+1), im(i*3+2) );
  END GENERATE;
--
END GENERATE; -- Outer Generate
END iterative;
```

2-18

4-Bit Comparator: Alternative Architecture (Single Generate)

```


ARCHITECTURE Alt_iterative OF nibble_comparator IS
constant n: Positive :=4;
COMPONENT comp1
  PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END COMPONENT;
FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
SIGNAL im : BIT_VECTOR ( 0 TO 3*n+2);
BEGIN
im(0 To 2) <= gt&eq&lt;
cALL: FOR i IN 0 TO n-1 GENERATE
c: comp1 PORT MAP (a(i), b(i), im(i*3), im(i*3+1), im(i*3+2),
im(i*3+3), im(i*3+4), im(i*3+5) );
END GENERATE;
a_gt_b <= im(3*n);
a_eq_b <= im(3*n+1);
a_lt_b <= im(3*n+2);
END Alt_iterative ;

```

2-19

Structural Test Bench

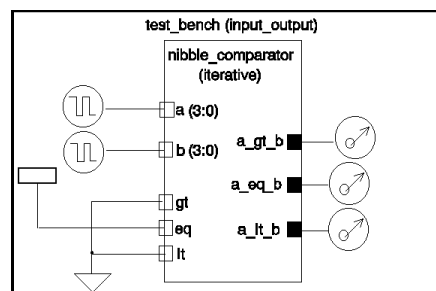- A Testbench is an Entity without Ports that has a Structural Architecture
- The Testbench Architecture, in general, has 3 major components:
 - Instance of the Entity Under Test (EUT)
 - Test Pattern Generator (Generates Test Inputs for the Input Ports of the EUT)
 - Response Evaluator (Compares the EUT Output Signals to the Expected Correct Output)



2-20

Testbench Example ...

```
Entity nibble_comparator_test_bench IS
End nibble_comparator_test_bench ;
--
ARCHITECTURE input_output OF nibble_comparator_test_bench IS
--
COMPONENT comp4 PORT (a, b : IN bit_vector (3 DOWNT0 0);
gt, eq, lt : IN BIT;
a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END COMPONENT;
--
FOR a1 : comp4 USE ENTITY WORK.nibble_comparator(iterative);
--
SIGNAL a, b : BIT_VECTOR (3 DOWNT0 0);
SIGNAL eql, lss, gtr, gnd : BIT;
SIGNAL vdd : BIT := '1';
--
BEGIN
a1: comp4 PORT MAP (a, b, gnd, vdd, gnd, gtr, eql, lss);
--
```

2-21

...Testbench Example

```
a2: a <= "0000",      -- a = b (steady state)
"1111" AFTER 0500 NS, -- a > b (worst case)
"1110" AFTER 1500 NS, -- a < b (worst case)
"1110" AFTER 2500 NS, -- a > b (need bit 1 info)
"1010" AFTER 3500 NS, -- a < b (need bit 2 info)
"0000" AFTER 4000 NS, -- a < b (steady state, prepare FOR next)
"1111" AFTER 4500 NS, -- a = b (worst case)
"0000" AFTER 5000 NS, -- a < b (need bit 3 only, best case)
"0000" AFTER 5500 NS, -- a = b (worst case)
"1111" AFTER 6000 NS; -- a > b (need bit 3 only, best case)
--
a3: b <= "0000",      -- a = b (steady state)
"1110" AFTER 0500 NS, -- a > b (worst case)
"1111" AFTER 1500 NS, -- a < b (worst case)
"1100" AFTER 2500 NS, -- a > b (need bit 1 info)
"1100" AFTER 3500 NS, -- a < b (need bit 2 info)
"1101" AFTER 4000 NS, -- a < b (steady state, prepare FOR next)
"1111" AFTER 4500 NS, -- a = b (worst case)
"1110" AFTER 5000 NS, -- a < b (need bit 3 only, best case)
"0000" AFTER 5500 NS, -- a = b (worst case)
"1110" AFTER 6000 NS; -- a > b (need bit 3 only, best case)
END input_output;
```


2-22

Different Binding Schemes

```
Entity sr_latch IS
  Port (S, R, C : IN Bit; q : Out Bit);
END sr_latch;
```

**USE 4 2-Input NAND gates
to design an SR latch**
 
```
ARCHITECTURE Wrong OF sr_latch IS
  COMPONENT n2
    PORT (i1, i2: IN BIT; o1: OUT BIT);
  END COMPONENT;
```



```
FOR ALL : n2 USE ENTITY WORK.nand2 (single_delay);
```

```
SIGNAL im1, im2, im4 : BIT;
```

```
BEGIN
```

```
g1 : n2 PORT MAP (s, c, im1);
```

```
g2 : n2 PORT MAP (r, c, im2);
```

```
g3 : n2 PORT MAP (im1, im4, q);
```

```
g4 : n2 PORT MAP (q, im2, im4); -- Error ... q declared as Output
```

```
END Wrong;
```

2-23

SR Latch Modeling ...

Fix #1 (Same Architecture -- Change mode of q to Inout)

```
Entity sr_latch IS
  Port (S, R, C : IN Bit; q : InOut Bit);
END sr_latch;
```

Fix #2 (Same Architecture -- Change mode of q to Buffer)

```
Entity sr_latch IS
  Port (S, R, C : IN Bit; q : Buffer Bit);
END sr_latch;
```

2-24

... SR Latch Modeling ...

Fix #3 (*Use Local Signal—Mode of q is maintained as Out*)

```
ARCHITECTURE Problem OF sr_latch IS
COMPONENT n2
  PORT (i1, i2: IN BIT; o1: OUT BIT);
END COMPONENT;
FOR ALL : n2 USE ENTITY WORK.nand2 (single_delay);
SIGNAL im1, im2, im3, im4 : BIT;
BEGIN
  g1 : n2 PORT MAP (s, c, im1);
  g2 : n2 PORT MAP (r, c, im2);
  g3 : n2 PORT MAP (im1, im4, im3);
  g4 : n2 PORT MAP (im3, im2, im4);
  q <= im3;
END Problem;
```

- Correct Syntax → Problem Oscillating
- If all delays are equal then (0,0) on (q, qbar) will oscillate
- Remedy by using gates of different delay values

2-25

... SR Latch Modeling

```
ARCHITECTURE fast_single_delay OF nand2 IS
BEGIN
  o1 <= i1 NAND i2 AFTER 1 NS;
END fast_single_delay;
```


```
ARCHITECTURE gate_Level OF sr_latch IS
COMPONENT n2
  PORT (i1, i2: IN BIT; o1: OUT BIT);
END COMPONENT;
FOR g1, g3 : n2 USE ENTITY WORK.nand2 (fast_single_delay);
FOR g2, g4 : n2 USE ENTITY WORK.nand2 (single_delay);
SIGNAL im1, im2, im3, im4 : BIT;
BEGIN
  g1 : n2 PORT MAP (s, c, im1);
  g2 : n2 PORT MAP (r, c, im2);
  g3 : n2 PORT MAP (im1, im4, im3);
  g4 : n2 PORT MAP (im3, im2, im4);
  q <= im3;
END gate_Level;
```

2-26

Binding 3-Input NAND Entity (*Different Delay*) to 2-Input “NAND” Component


```

ARCHITECTURE gate_level OF sr_latch IS
  COMPONENT n2
    PORT (x, y: in BIT; z: out BIT);
  END COMPONENT;
  FOR g1, g3 : n2 USE ENTITY WORK.nand2
    (single_delay) PORT MAP (x, y, z);
  FOR g2, g4 : n2 USE ENTITY WORK.nand3
    (single_delay) PORT MAP (x, x, y, z);
  SIGNAL im1, im2, im3, im4 : BIT;
  BEGIN
    g1 : n2 PORT MAP (s, c, im1);
    g2 : n2 PORT MAP (r, c, im2);
    g3 : n2 PORT MAP (im1, im4, im3);
    g4 : n2 PORT MAP (im3, im2, im4);
    q <= im3;
  END gate_level;
  
```

 

2-27

Port Map Association ...

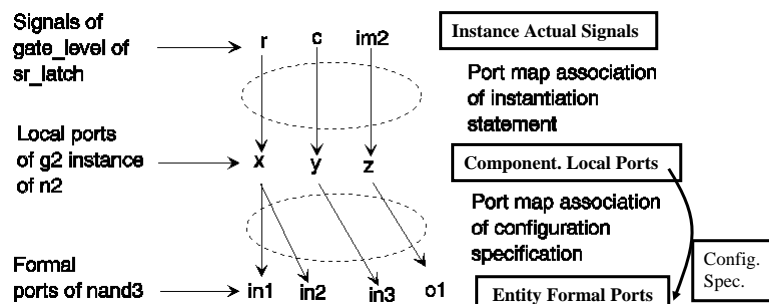

2-28

... Port Map Association

- Association is done in two steps:
 - Instance-To-Component
(*Actuals* → *Component Local Ports*)
 - Component-To-Entity (Configuration Port Map)
(*Component Local Ports* → *Entity Formal Ports*)
 - Specifying PORT MAP in Configuration Statements is Optional
 - PORT MAP of COMPONENT declaration is the default
 - To Override Component Local Port Names, USE PORT MAP in configuration declaration
 - IF No Port Map is Specified in Configuration Statement, Local Port Names of COMPONENT declaration are the Default and they must be the Same as the Formals of the Design Entity.

2-29

Default Binding

- **Default Binding:** Component instance is Bound to an Entity which:
 - Has the same NAME as the Component
 - Has the same number of Ports as the Component
 - *Ports* must have the *Same Name, Type* and be of *Compatible modes*
 - The most Recently analyzed Architecture will Be used
 - A declared **Signal** can be associated with A Formal Port of **Any Mode** as long as it has the **Same Type**
- **Port Compatibility:** Formal => Actual


Actual's Mode (Instance Ports)

	IN	OUT	INOUT	BUFFER
IN	X		X	
OUT		X	X	
INOUT			X	
BUFFER				X

*Formal's Mode
Entity Formal Ports*

2-30


Use of Configuration Specifications

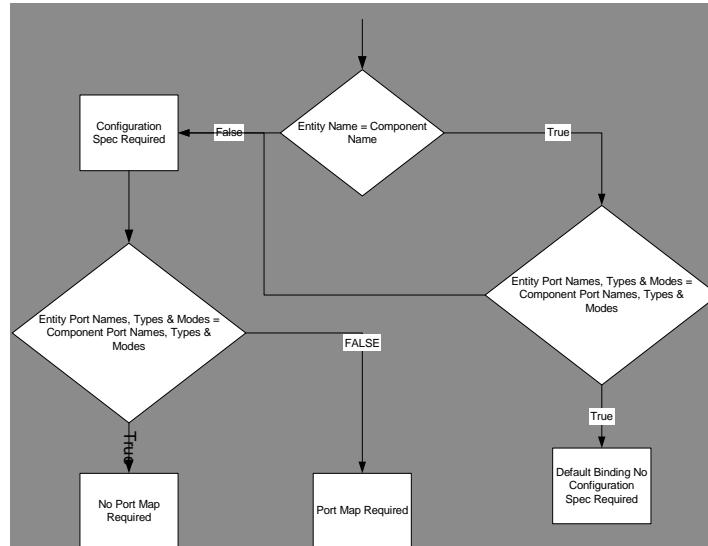

2-31

Sequential Comparator ...

 
- Compare consecutive sets of data on an 8-bit input bus.
- Data on the input bus are synchronized with a clock signal (new value on falling edge of clock)



2-32

D-Latch
 
```
ENTITY d_latch IS
  PORT (d, c : IN BIT; q: OUT BIT);
END d_latch;
--
ARCHITECTURE sr_based OF d_latch IS
  COMPONENT sr_latch
    PORT (s, r, C : IN BIT; q : OUT BIT);
  END COMPONENT;
  COMPONENT inv
    PORT (i1 : IN BIT; o1 : OUT BIT);
  END COMPONENT;
  SIGNAL dbar: BIT;
BEGIN
  c1 : sr_latch PORT MAP (d, dbar, c, q);
  c2 : inv PORT MAP (d, dbar);
END sr_based;
```



2-33

Byte Latch

```
ENTITY byte_latch IS
  PORT ( di : IN BIT_VECTOR (7 DOWNTO 0); clk : IN BIT; qo : OUT
    BIT_VECTOR( 7 DOWNTO 0));
END byte_latch;
--
ARCHITECTURE iterative OF byte_latch IS
  COMPONENT d_latch
  PORT (d, c : IN BIT; q : OUT BIT);
  END COMPONENT;
BEGIN
  g : FOR i IN di'RANGE GENERATE
    L7DT0 : d_latch PORT MAP (di(i), clk, qo(i));
  END GENERATE;
END iterative;
```


2-34

... Sequential Comparator ...

```

ENTITY old_new_comparator IS
PORT (i : IN BIT_VECTOR (7 DOWNTO 0);
      clk : IN BIT; compare : OUT BIT);
END old_new_comparator;
--
ARCHITECTURE wiring Of old_new_comparator IS
COMPONENT byte_latch PORT (di : IN
  BIT_VECTOR (7 DOWNTO 0); clk : IN BIT;
  qo : OUT BIT_VECTOR (7 DOWNTO 0));
END COMPONENT;
COMPONENT byte_comparator
  PORT (a, b : BIT_VECTOR (7 DOWNTO 0);
        gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END COMPONENT;
SIGNAL con1 : BIT_VECTOR (7 DOWNTO 0);
SIGNAL vdd : BIT := '1';
SIGNAL gnd : BIT := '0';

```

 

2-35

... Sequential Comparator

```

BEGIN
I : byte_latch PORT MAP (i, clk, con1);
c : byte_comparator
  PORT MAP (con1, i, gnd, vdd, gnd, OPEN, compare, OPEN);
END wiring;

```

- Unconnected Outputs → OPEN
- Unconnected Inputs (Only with Default Specified) → OPEN

2-36