
COE 561

Digital System Design & Synthesis

Introduction to VHDL

Dr. Aiman H. El-Maleh
Computer Engineering Department
King Fahd University of Petroleum & Minerals

Outline ...

- **Hardware description languages**
- **VHDL terms**
- **Design Entity**
- **Design Architecture**
- **VHDL model of full adder circuit**
- **VHDL model of 1's count circuit**
- **Other VHDL model examples**
- **Structural modeling of 4-bit comparator**
- **Design parameterization using Generic**

... Outline

- Test Bench example
- VHDL objects
- Variables vs. Signals
- Signal assignment & Signal attributes
- Subprograms, Packages, and Libraries
- Data types in VHDL
- Data flow modeling in VHDL
- Behavioral modeling in VHDL

3

Hardware Description Languages

- HDLs are used to describe the hardware for the purpose of modeling, simulation, testing, design, and documentation.
 - Modeling: behavior, flow of data, structure
 - Simulation: verification and test
 - Design: synthesis
- Two widely-used HDLs today
 - **VHDL**: VHSIC (Very High Speed Integrated Circuit) Hardware Description Language
 - **Verilog** (from Cadence, now IEEE standard)

4

Styles in VHDL

- **Behavioral**
 - High level, algorithmic, sequential execution
 - Hard to synthesize well
 - Easy to write and understand (like high-level language code)
- **Dataflow**
 - Medium level, register-to-register transfers, concurrent execution
 - Easy to synthesize well
 - Harder to write and understand (like assembly code)
- **Structural**
 - Low level, netlist, component instantiations and wiring
 - Trivial to synthesize
 - Hardest to write and understand (very detailed and low level)

5

VHDL Terms ...

- **Entity:**
 - All designs are expressed in terms of entities
 - Basic building block in a design
- **Ports:**
 - Provide the mechanism for a device to communication with its environment
 - Define the names, types, directions, and possible default values for the signals in a component's interface
- **Architecture:**
 - All entities have an architectural description
 - Describes the behavior of the entity
 - A single entity can have multiple architectures (behavioral, structural, ...etc)
- **Configuration:**
 - A configuration statement is used to bind a component instance to an entity-architecture pair.
 - Describes which behavior to use for each entity

6

... VHDL Terms ...

■ **Generic:**

- A parameter that passes information to an entity
- Example: for a gate-level model with rise and fall delay, values for the rise and fall delays passed as generics

■ **Process:**

- Basic unit of execution in VHDL
- All operations in a VHDL description are broken into single or multiple processes
- Statements inside a process are processed sequentially

■ **Package:**

- A collection of common declarations, constants, and/or subprograms to entities and architectures.

7

VHDL Terms ...

■ **Attribute:**

- Data attached to VHDL objects or predefined data about VHDL objects
- Examples:
 - maximum operation temperature of a device
 - Current drive capability of a buffer

■ **VHDL is NOT Case-Sensitive**


- Begin = begin = beGiN

■ **Semicolon “ ; ” terminates declarations or statements.**

- **After a double minus sign (--) the rest of the line is treated as a comment**


8

VHDL Models ...

 

9

... VHDL Models

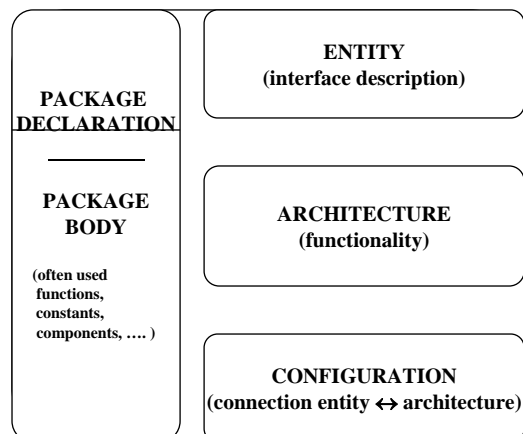


10

Design Entity ...



- In VHDL, the name of the system is the same as the name of its entity.
- Entity comprises two parts:
 - *parameters* of the system as seen from outside such as bus-width of a processor or max clock frequency
 - *connections* which are transferring information to and from the system (system's inputs and outputs)
- All parameters are declared as generics and are passed on to the body of the system
- Connections, which carry data to and from the system, are called *ports*. They form the second part of the entity.

11

Illustration of an Entity

 

entity Eight_bit_register is

  


end [entity] [Eight_bit_register]

12

Entity Examples ...

 - Entity FULLADDER is
 - Interface description of FULLADDER
- ```
port (A, B, C: in bit;
 SUM, CARRY: out bit);
end FULLADDER;
```




13
 
## ... Entity Examples


---

- Entity Register is
    - parameter: width of the register
    - generic (width: integer);
    - input and output signals
- ```
port ( CLK, Reset: in bit;  
      D: in bit_vector(1 to width);  
      Q: out bit_vector(1 to width));  
end Register;
```



14

... Design Entity

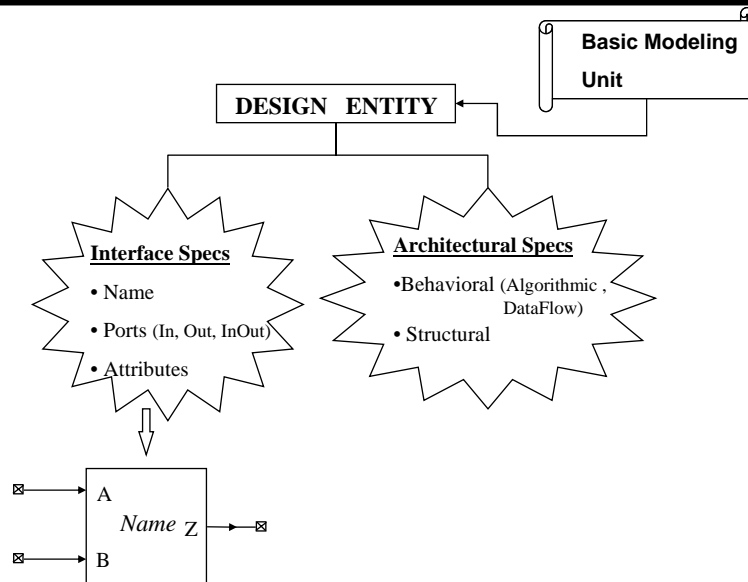

15

Architecture Examples: Behavioral Description

- Entity FULLADDER is

```
port (
    A, B, C: in bit;
    SUM, CARRY: out bit);
end FULLADDER;
```
- Architecture CONCURRENT of FULLADDER is

```
begin
    SUM <= A xor B xor C after 5 ns;
    CARRY <= (A and B) or (B and C) or (A and C) after 3
    ns;
end CONCURRENT;
```


16

Architecture Examples: Structural Description ...

```

■ architecture STRUCTURAL of FULLADDER is
  signal S1, C1, C2 : bit;
  component HA
    port (I1, I2 : in bit; S, C : out bit);
  end component;
  component OR
    port (I1, I2 : in bit; X : out bit);
  end component;
begin
  INST_HA1 : HA port map (I1 => B, I2 => C, S => S1, C => C1);
  INST_HA2 : HA port map (I1 => A, I2 => S1, S => SUM, C => C2);
  INST_OR : OR port map (I1 => C2, I2 => C1, X => CARRY);
end STRUCTURAL;

```

 

17

... Architecture Examples: Structural Description

```

Entity HA is
PORT (I1, I2 : in bit; S, C : out bit);
end HA ;
Architecture behavior of HA is
begin
  S <= I1 xor I2;
  C <= I1 and I2;
end behavior;

```

```


Entity OR is
PORT (I1, I2 : in bit; X : out bit);
end OR ;
Architecture behavior of OR is
begin
  X <= I1 or I2;
end behavior;

```

18

One Entity Many Descriptions

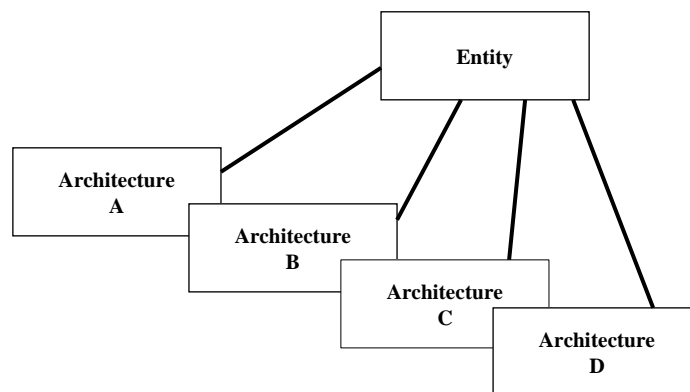- A system (an *entity*) can be specified with different *architectures*




19

 Example: Ones Count Circuit

- Value of $C1$ $C0$ = No. of ones in the inputs $A2$, $A1$, and $A0$

- $C1$ is the Majority Function ($=1$ iff two or more inputs $=1$)
- $C0$ is a 3-Bit Odd-Parity Function (OPAR3))
- $C1 = A1 A0 + A2 A0 + A2 A1$
- $C0 = A2 A1' A0' + A2' A1 A0' + A2' A1' A0 + A2 A1 A0$



20

Ones Count Circuit Interface Specification

1 → entity *ONES_CNT* is

2 → port (A : in BIT_VECTOR(2 downto 0);
C : out BIT_VECTOR(1 downto 0));

DOCUMENTATION

-- *Function Documentation of ONES_CNT*
-- (Truth Table Form)

A2	A1	A0	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3 → end *ONES_CNT*;

21

Ones Count Circuit Architectural Body: Behavioral (Truth Table)

Architecture *Truth_Table* of *ONES_CNT* is

```
begin
  Process(A) -- Sensitivity List Contains only Vector A
  begin
    CASE A is
      WHEN "000" => C <= "00";
      WHEN "001" => C <= "01";
      WHEN "010" => C <= "01";
      WHEN "011" => C <= "10";
      WHEN "100" => C <= "01";
      WHEN "101" => C <= "10";
      WHEN "110" => C <= "10";
      WHEN "111" => C <= "11";
    end CASE;
  end process;
end Truth_Table;
```

22

Ones Count Circuit Architectural Body: Behavioral (Algorithmic)

```
Architecture Algorithmic of ONES_CNT is
begin
    Process(A) -- Sensitivity List Contains only Vector A
        Variable num: INTEGER range 0 to 3;
    begin
        num :=0;
        For i in 0 to 2 Loop
            IF A(i) = '1' then
                num := num+1;
            end if;
        end Loop;
        --
        -- Transfer "num" Variable Value to a SIGNAL
        --
        CASE num is
            WHEN 0 => C <= "00";
            WHEN 1 => C <= "01";
            WHEN 2 => C <= "10";
            WHEN 3 => C <= "11";
        end CASE;
    end process;
end Algorithmic;
```

23

Ones Count Circuit Architectural Body: Data Flow

- $C1 = A1 A0 + A2 A0 + A2 A1$
- $C0 = A2 A1' A0' + A2' A1 A0' + A2' A1' A0 + A2 A1 A0$

```
Architecture Dataflow of ONES_CNT is
begin
```

```
    C(1) <=(A(1) and A(0)) or (A(2) and A(0))
           or (A(2) and A(1));
```

```
    C(0) <= (A(2) and not A(1) and not A(0))
           or (not A(2) and A(1) and not A(0))
           or (not A(2) and not A(1) and A(0))
           or (A(2) and A(1) and A(0));
```


```
end Dataflow;
```

24

Ones Count Circuit Architectural Body: Structural ...

- $C1 = A1 A0 + A2 A0 + A2 A1 = \text{MAJ3}(A)$
- $C0 = A2 A1' A0' + A2' A1 A0' + A2' A1' A0 + A2 A1 A0 = \text{OPAR3}(A)$

Structural Design Hierarchy

 


25

Ones Count Circuit Architectural Body: Structural ...

- Entity MAJ3 is
PORT(X: in BIT_Vector(2 downto 0);
Z: out BIT);
end MAJ3;
- Entity OPAR3 is
PORT(X: in BIT_Vector(2 downto 0);
Z: out BIT);
end OPAR3;

26

 VHDL Structural Description of Majority Function ...



Architecture Structural of MAJ3 is

Component AND2

PORT(I1, I2: in BIT; O: out BIT);

end Component ;

Component OR3

PORT(I1, I2, I3: in BIT; O: out BIT);

end Component ;

Declare Components
To be Instantiated

27

VHDL Structural Description of Majority Function

SIGNAL A1, A2, A3: BIT; *Declare Maj3 Local Signals*

begin

-- Instantiate Gates

g1: AND2 PORT MAP (X(0), X(1), A1);

g2: AND2 PORT MAP (X(0), X(2), A2);

g3: AND2 PORT MAP (X(1), X(2), A3);

g4: OR3 PORT MAP (A1, A2, A3, Z);

end Structural;

*Wiring of
Maj3
Components*

28

VHDL Structural Description of Odd Parity Function ...

Architecture Structural of *OPAR3* is

Component INV

PORT(Ipt: in BIT; Opt: out BIT);

end Component ;

Component NAND3

PORT(I1, I2, I3: in BIT;

O: out BIT);


end Component ;

Component NAND4

PORT(I1, I2, I3, I4: in BIT;

O: out BIT);

end Component ;

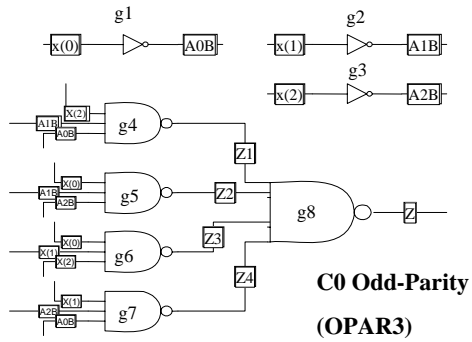

29

VHDL Structural Description of Odd Parity Function

SIGNAL A0B, A1B, A2B, Z1, Z2, Z3, Z4: BIT;

begin

g1: INV PORT MAP (X(0), A0B);

g2: INV PORT MAP (X(1), A1B);

g3: INV PORT MAP (X(2), A2B);

g4: NAND3 PORT MAP (X(2), A1B, A0B, Z1);

g5: NAND3 PORT MAP (X(0), A1B, A2B, Z2);

g6: NAND3 PORT MAP (X(0), X(1), X(2), Z3);

g7: NAND3 PORT MAP (X(1), A2B, A0B, Z4);

g8: NAND4 PORT MAP (Z1, Z2, Z3, Z4, Z);

end Structural;

30

VHDL Top Structural Level of Ones Count Circuit

```
Architecture Structural of ONES_CNT is
Component MAJ3
  PORT( X: in BIT_Vector(2 downto 0); Z: out BIT);
END Component ;
Component OPAR3
  PORT( X: in BIT_Vector(2 downto 0); Z: out BIT);
END Component ;
begin
-- Instantiate Components
  c1: MAJ3 PORT MAP (A, C(1));
  c2: OPAR3 PORT MAP (A, C(0));
end Structural;
```

31

VHDL Behavioral Definition of Lower Level Components

```
Entity INV is
  PORT( Ipt: in BIT;
        Opt: out BIT);
end INV;
Architecture behavior of INV is
begin
  Opt <= not Ipt;
end behavior;
```

```
Entity NAND2 is
  PORT( I1, I2: in BIT;
        O: out BIT);
end NAND2;
Architecture behavior of NAND2 is
begin
  O <= not (I1 and I2);
end behavior;
```

Other Lower Level Gates Are Defined Similarly

32

VHDL Model of 2x1 Multiplexer

Entity mux2_1 IS

Generic (dz_delay: TIME := 6 NS);

PORT (sel, data1, data0: IN BIT; z: OUT BIT);

END mux2_1;


Architecture dataflow OF mux2_1 IS

Begin

z <= data1 AFTER dz_delay WHEN sel='1' ELSE

data0 AFTER dz_delay;

END dataflow;

 

33

VHDL Model of D-FF – Synchronous Reset

Entity DFF IS

Generic (td_reset, td_in: TIME := 8 NS);

PORT (reset, din, clk: IN BIT; qout: OUT BIT := '0');

END DFF;

Architecture behavioral OF DFF IS

Begin

Process(clk)

Begin

IF (clk = '0' AND clk'Event) Then

IF reset = '1' Then

qout <= '0' AFTER td_reset ;

ELSE


qout <= din AFTER td_in ;

END IF;

END IF;

END process;

END behavioral ;

 

34

VHDL Model of D-FF – Asynchronous Reset

Entity DFF IS

Generic (td_reset, td_in: TIME := 8 NS);
 PORT (reset, din, clk: IN BIT; qout: OUT BIT :='0');

END DFF;

Architecture behavioral OF DFF IS

Begin

Process(clk, reset)

Begin

IF reset = '1' Then
 qout <= '0' AFTER td_reset ;

ELSE


IF (clk = '0' AND clk'Event) Then
 qout <= din AFTER td_in ;

END IF;

END IF;

END process;

END behavioral ;

 

35

Divide-by-8 Counter

Entity counter IS

Generic (td_cnt: TIME := 8 NS);
 PORT (reset, clk: IN BIT; counting: OUT BIT :='0');
 Constant limit: INTEGER :=8;

END counter ;

Architecture behavioral OF counter IS

Begin

Process(clk)

Variable count: INTEGER := limit;

Begin

IF (clk = '0' AND clk'Event) THEN

IF reset = '1' THEN count := 0 ;

ELSE IF count < limit THEN count:= count+1; END IF;

END IF;

IF count = limit Then counting <= '0' AFTER td_cnt;

ELSE counting <= '1' AFTER td_cnt;

END IF;

END IF;

END process;



END behavioral ;

36

Controller Description

■ Moore Sequence Detector

- Detection sequence is 110

  

37


VHDL Description of Moore 110 Sequence Detector

```

ENTITY moore_110_detector IS
  PORT (x, clk : IN BIT; z : OUT BIT);
END moore_110_detector;
ARCHITECTURE behavioral OF moore_110_detector IS
  TYPE state IS (reset, got1, got11, got110);
  SIGNAL current : state := reset;
BEGIN
  PROCESS(clk)
  BEGIN
    IF (clk = '1' AND CLK'Event) THEN
      CASE current IS
        WHEN reset =>
          IF x = '1' THEN current <= got1;
          ELSE current <= reset; END IF;
        WHEN got1 =>
          IF x = '1' THEN current <= got11;
          ELSE current <= reset; END IF;
        WHEN got11 =>
          IF x = '1' THEN current <= got11;
          ELSE current <= got110; END IF;
        WHEN got110 =>
          IF x = '1' THEN current <= got1;
          ELSE current <= reset; END IF;
      END CASE;
    END IF;
  END PROCESS;
  z <= '1' WHEN current = got110 ELSE '0';
END behavioral;
  
```

38


Structural 4-Bit Comparator

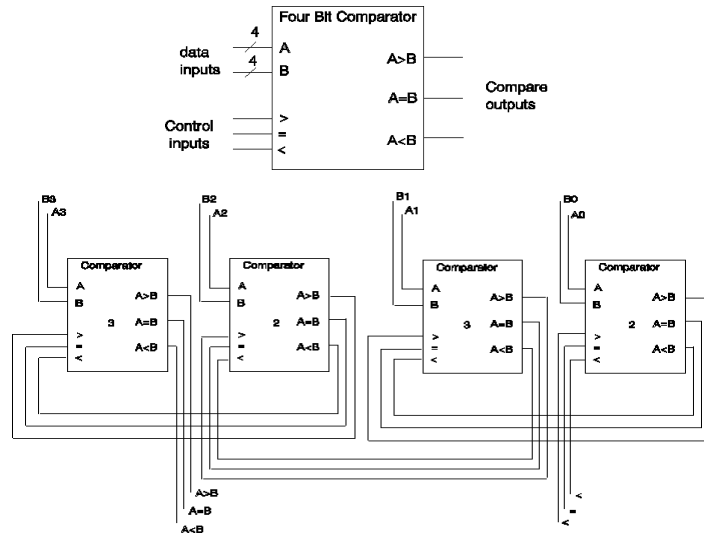

39

A Cascadable Single-Bit Comparator

 - When $a > b$ the a_gt_b becomes 1
- When $a < b$ the a_lt_b becomes 1
- If $a = b$ outputs become the same as corresponding inputs



		a,b			
		00	01	11	10
>	0				1
	1	1		1	1

a>b

		a,b			
		00	01	11	10
=	0				
	1	1		1	

a=b


		a,b			
		00	01	11	10
<	0		1		
	1	1	1	1	

a<b

40

Structural Single-Bit Comparator

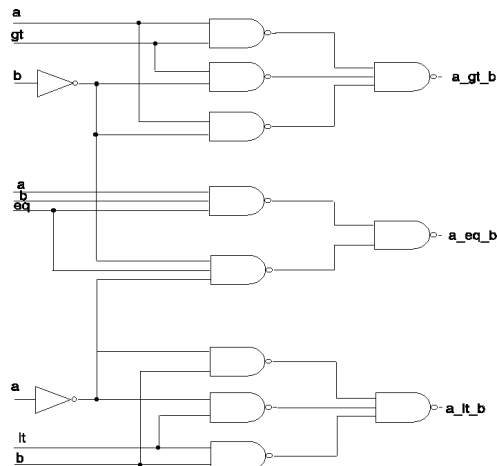- Design uses basic components
- The less-than and greater-than outputs use the same logic



41

Structural Model of Single-Bit Comparator ...

```

ENTITY bit_comparator IS
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END bit_comparator;
ARCHITECTURE gate_level OF bit_comparator IS
--
    COMPONENT n1 PORT (i1: IN BIT; o1: OUT BIT); END COMPONENT ;
    COMPONENT n2 PORT (i1,i2: IN BIT; o1:OUT BIT); END COMPONENT;
    COMPONENT n3 PORT (i1, i2, i3: IN BIT; o1: OUT BIT); END COMPONENT;
-- Component Configuration
    FOR ALL : n1 USE ENTITY WORK.inv (single_delay);
    FOR ALL : n2 USE ENTITY WORK.nand2 (single_delay);
    FOR ALL : n3 USE ENTITY WORK.nand3 (single_delay);
--Intermediate signals
    SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;

```

42

... Structural Model of Single-Bit Comparator

```
BEGIN
-- a_gt_b output
  g0 : n1 PORT MAP (a, im1);
  g1 : n1 PORT MAP (b, im2);
  g2 : n2 PORT MAP (a, im2, im3);
  g3 : n2 PORT MAP (a, gt, im4);
  g4 : n2 PORT MAP (im2, gt, im5);
  g5 : n3 PORT MAP (im3, im4, im5, a_gt_b);
-- a_eq_b output
  g6 : n3 PORT MAP (im1, im2, eq, im6);
  g7 : n3 PORT MAP (a, b, eq, im7);
  g8 : n2 PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
  g9 : n2 PORT MAP (im1, b, im8);
  g10 : n2 PORT MAP (im1, lt, im9);
  g11 : n2 PORT MAP (b, lt, im10);
  g12 : n3 PORT MAP (im8, im9, im10, a_lt_b);
END gate_level;
```

43

Netlist Description of Single-Bit Comparator

```
ARCHITECTURE netlist OF bit_comparator IS
SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;
BEGIN
-- a_gt_b output
  g0 : ENTITY Work.inv(single_delay) PORT MAP (a, im1);
  g1 : ENTITY Work.inv(single_delay) PORT MAP (b, im2);
  g2 : ENTITY Work.nand2(single_delay) PORT MAP (a, im2, im3);
  g3 : ENTITY Work.nand2(single_delay) PORT MAP (a, gt, im4);
  g4 : ENTITY Work.nand2(single_delay) PORT MAP (im2, gt, im5);
  g5 : ENTITY Work.nand3(single_delay) PORT MAP (im3, im4, im5, a_gt_b);
-- a_eq_b output
  g6 : ENTITY Work.nand3(single_delay) PORT MAP (im1, im2, eq, im6);
  g7 : ENTITY Work.nand3(single_delay) PORT MAP (a, b, eq, im7);
  g8 : ENTITY Work.nand2(single_delay) PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
  g9 : ENTITY Work.nand2(single_delay) PORT MAP (im1, b, im8);
  g10 : ENTITY Work.nand2(single_delay) PORT MAP (im1, lt, im9);
  g11 : ENTITY Work.nand2(single_delay) PORT MAP (b, lt, im10);
  g12 : ENTITY Work.nand3(single_delay) PORT MAP (im8, im9, im10, a_lt_b);
END netlist;
```

44

4-Bit Comparator Iterative Structural Wiring: “For Generate” Statement...

```
ENTITY nibble_comparator IS
  PORT (a, b : IN BIT_VECTOR (3 DOWNT0 0); -- a and b data inputs
        gt, eq, lt : IN BIT; -- previous greater, equal & less than
        a_gt_b, a_eq_b, a_lt_b : OUT BIT); -- a > b, a = b, a < b
END nibble_comparator;
--
ARCHITECTURE iterative OF nibble_comparator IS

  COMPONENT comp1
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
  END COMPONENT;
  FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
  SIGNAL im : BIT_VECTOR ( 0 TO 8);
BEGIN

  c0: comp1 PORT MAP (a(0), b(0), gt, eq, lt, im(0), im(1), im(2));
```

45

... 4-Bit Comparator: “For Generate” Statement

```
c1to2: FOR i IN 1 TO 2 GENERATE

  c: comp1 PORT MAP ( a(i), b(i), im(i*3-3), im(i*3-2), im(i*3-1),
                    im(i*3+0), im(i*3+1), im(i*3+2) );

END GENERATE;
c3: comp1 PORT MAP (a(3), b(3), im(6), im(7), im(8), a_gt_b,
                  a_eq_b, a_lt_b);

END iterative;
```

- USE BIT_VECTOR for Ports a & b
- Separate first and last bit-slices from others
- Arrays FOR intermediate signals facilitate iterative wiring
- Can easily expand to an n-bit comparator

46

4-Bit Comparator: “IF Generate” Statement ...

```
ARCHITECTURE iterative OF nibble_comparator IS
--
  COMPONENT comp1
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
  END COMPONENT;
--
  FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
  CONSTANT n : INTEGER := 4;
  SIGNAL im : BIT_VECTOR ( 0 TO (n-1)*3-1);
--
BEGIN
  c_all: FOR i IN 0 TO n-1 GENERATE

  /: IF i = 0 GENERATE
    least: comp1 PORT MAP (a(i), b(i), gt, eq, lt, im(0), im(1), im(2) );
  END GENERATE;
```

47

... 4-Bit Comparator: “IF Generate” Statement

```
--
  m: IF i = n-1 GENERATE
    most: comp1 PORT MAP (a(i), b(i), im(i*3-3), im(i*3-2),
                        im(i*3-1), a_gt_b, a_eq_b, a_lt_b);
  END GENERATE;
--
  r: IF i > 0 AND i < n-1 GENERATE
    rest: comp1 PORT MAP (a(i), b(i), im(i*3-3), im(i*3-2),
                        im(i*3-1), im(i*3+0), im(i*3+1), im(i*3+2) );
  END GENERATE;
--
END GENERATE; -- Outer Generate
END iterative;
```

48

4-Bit Comparator: Alternative Architecture (Single Generate)

```
ARCHITECTURE Alt_iterative OF nibble_comparator IS
constant n: Positive :=4;
COMPONENT comp1
  PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END COMPONENT;
FOR ALL : comp1 USE ENTITY WORK.bit_comparator (gate_level);
SIGNAL im : BIT_VECTOR ( 0 TO 3*n+2);
BEGIN
im(0 To 2) <= gt&eq&lt;
cALL: FOR i IN 0 TO n-1 GENERATE
c: comp1 PORT MAP (a(i), b(i), im(i*3), im(i*3+1), im(i*3+2),
im(i*3+3), im(i*3+4), im(i*3+5) );
END GENERATE;
a_gt_b <= im(3*n);
a_eq_b <= im(3*n+1);
a_lt_b <= im(3*n+2);
END Alt_iterative ;
```

49

Design Parameterization ...

- GENERICS can pass design parameters
- GENERICS can include default values
- New versions of gate descriptions contain timing

```
ENTITY inv_t IS
GENERIC (tph : TIME := 3 NS; tplh : TIME := 5 NS);
PORT (i1 : in BIT; o1 : out BIT);
END inv_t;
--
ARCHITECTURE average_delay OF inv_t IS
BEGIN
o1 <= NOT i1 AFTER (tplh + tph) / 2;
END average_delay;
```

50

... Design Parameterization ...

```

ENTITY nand2_t IS
GENERIC (tph : TIME := 4 NS;
tphl : TIME := 6 NS);
PORT (i1, i2 : IN BIT; o1 : OUT
BIT);
END nand2_t;
--
ARCHITECTURE average_delay
OF nand2_t IS
BEGIN
o1 <= i1 NAND i2 AFTER (tph +
tphl) / 2;
END average_delay;

```

```

ENTITY nand3_t IS
GENERIC (tph : TIME := 5 NS;
tphl : TIME := 7 NS);
PORT (i1, i2, i3 : IN BIT; o1 :
OUT BIT);
END nand3_t;
--
ARCHITECTURE average_delay
OF nand3_t IS
BEGIN
o1 <= NOT ( i1 AND i2 AND i3 )
AFTER (tph + tphl) / 2;
END average_delay;

```

51

Using Default values ...

```

ARCHITECTURE default_delay OF bit_comparator IS
Component n1 PORT (i1: IN BIT; o1: OUT BIT);
END Component;
Component n2 PORT (i1, i2: IN BIT; o1: OUT BIT);
END Component;
Component n3 PORT (i1, i2, i3: IN BIT; o1: OUT BIT);
END Component;
FOR ALL : n1 USE ENTITY WORK.inv_t (average_delay);
FOR ALL : n2 USE ENTITY WORK.nand2_t (average_delay);
FOR ALL : n3 USE ENTITY WORK.nand3_t (average_delay);
-- Intermediate signals
SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;
BEGIN
-- a_gt_b output
g0 : n1 PORT MAP (a, im1);
g1 : n1 PORT MAP (b, im2);
g2 : n2 PORT MAP (a, im2, im3);
g3 : n2 PORT MAP (a, gt, im4);
g4 : n2 PORT MAP (im2, gt, im5);
g5 : n3 PORT MAP (im3, im4, im5, a_gt_b);

```

*No Generics Specified in
Component Declarations*

52

... Using Default values

```
-- a_eq_b output
g6 : n3 PORT MAP (im1, im2, eq, im6);
g7 : n3 PORT MAP (a, b, eq, im7);
g8 : n2 PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
g9 : n2 PORT MAP (im1, b, im8);
g10 : n2 PORT MAP (im1, lt, im9);
g11 : n2 PORT MAP (b, lt, im10);
g12 : n3 PORT MAP (im8, im9, im10, a_lt_b);
END default_delay;
```

- *Component declarations do not contain **GENERICs***
- *Component instantiation are as before*
- *If default values exist, they are used*

53

Assigning Fixed Values to Generic Parameters ...

```
ARCHITECTURE fixed_delay OF bit_comparator IS
Component n1
Generic (tplh, tphl : Time); Port (i1: in Bit; o1: out Bit);
END Component;
Component n2
Generic (tplh, tphl : Time); Port (i1, i2: in Bit; o1: out Bit);
END Component;
Component n3
Generic (tplh, tphl : Time); Port (i1, i2, i3: in Bit; o1: out Bit);
END Component;
FOR ALL : n1 USE ENTITY WORK.inv_t (average_delay);
FOR ALL : n2 USE ENTITY WORK.nand2_t (average_delay);
FOR ALL : n3 USE ENTITY WORK.nand3_t (average_delay);
-- Intermediate signals
SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;
BEGIN
-- a_gt_b output
g0 : n1 Generic Map (2 NS, 4 NS) Port Map (a, im1);
g1 : n1 Generic Map (2 NS, 4 NS) Port Map (b, im2);
g2 : n2 Generic Map (3 NS, 5 NS) Port Map (a, im2, im3);
```

54

... Assigning Fixed Values to Generic Parameters

```

g3 : n2 Generic Map (3 NS, 5 NS) Port Map P (a, gt, im4);
g4 : n2 Generic Map (3 NS, 5 NS) Port Map (im2, gt, im5);
g5 : n3 Generic Map (4 NS, 6 NS) Port Map (im3, im4, im5, a_gt_b);
-- a_eq_b output
g6 : n3 Generic Map (4 NS, 6 NS) Port Map (im1, im2, eq, im6);
g7 : n3 Generic Map (4 NS, 6 NS) PORT MAP (a, b, eq, im7);
g8 : n2 Generic Map (3 NS, 5 NS) PORT MAP (im6, im7, a_eq_b);
-- a_lt_b output
g9 : n2 Generic Map (3 NS, 5 NS) Port Map (im1, b, im8);
g10 : n2 Generic Map (3 NS, 5 NS) PORT MAP (im1, lt, im9);
g11 : n2 Generic Map (3 NS, 5 NS) PORT MAP (b, lt, im10);
g12 : n3 Generic Map (4 NS, 6 NS) PORT MAP (im8, im9, im10, a_lt_b);
END fixed_delay;

```

- *Component declarations contain **GENERICs***
- *Component instantiation contain **GENERIC Values***
- ***GENERIC Values** overwrite default values*

55

Instances with OPEN Parameter Association

```

ARCHITECTURE iterative OF
nibble_comparator IS
.....
BEGIN
c0: comp1
GENERIC MAP (Open, Open, 8
NS, Open, Open, 10 NS)
PORT MAP (a(0), b(0), gt, eq, lt,
im(0), im(1), im(2));
.....
END iterative;

```

```

ARCHITECTURE iterative OF
nibble_comparator IS
.....
BEGIN
c0: comp1
GENERIC MAP (tplh3 => 8 NS,
tplh3 => 10 NS)
PORT MAP (a(0), b(0), gt, eq, lt,
im(0), im(1), im(2));
.....
END iterative;


```

- *A **GENERIC Map** may specify only some of the parameters*
- *Using **OPEN** causes use of default component values*
- *Alternatively, association by name can be used*
- *Same applies to **PORT MAP***

56

Structural Test Bench

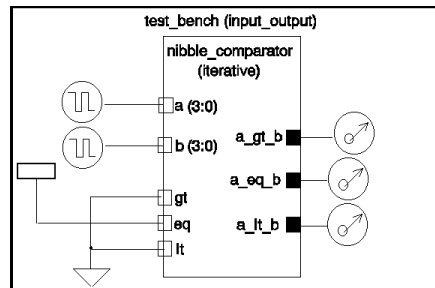- A Testbench is an Entity without Ports that has a Structural Architecture
- The Testbench Architecture, in general, has 3 major components:
 - Instance of the Entity Under Test (EUT)
 - Test Pattern Generator (Generates Test Inputs for the Input Ports of the EUT)
 - Response Evaluator (Compares the EUT Output Signals to the Expected Correct Output)



57

Testbench Example ...

```

Entity nibble_comparator_test_bench IS
End nibble_comparator_test_bench ;
--
ARCHITECTURE input_output OF nibble_comparator_test_bench IS
--
COMPONENT comp4 PORT (a, b : IN bit_vector (3 DOWNTO 0);
gt, eq, lt : IN BIT;
a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END COMPONENT;
--
FOR a1 : comp4 USE ENTITY WORK.nibble_comparator(iterative);
--
SIGNAL a, b : BIT_VECTOR (3 DOWNTO 0);
SIGNAL eq1, lss, gtr, gnd : BIT;
SIGNAL vdd : BIT := '1';
--
BEGIN
a1: comp4 PORT MAP (a, b, gnd, vdd, gnd, gtr, eq1, lss);
--

```

58

...Testbench Example

```
a2: a <= "0000",      -- a = b (steady state)
"1111" AFTER 0500 NS, -- a > b (worst case)
"1110" AFTER 1500 NS, -- a < b (worst case)
"1110" AFTER 2500 NS, -- a > b (need bit 1 info)
"1010" AFTER 3500 NS, -- a < b (need bit 2 info)
"0000" AFTER 4000 NS, -- a < b (steady state, prepare FOR next)
"1111" AFTER 4500 NS, -- a = b (worst case)
"0000" AFTER 5000 NS, -- a < b (need bit 3 only, best case)
"0000" AFTER 5500 NS, -- a = b (worst case)
"1111" AFTER 6000 NS; -- a > b (need bit 3 only, best case)
--
a3: b <= "0000",      -- a = b (steady state)
"1110" AFTER 0500 NS, -- a > b (worst case)
"1111" AFTER 1500 NS, -- a < b (worst case)
"1100" AFTER 2500 NS, -- a > b (need bit 1 info)
"1100" AFTER 3500 NS, -- a < b (need bit 2 info)
"1101" AFTER 4000 NS, -- a < b (steady state, prepare FOR next)
"1111" AFTER 4500 NS, -- a = b (worst case)
"1110" AFTER 5000 NS, -- a < b (need bit 3 only, best case)
"0000" AFTER 5500 NS, -- a = b (worst case)
"0111" AFTER 6000 NS; -- a > b (need bit 3 only, best case)
END input_output;
```

59

VHDL Predefined Operators

- **Logical Operators: NOT, AND, OR, NAND, NOR, XOR, XNOR**
 - Operand Type: Bit, Boolean, Bit_vector
 - Result Type: Bit, Boolean, Bit_vector
- **Relational Operators: =, /=, <, <=, >, >=**
 - Operand Type: Any type
 - Result Type: Boolean
- **Arithmetic Operators: +, -, *, /**
 - Operand Type: Integer, Real
 - Result Type: Integer, Real
- **Concatenation Operator: &**
 - Operand Type: Arrays or elements of same type
 - Result Type: Arrays
- **Shift Operators: SLL, SRL, SLA, SRA, ROL, ROR**
 - Operand Type: Bit or Boolean vector
 - Result Type: same type

60

VHDL Reserved Words

abs	disconnect	label	package	
access	downto	library	Poll	units
after	linkage		procedure	until
alias	else	loop	process	use
all	elsif			variable
and	end	map	range	
architecture	entity	mod	record	wait
array	exit	nand	register	when
assert	new	rem	while	
attribute	file	next	report	with
begin	for	nor	return	xor
block	function	not	select	
body	generate	null	severity	
buffer	generic	of	signal	
bus	guarded	on	subtype	
case	if	open	then	
component	in	or	to	
configuration	inout	others	transport	
constant	is	out	type	

61

VHDL Language Grammar

- Formal grammar of the IEEE Standard 1076-1993 VHDL language in BNF format
 - http://www.iis.ee.ethz.ch/~zimmi/download/vhdl93_syntax.html

62


VHDL Objects ...

- VHDL *OBJECT*: Something that can hold a value of a given *Data Type*.
- VHDL has 3 classes of objects
 - CONSTANTS
 - VARIABLES
 - SIGNALS
- Every object & expression must unambiguously belong to one *named Data Type*
- Every object must be *Declared*.

63

... VHDL Object ...

Syntax

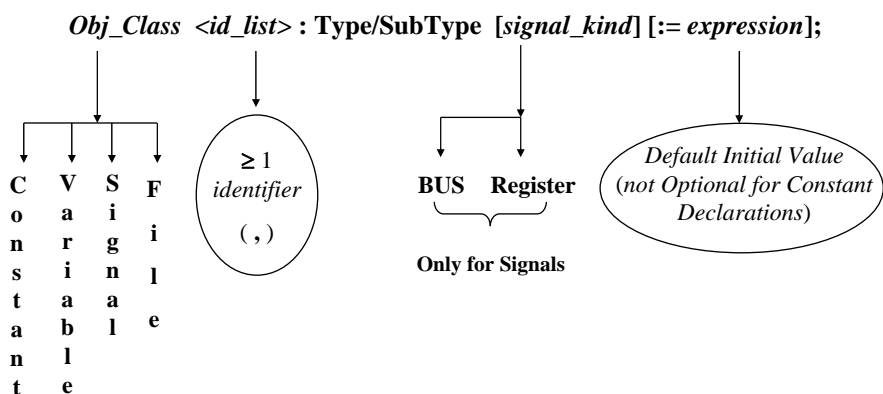

64

... VHDL Object ...

- Value of Constants ***must*** be specified when declared.
- ***Initial*** values of Variables or Signals ***may*** be specified when declared.
- If not explicitly specified, ***Initial*** values of Variables or Signals ***default*** to the value of the Left Element in the type range specified in the declaration.
- **Examples:**
 - **Constant** Rom_Size : Integer := 2**16;
 - **Constant** Address_Field : Integer := 7;
 - **Constant** Ovfl_Msg : String (1 To 20) := ``Accumulator OverFlow``;
 - **Variable** Busy, Active : Boolean := False;
 - **Variable** Address : Bit_Vector (0 To Address_Field) := ``00000000``;
 - **Signal** Reset: Bit := `0`;

65

Variables vs. Signals

Variables & Signals

VARIABLES	SIGNALS
<ul style="list-style-type: none"> • Variables are only <i>Local</i> and May Only Appear within the Body of a Process or a SubProgram • Variable Declarations Are Not Allowed in Declarative Parts of Architecture Bodies or Blocks. 	<ul style="list-style-type: none"> • Signals May be Local or Global. • Signals May not be Declared within Process or Subprogram Bodies. • All Port Declarations Are for Signals.
A Variable Has No Hardware Correspondence	A Signal Represents a Wire or a Group of Wires (BUS)
Variables Have No <i>Time</i> Dimension Associated With Them. (<i>Variable Assignment occurs instantaneously</i>)	Signals Have <i>Time</i> Dimension (<i>A Signal Assignment is Never Instantaneous (Minimum Delay = δ Delay)</i>)
Variable Assignment Statement is always SEQUENTIAL	Signal Assignment Statement is Mostly CONCURRENT (<i>Within Architectural Body</i>). It Can Be SEQUENTIAL (<i>Within Process Body</i>)
Variable Assignment Operator is :=	Signal Assignment Operator is <=

Variables Within Process Bodies are **STATIC**, i.e. a Variable Keeps its Value from One Process Call to Another. Variables Within Subprogram Bodies Are **DYNAMIC**, i.e. Variable Values are Not held from one Call to Another.

66

Signal Assignments ...

■ Syntax:

Target Signal <= [Transport] Waveform ;

Waveform := Waveform_element {, Waveform_element }

Waveform_element := Value_Expression [After Time_Expression]

■ Examples:

- X <= '0' ; -- Assignment executed After δ delay
- S <= '1' After 10 ns;
- Q <= Transport '1' After 10 ns;
- S <= '1' After 5 ns, '0' After 10 ns, '1' After 15 ns;

■ Signal assignment statement

- mostly **concurrent** (within architecture bodies)
- can be **sequential** (within process body)

67

... Signal Assignments

■ Concurrent signal assignments are order independent

■ Sequential signal assignments are order dependent


■ Concurrent signal assignments are executed

- Once *at the beginning* of simulation
- Any time a signal on the right hand side changes

* A Signal Has a 1- Current Value (CV), and
 2- Projected WaveForm (P_Wfm)

* A WaveForm: Consists of a Set of *Signal Transactions*

 * Signal Transaction = Pair (Value, Time)



68

Delta Delay


- If no Time Delay is *explicitly specified*, Signal assignment is executed after a δ -delay

- Delta is a simulation cycle, and not a real time
- Delta is used for scheduling
- A million deltas do not add to a femto second

```

ARCHITECTURE concurrent
OF timing_demo IS
SIGNAL a, b, c : BIT := '0';
BEGIN
a <= '1';
b <= NOT a;
c <= NOT b;
END concurrent;

```

 

Signal Attributes...

- Attributes are named characteristics of an Object (or Type) which has a value that can be referenced.

- Signal Attributes

- S`Event -- Is TRUE if Signal S has changed.
- S`Stable(t) -- Is TRUE if Signal S has not changed for the last ``t`` period. If t=0; it is written as S`Stable
- S`Last_Value -- Returns the previous value of S before the last change.
- S`Active -- -- Is TRUE if Signal S has had a transaction in the current simulation cycle.
- S`Quiet(t) -- -- Is TRUE if no transaction has been placed on Signal S for the last ``t`` period. If t=0; it is written as S`Quiet
- S`Last_Event -- Returns the amount of time since the last value change on S.

70

Subprograms...

- **Subprograms consist of functions and procedures.**
- **Subprograms are used to**
 - Simplify coding,
 - Achieve modularity,
 - Improve readability.
- **Functions return values and cannot alter values of their parameters.**
- **Procedures used as a statement and can alter values of their parameters.**
- **All statements inside a subprogram are sequential.**

71

...Subprograms

- **Subprograms**
 - Concurrent
 - Sequential
- **Concurrent subprograms exist outside of a process or another subprogram.**
- **Sequential subprograms exist in a process statement or another subprogram.**
- **A procedure exists as a separate statement in architecture or process.**
- **A function usually used in assignment statement or expression.**

72

Functions

■ Function specification:

- Name of the function
- Formal parameters of the function
 - Name of the parameter
 - Type of the parameter
 - Mode IN is default & only allowed mode
 - Class constant is default
- Return type of the function
- Local declarations

■ A function body

- Must contain at least one return statement
- May not contain a wait statement

73

A Left-Shift Function

Subtype Byte IS Bit_Vector (7 Downto 0);

Function SLL (V: Byte; N: Natural; Fill: Bit) Return Byte IS

Variable Result: Byte := V;

Begin

For I IN 1 To N Loop

Result := Result (6 Downto 0) & Fill;

End Loop;

Return Result;

End SLL;

74

Using the Function

Architecture Functional Of LeftShifter IS

Subtype Byte IS Bit_Vector (7 Downto 0);

Function SLL (V: Byte; N: Natural; Fill: Bit) Return Byte is

Variable Result: Byte := V;

Begin

For I IN 1 To N Loop

Result := Result (6 Downto 0) & Fill;

End Loop;

Return Result;

End SLL;

Begin

Sout <= SLL(Sin, 1, '0') After 12 ns;

End Functional;

75

A Single-Bit Comparator

Entity Bit_Comparator IS

Port (a, b, -- data inputs
gt, -- previous greater than
eq, -- previous equal
lt: IN BIT; -- previous less than
a_gt_b, -- greater
a_eq_b, -- equal
a_lt_b: OUT BIT); -- less than

End Bit_Comparator;

a_gt_b = a . gt + b` . gt + a . b`

a_eq_b = a . b . eq + a` . b` . eq

a_lt_b = b . lt + a` . lt + b . a`

76

A Single-Bit Comparator using Functions

Architecture Functional of Bit_Comparator IS

Function fgl (w, x, gl: BIT) Return BIT IS

Begin

Return (w AND gl) OR (NOT x AND gl) OR (w AND NOT x);

End fgl;

Function feq (w, x, eq: BIT) Return BIT IS

Begin

Return (w AND x AND eq) OR (NOT w AND NOT x AND eq);

End feq;

Begin

a_gt_b <= fgl (a, b, gt) after 12 ns;

a_eq_b <= feq (a, b, eq) after 12 ns;

a_lt_b <= fgl (b, a, lt) after 12 ns;

End Functional;

77

Binary to Integer Conversion Function

Function To_Integer (Bin : BIT_VECTOR) Return Integer IS

Variable Result: Integer;

Begin

Result := 0;

For I IN Bin`RANGE Loop

If Bin(I) = '1' then

Result := Result + 2**I;

End if;

End Loop;

Return Result;

End To_Integer;

78

Procedure Specification

- **Name of the procedure**
- **Formal parameters of the procedure**
 - Class of the parameter
 - optional
 - defaults to constant
 - Name of the parameter
 - Mode of the parameter
 - optional
 - defaults to IN
 - Type of the parameter
- **Local declarations**

79

A Left-Shift Procedure

```
Subtype Byte is Bit_Vector (7 downto 0);
Procedure SLL (Signal Vin : In Byte; Signal Vout :out
Byte; N: Natural; Fill: Bit;
ShiftTime: Time) IS
    Variable Temp: Byte := Vin;
Begin
    For I IN 1 To N Loop
        Temp := Temp (6 downto 0) & Fill;
    End Loop;
    Vout <= Temp after N * ShiftTime;
End SLL;
```

80

Using the Procedure

Architecture Procedural of LeftShifter is

Subtype Byte is Bit_Vector (7 downto 0);

Procedure SLL (Signal Vin : In Byte; Signal Vout :out Byte; N: Natural;
Fill: Bit; ShiftTime: Time) IS

Variable Temp: Byte := Vin;

Begin

For I IN 1 To N Loop

Temp := Temp (6 downto 0) & Fill;

End Loop;

Vout <= Temp after N * ShiftTime;

End SLL;

Begin

Process (Sin)

Begin

SLL(Sin, Sout, 1, '0', 12 ns) ;

End process;

End Procedural;

81

Binary to Integer Conversion Procedure

Procedure Bin2Int (Bin : IN BIT_VECTOR; Int: OUT Integer) IS

Variable Result: Integer;

Begin

Result := 0;

For I IN Bin`RANGE Loop

If Bin(I) = '1' Then

Result := Result + 2**I;

End If;

End Loop;

Int := Result;

End Bin2Int;

82

Integer to Binary Conversion Procedure

```
Procedure Int2Bin (Int: IN Integer; Bin : OUT BIT_VECTOR) IS
  Variable Tmp: Integer;
Begin
  Tmp := Int;
  For I IN 0 To (Bin`Length - 1) Loop
    If ( Tmp MOD 2 = 1) Then
      Bin(I) := '1';
    Else Bin(I) := '0';
    End If;
    Tmp := Tmp / 2;
  End Loop;
End Int2Bin;
```

83

Packages...

- A package is a common storage area used to hold data to be shared among a number of entities.
- Packages can encapsulate subprograms to be shared.
- A package consists of
 - Declaration section
 - Body section
- The package declaration section contains subprogram declarations, not bodies.
- The package body contains the subprograms' bodies.
- The package declaration defines the interface for the package.

84

...Packages

- All items declared in the package declaration section are visible to any design unit that uses the package.
- A package is used by the USE clause.
- The interface to a package consists of any subprograms or deferred constants declared in the package declaration.
- The subprogram and deferred constant declarations must have a corresponding subprogram body and deferred constant value in the package body.
- Package body May contain other declarations needed solely within the package body.
 - Not visible to external design units.

85

Package Declaration

- The package declaration section can contain:
 - Subprogram declaration
 - Type, subtype declaration
 - Constant, deferred constant declaration
 - Signal declaration creates a global signal
 - File declaration
 - Alias declaration
 - Component declaration
 - Attribute declaration, a user-defined attribute
 - Attribute specification
 - Use clause

86

Package Body

- **The package body main purpose is**
 - Define the values of deferred constants
 - Specify the subprogram bodies for subprograms declared in the package declaration
- **The package body can also contain:**
 - Subprogram declaration
 - Subprogram body
 - Type, subtype declaration
 - Constant declaration, which fills in the value for deferred constants
 - File declaration
 - Alias declaration
 - Use clause

87

Existing Packages

- **Standard Package**
 - Defines primitive types, subtypes, and functions.
 - e.g. Type Boolean IS (false, true);
 - e.g. Type Bit is ('0', '1');
- **TEXTIO Package**
 - Defines types, procedures, and functions for standard text I/O from ASCII files.

88

Package Example for Component Declaration

```
Package simple_gates is
COMPONENT n1 PORT (i1: IN BIT; o1: OUT BIT); END COMPONENT ;
COMPONENT n2 PORT (i1,i2: IN BIT;o1:OUT BIT);END COMPONENT;
COMPONENT n3 PORT (i1, i2, i3: IN BIT; o1: OUT BIT); END COMPONENT;
end simple_gates;

Use work.simple_gates.all;
ENTITY bit_comparator IS
    PORT (a, b, gt, eq, lt : IN BIT; a_gt_b, a_eq_b, a_lt_b : OUT BIT);
END bit_comparator;
ARCHITECTURE gate_level OF bit_comparator IS
FOR ALL : n1 USE ENTITY WORK.inv (single_delay);
FOR ALL : n2 USE ENTITY WORK.nand2 (single_delay);
FOR ALL : n3 USE ENTITY WORK.nand3 (single_delay);
--Intermediate signals
SIGNAL im1,im2, im3, im4, im5, im6, im7, im8, im9, im10 : BIT;
BEGIN
-- description of architecture
END gate_level;
```

89

Package Example...

```
Package Shifters IS
    Subtype Byte IS Bit_Vector (7 Downto 0);
    Function SLL (V: Byte; N: Natural; Fill: Bit := '0') Return Byte;
    Function SRL (V: Byte; N: Natural; Fill: Bit := '0') Return Byte;
    Function SLA (V: Byte; N: Natural; Fill: Bit := '0') Return Byte;
    Function SRA (V: Byte; N: Natural) Return Byte;
    Function RLL (V: Byte; N: Natural) Return Byte;
    Function RRL (V: Byte; N: Natural) Return Byte;
End Shifters;
```

90

...Package Example...

Package Body Shifters IS

Function SLL (V: Byte; N: Natural; Fill: Bit) Return Byte is

Variable Result: Byte := V;

Begin

If N >= 8 Then

Return (Others => Fill);

End If;

For I IN 1 To N Loop

Result := Result (6 Downto 0) & Fill;

End Loop;

Return Result;

End SLL;

.
.
.

End Shifters;

91

...Package Example

USE WORK.Shifters.ALL

Architecture Functional of LeftShifter IS

Begin

Sout <= SLL(Sin, 1, '0') After 12 ns;

End Functional;

92

Another Package Example...

Package Basic_Uilities IS

```
Type Integers IS Array (0 to 5) of Integer;  
Function fgl (w, x, gl: BIT) Return BIT;  
Function feq (w, x, eq: BIT) Return BIT;  
Procedure Bin2Int (Bin : IN BIT_VECTOR; Int: OUT Integer);  
Procedure Int2Bin (Int: IN Integer; Bin : OUT BIT_VECTOR);  
Procedure Apply_Data (  
    Signal Target: OUT Bit_Vector (3 Downto 0);  
    Constant Values: IN Integers;  
    Constant Period: IN Time);  
Function To_Integer (Bin : BIT_VECTOR) Return Integer;  
  
End Basic_Uilities;
```

93

...Another Package Example...

Package Body Basic_Uilities IS

```
Function fgl (w, x, gl: BIT) Return BIT IS  
    Begin  
        Return (w AND gl) OR (NOT x AND gl) OR (w AND NOT x);  
    End fgl;  
Function feq (w, x, eq: BIT) Return BIT IS  
    Begin  
        Return (w AND x AND eq) OR (NOT w AND NOT x AND eq);  
    End feq;  
    .  
    .  
    .  
End Basic_Uilities;
```

94

...Another Package Example

```
USE WORK.Basic_Uilities.ALL
Architecture Functional of Bit_Comparator IS
Begin
  a_gt_b <= fgl (a, b, gt) after 12 ns;
  a_eq_b <= feq (a, b, eq) after 12 ns;
  a_lt_b <= fgl (b, a, lt) after 12 ns;
End Functional;
```

95

Design Libraries...

- VHDL supports the use of design libraries for categorizing components or utilities.
- Applications of libraries include
 - Sharing of components between designers
 - Grouping components of standard logic families
 - Categorizing special-purpose utilities such as subprograms or types
- Two Types of Libraries
 - Working Library (WORK) {A *Predefined* library into which a *Design Unit is Placed after Compilation.*}
 - Resource Libraries {Contain design units that can be referenced within the design unit being compiled}.

96

... Design Libraries...

- Only one library can be the **Working** library
- Any number of Resource Libraries may be used by a Design Entity
- There is a number of predefined Resource Libraries
- The **Library** clause is used to make a given library visible
- The **Use** clause causes Package Declarations within a Library to be visible
- Library management tasks, e.g. Creation or Deletion, are not part of the VHDL Language Standard → Tool Dependent

97

... Design Libraries...

- **Existing libraries**
 - STD Library
 - Contains the **STANDARD** and **TEXTIO** packages
 - Contains all the standard types & utilities
 - Visible to all designs
 - WORK library
 - Root library for the user
- **IEEE library**
 - Contains VHDL-related standards
 - Contains the std_logic_1164 (IEEE 1164.1) package
 - Defines a nine values logic system
 - De Facto Standard for all Synthesis Tools

98

...Design Libraries

- To make a library visible to a design
 - LIBRARY libname;
- The following statement is assumed by all designs
 - LIBRARY WORK;
- To use the `std_logic_1164` package
 - LIBRARY IEEE
 - USE IEEE.std_logic_1164.ALL
- By default, every design unit is assumed to contain the following declarations:
 - LIBRARY STD , work ;
 - USE STD.Standard.All ;

99


Arithmetic & Logical Operators for `std_logic` : Example

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity example is
port (a, b: IN std_logic_vector (7 downto 0));
end example;
architecture try of example is
signal x1, x2, x3, x4, x5, x6, x7, x8, x9, x10, x11, x12 : std_logic_vector (7 downto 0);
begin
  x1 <= not a;
  x2 <= a and b;
  x3 <= a nand b;
  x4 <= a or b;
  x5 <= a nor b;
  x6 <= a xor b;
  x7 <= a xnor b;
  x8 <= a + b;
  x9 <= a - b;
  x10 <= "+" (a, b);
end try;
```

100

Data Types

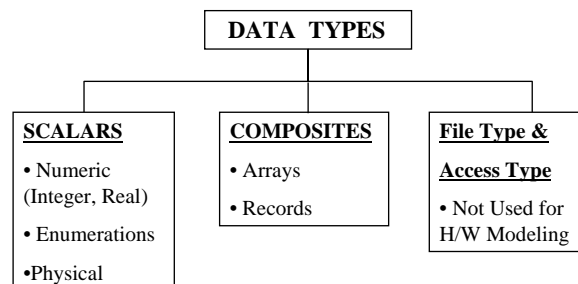- A Data Type defines a set of values & a set of operations.
- VHDL is a strongly-typed Language. Types cannot be mixed in Expressions or in assigning values to Objects in general



101

Scalar Data Types

- **SYNTAX**
 - TYPE Identifier IS Type-Definition
- **Numeric Data Type**
 - Type-Definition is a Range_Constraint as follows:
 - Type-Definition := Range Initial-Value < To | DownTo> Final-Value
- **Examples**
 - TYPE address IS RANGE 0 To 127;
 - TYPE index IS RANGE 7 DownTo 0;
 - TYPE voltage IS RANGE -0.5 To 5.5;

102

Number Formats

- Integers have no Decimal Point.
- Integers may be Signed or Unsigned (e.g. -5 356)
- A Real number must have either a Decimal Point, a -ive Exponent Term (Scientific Notation), or both.
- Real numbers may be Signed or Unsigned (e.g. -3.75 1E-9 1.5E-12)
- Based Numbers:
 - Numbers Default to Base 10 (Decimal)
 - VHDL Allows Expressing Numbers Using Other Bases
 - Syntax
 - B#nnnn# -- Number nnnn is in Base B
 - Examples
 - 16#DF2# -- Base 16 Integer (HEX)
 - 8#7134# -- Base 8 Integer (OCTAL)
 - 2#10011# -- Base 2 Integer (Binary)
 - 16#65_3EB.37# -- Base 16 REAL (HEX)

103

Predefined Numeric Data Types

- **INTEGER** -- Range is Machine limited but At Least $-(2^{31} - 1)$ To $(2^{31} - 1)$
- **POSITIVE** -- INTEGERS > 0
- **NATURAL** -- INTEGERS ≥ 0
- **REAL** -- Range is Machine limited

104

Enumeration Data Type

- **Parenthesized ordered list of literals.**
 - Each may be an identifier or a character literal.
 - The list elements are separated by commas
- **A Position # is associated with each element in the List**
- **Position #'s begin with 0 for the Leftmost Element**
- **Variables & Signals of type ENUMERATION will have the leftmost element as their Default (Initial) value unless, otherwise explicitly assigned.**
- **Examples**
 - TYPE Color IS (Red, Orange, Yellow, Green, Blue, Indigo, Violet);
 - TYPE Tri_Level IS (`0`, `1`, `Z`);
 - TYPE Bus_Kind IS (Data, Address, Control);
 - TYPE state IS (Init, Xmit, Receive, Wait, Terminal);

105

Predefined Enumerated Data Types

- TYPE BIT IS (`0` , `1`);
- TYPE BOOLEAN IS (False, True);
- TYPE CHARACTER IS (128 ASCII Chars.....) ;
- TYPE Severity_Level IS (Note, Warning, Error, Failure) ;
- TYPE Std_U_Logic IS (
 - `U` , -- Uninitialized
 - `X` , -- Forcing Unknown
 - `0` , -- Forcing 0
 - `1` , -- Forcing 1
 - `Z` , -- High Impedence
 - `W` , -- Weak Unknown
 - `L` , -- Weak 0
 - `H` , -- Weak 1
 - `-` , -- Don't Care);
- SUBTYPE Std_Logic IS resolved Std_U_Logic ;

106

Physical Data Type

- Specifies a Range Constraint , one Base Unit, and 0 or more secondary units.
- Base unit is indivisible, i.e. no fractional quantities of the Base Units are allowed.
- Secondary units must be integer multiple of the indivisible Base Unit.

- **Examples**

```
TYPE Resistance IS Range 1 To Integer'High
Units
  Ohm;      -- Base Unit
  Kohm = 1000 Ohm;  -- Secondary Unit
  Mohm = 1000 Kohm; -- Secondary Unit
end Units ;
```

107

Predefined Physical Data Types

- Time is the **ONLY** predefined Physical data type

```
TYPE Time IS Range 0 To 1E20
Units
  fs;  -- Base Unit (Femto Second = 1E-15 Second)
  ps = 1000 fs;  -- Pico_Second
  ns = 1000 ps;  -- Nano_Second
  us = 1000 ns;  -- Micro_Second
  ms = 1000 us;  -- Milli_Second
  sec = 1000 ms; -- Second
  min = 60 sec;  -- Minute
  hr = 60 min;   -- Hour
end Units ;
```

108

Composite Data Types: Arrays

- Elements of an Array have the same data type
- Arrays may be Single/Multi - Dimensional
- Array bounds may be either Constrained or Unconstrained.
- **Constrained Arrays**
 - Array Bounds Are Specified
 - Syntax:
 - TYPE id Is Array (Range_Constraint) of Type;
- **Examples**
 - TYPE word Is Array (0 To 7) of Bit;
 - TYPE pattern Is Array (31 DownTo 0) of Bit;
 - 2-D Arrays
 - TYPE col Is Range 0 To 255;
 - TYPE row Is Range 0 To 1023;
 - TYPE Mem_Array Is Array (row, col) of Bit;
 - TYPE Memory Is Array (row) of word;

109

Unconstrained Arrays

- Array Bounds not specified through using the notation RANGE<>
- Type of each Dimension is specified, but the exact Range and Direction are not Specified.
- Useful in Interface_Lists → Allows Dynamic Sizing of Entities , e.g. Registers.
- Bounds of Unconstrained Arrays in such entities assume the Actual Array Sizes when wired to the Actual Signals.
- **Example**
 - TYPE Screen Is Array (Integer Range<> , Integer Range<>) of BIT;

110

Predefined Array Types

- **Two UNCONSTRAINED Array Types are predefined**
- **BIT_VECTOR**
 - TYPE Bit_Vector Is Array (Natural Range<>) of Bit;
- **String**
 - TYPE String Is Array (Positive Range<>) of Character;
- **Example**
 - SUBTYPE Pixel Is Bit_Vector (7 DownTo 0);

111

DATA FLOW MODEL

- **Represents Register Transfer operations**
- **There is Direct Mapping between Data Flow Statements && Register Structural Model**
 - Implied Module Connectivity
 - Implied Muxes & Buses
- **Main Data Flow VHDL Constructs**
 - Concurrent Signal Assignment Statements
 - Block Statement

112

Signal Assignment ...

- Unconditional: Both Sequential & Concurrent.
- Conditional: Only Concurrent; Conditions must be Boolean, may overlap and need not be Exhaustive.
- Selected: Only Concurrent; Cases must not overlap and must be Exhaustive.
- Conditional Signal Assignment

```
[ Label: ] target <= [Guarded] [Transport ]
      Wave1  when Cond1  Else
      Wave2  when Cond2  Else
      .....
      Waven-1 when Condn-1 Else
      Waven ; -- Mandatory Wave
```

113

... Signal Assignment

- Selected Signal Assignment

```
With Expression Select
      target <= [Guarded] [Transport]
      Wave1  when Choice1 ,
      Wave2  when Choice2 ,
      .....
      Waven-1 when Choicen-1 ,
      Waven  when OTHERS ;
```

VHDL-93: Any *Wave_i* can be replaced by the Keyword **UNAFFECTED** (Which doesn't schedule any Transactions on the target signal.)

114

Signal Assignment Examples

Example: A 2x4 Decoder

Signal D : Bit_Vector(1 To 4) := "0000";

Signal S0, S1 : Bit;

.....
Decoder: D <= "0001" after T When S1='0' and S0='0' else
 "0010" after T When S1='0' else
 "0100" after T When S0='0' else "1000";

Example: 4-Phase Clock Generator

Signal Phi4 : Bit_Vector(1 To 4) := "0000";


.....
ClkGen: With Phi4 Select

Phi4 <= "1000" after T When "0000",
 "0100" after T When "1000",
 "0010" after T When "0100",
 "0001" after T When "0010",
 "1000" after T When "0001",
 "0000" When **Others** ; -- Exhaustive

115

Multiplexing ...

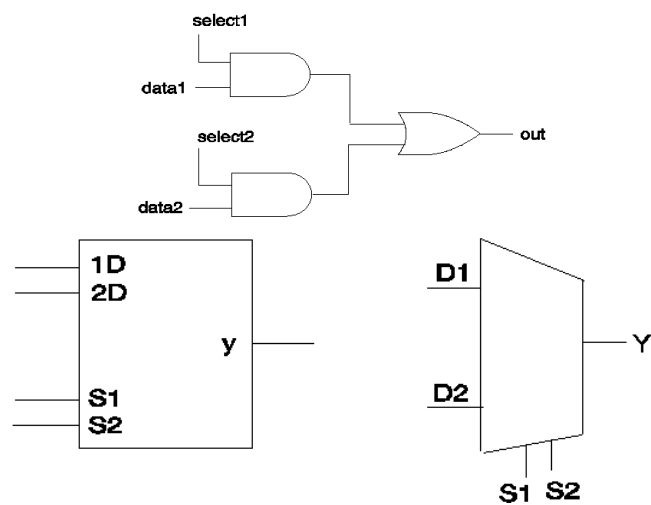- Multiplexers are used for data selection




116

... Multiplexing

```

USE WORK.basic_utilities.ALL;
-- FROM PACKAGE USE: qit, qit_vector
ENTITY mux_8_to_1 IS
PORT (i7, i6, i5, i4, i3, i2, i1, i0 : IN qit;
s7, s6, s5, s4, s3, s2, s1, s0 : IN qit; z : OUT qit );
END mux_8_to_1;
--
ARCHITECTURE dataflow OF mux_8_to_1 IS
SIGNAL sel_lines : qit_vector ( 7 DOWNT0 0);
BEGIN
sel_lines <= s7&s6&s5&s4&s3&s2&s1&s0;
WITH sel_lines SELECT
z <= '0' AFTER 3 NS WHEN "00000000",
i7 AFTER 3 NS WHEN "10000000" | "Z0000000",
i6 AFTER 3 NS WHEN "01000000" | "0Z000000",
i5 AFTER 3 NS WHEN "00100000" | "00Z00000",
i4 AFTER 3 NS WHEN "00010000" | "000Z0000",
i3 AFTER 3 NS WHEN "00001000" | "0000Z000",
i2 AFTER 3 NS WHEN "00000100" | "00000Z00",
i1 AFTER 3 NS WHEN "00000010" | "000000Z0",
i0 AFTER 3 NS WHEN "00000001" | "0000000Z",
'X' WHEN OTHERS;
END dataflow;

```

 


117

3-to-8 Decoder

```

USE WORK.basic_utilities.ALL;
-- FROM PACKAGE USE : qit_vector
ENTITY dcd_3_to_8 IS
PORT (adr : IN qit_vector (2 DOWNT0 0);
so : OUT qit_vector (7 DOWNT0 0));
END dcd_3_to_8;
--
ARCHITECTURE dataflow OF dcd_3_to_8 IS
BEGIN
WITH adr SELECT
so <= "00000001" AFTER 2 NS WHEN "000",
"00000010" AFTER 2 NS WHEN "00Z" | "001",
"00000100" AFTER 2 NS WHEN "0Z0" | "010",
"00001000" AFTER 2 NS WHEN "0ZZ" | "0Z1" | "01Z" |
"011",
"00010000" AFTER 2 NS WHEN "100" | "Z00",
"00100000" AFTER 2 NS WHEN "Z0Z" | "Z01" | "10Z" |
"101",
"01000000" AFTER 2 NS WHEN "ZZ0" | "Z10" | "1Z0" |
"110",
"10000000" AFTER 2 NS WHEN "ZZZ" | "ZZ1" | "Z1Z" |
"Z11" | "1ZZ" | "1Z1" | "11Z" | "111",
"XXXXXXXX" WHEN OTHERS;
END dataflow;

```

 

118

Block Statement

- Block statement is a Concurrent VHDL Construct which is used within an Architectural Body to group (Bind) a set of cConcurrent statements

```
Block_Label: Block [ (Guard_Condition) ] [ IS ]
                Block_Header;
                Block_Declarations;
                Begin
                Concurrent_Statements;
                END Block Block_Label ;
```

- A Guard Condition may be associated with a Block Statement to allow Enabling/Disabling of certain Signal Assignment statements.
- The Guard Condition defines an *Implicit Signal* called *GUARD*.
- In the simplest case, Binding (*Packing !*) statements within a Block has No Effect on the model.
- Blocks can be Nested.

119

Block Statement Example

```
Architecture DF of D_Latch is
  Begin
  B : Block (Clk = `1`)
    Signal I_State :Bit; Block Local Signal
    Begin
      I_State <= Guarded D ;
      Q  <= I_State after 5 ns;
      QB <= not I_State after 5 ns;
    END Block B ;
  END DF ;
```

- UnGuarded Signal Targets (e.g., Q, QB) are independent of the Guard Condition

- If *Guard Condition* (Clk=`1`) is TRUE, *Guarded Statements* within block are Enabled (*Made Active*)
- Guarded Statements (e.g., *I_State*) execute when
 - Guard Condition Becomes True, AND
 - While Guard Condition is True, a Signal on the RHS Changes Value

120

Positive-Edge-Triggered DFF ...

```

Library IEEE;
Use IEEE.Std_Logic_1164.ALL;
Entity DFF is
    Generic(TDel: Time:= 5 NS);
    Port(D, Clk: in Std_Logic; Q, QB: out Std_Logic);
End DFF;
    
```

- We will show several dataflow architectures with and without Block statement.
- Will show why some of these architectures do not work.


121

... Positive-Edge-Triggered DFF ...

```

Arch 1
Architecture DF1_NO_Block of DFF is
    Signal I_State: Std_Logic:='1';
    begin
        I_State <= D when (Clk='1' and
        Clk'Event) else I_state;
        Q <= I_state after TDel ;
        QB <= not I_state after TDel ;
    End DF1_NO_Block ;
    
```

Works

 

Signal Evaluated
2-Times Per
Clock Cycle

122

... Positive-Edge-Triggered DFF ...


Doesn't Work

Arch 2

```

Architecture
DF2_NO_Block of DFF is
Signal I_State:
Std_Logic:='1';
begin
I_State <= D after TDel
when (Clk='1' and
(not(Clk'Stable))) else
I_state;
Q <= I_state;
QB <= not I_state;
End DF2_NO_Block ;
    
```

Signal Evaluated 4-Times Per
Clock Cycle

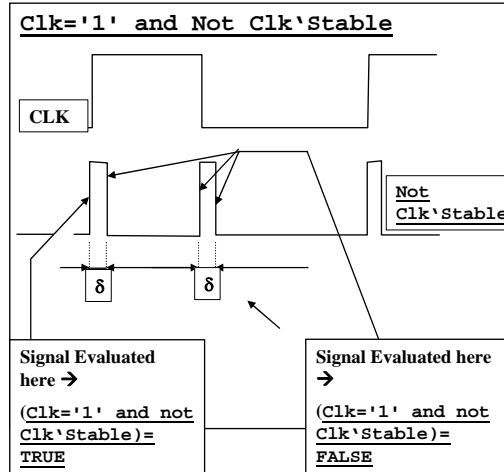

123

... Positive-Edge-Triggered DFF ...

Works

Arch 3

```

Architecture DF3_NO_Block of DFF
is
Signal I_State: Std_Logic:='1';
begin
I_State <= D when (Clk='1' and
(not(Clk'Stable))) else I_state;
Q <= I_state after TDel;
QB <= not I_state after TDel ;
End DF3_NO_Block ;
    
```

*I_State gets the value
of D after 1 delta and
Its value does not get
overwritten*

124

... Positive-Edge-Triggered DFF ...

Arch4


```

Architecture DF1_Block of DFF is
Signal I_State: Std_Logic:='1';
begin
  D_Blck: Block(Clk='1' and Clk'Event)
  Begin
    Q <= Guarded D after Tdel;
    QB <= Guarded not D after Tdel;
  End Block;
End DF1_Block ;

```

Doesn't Work

GUARD <= Clk='1' and Clk'Event

 

Signal Evaluated
Continuously while
Clk = '1' !!!

125

Positive-Edge-Triggered DFF ...

Arch5


```

Architecture DF2_Block of DFF is
Signal I_State: Std_Logic:='1';
begin
  D_Blck: Block(Clk='1' and not Clk'Stable)
  Begin
    Q <= Guarded D after Tdel;
    QB <= Guarded not D after Tdel;
  End Block;
End DF2_Block ;

```

Works

GUARD <= Clk='1' and not Clk'Stable

 

Signal Evaluated
Once Per Clock Cycle
(At Rising Edge of the
Clock)

126

Use of Nested Blocks For Composite Enabling Conditions

```
ARCHITECTURE guarding OF DFF IS
BEGIN
  edge: BLOCK ( c = '1' AND NOT c'STABLE )
  BEGIN
    gate: BLOCK ( e = '1' AND GUARD )
    BEGIN
      q <= GUARDED d AFTER delay1;
      qb <= GUARDED NOT d AFTER delay2;
    END BLOCK gate;
  END BLOCK edge;
END guarding;
```

- Inner Guard Signal <= (e= '1') AND (c= '1' AND NOT c'STABLE)
- Can nest block statements
- Combining guard expressions must be done explicitly
- Implicit GUARD signals in each block

127

Data Flow Example ...

Model A System with 2 8-Bit Registers R1 and R2, a 2-Bit Command signal "COM" and an external 8-Bit Input "INP"

- When Com= "00" → R1 is Loaded with External Input
- When Com= "01" → R2 is Loaded with External Input
- When Com= "10" → R1 is Loaded with **R1+R2**
- When Com= "11" → R1 is Loaded with **R1-R2**

Use Work.Utils_Pkg.ALL

Entity DF_Ex is

Port (Clk: IN Bit; Com: IN Bit_Vector (1 DownTo 0); INP: IN Bit_Vector(7 DownTo 0));

End DF_Ex;

128

... Data Flow Example ...

Architecture DF of DF_Ex is

Signal **Mux_R1**, R1, R2, R2C, R2TC, Mux_Add,

Sum: Bit_Vector(7 DownTo 0);

Signal **D00**, **D01**, **D10**, **D11**, **LD_R1**: Bit;

Begin

D00 <= not **Com(0)** and not **Com(1)**; -- *Decoder*

D01 <= not **Com(0)** and **Com(1)**; -- *Decoder*

D10 <= **Com(0)** and not **Com(1)**; -- *Decoder*

D11 <= **Com(0)** and **Com(1)**; -- *Decoder*

R2C <= not **R2**;

R2TC <= **INC(R2C)**; -- *Increment Function Defined in the Package*

Mux_Add <= **R2TC** when **D11** = '1' Else **R2** ;

129

... Data Flow Example

Sum <= **ADD(R1, Mux_Add)**; -- *ADD Function-- Defined in Package*

Mux_R1 <= **INP** when **D00** = '1' Else **Sum**;

R1E <= **D00 OR D10 OR D11**;

Rising Edge: **BLOCK**(Clk='1' and not Clk'Stable)

R1_Reg: **BLOCK**(**R1E**='1' AND **GUARD**)

R1 <= **Guarded Mux_R1** ;

End Block R1_Reg ;

R2_Reg: **BLOCK**(**D01**='1' AND **GUARD**)

R2 <= **Guarded INP** ;

End Block R2_Reg ;

End Block Rising Edge;

End DF;

130

Concurrent Versus Sequential Statements

Sequential Statements

- Used Within Process Bodies or SubPrograms
- Order Dependent
- Executed When Control is Transferred to the Sequential Body

- Assert
- Signal Assignment
- Procedure Call
- Variable Assignment
- IF Statements
- Case Statement
- Loops
- Wait, Null, Next, Exit, Return

Concurrent Statements


- Used Within Architectural Bodies or Blocks
- Order Independent
- Executed Once *At the Beginning of Simulation* or Upon Some Triggered Event

- Assert
- Signal Assignment
- Procedure Call (*None of Formal Parameters May be of Type Variable*)
- Process
- Block Statement
- Component Statement
- Generate Statement
- Instantiation Statement

131

Process Statement ...

 - Main construct for Behavioral Modeling.
- Other concurrent statements can be modeled by an equivalent process.
- Process statement is a Concurrent construct which performs a set of consecutive (Sequential) actions once it is activated. Thus, only sequential statements are allowed within the Process Body.




132

... Process Statement ...

- **Unless sequential part is suspended**

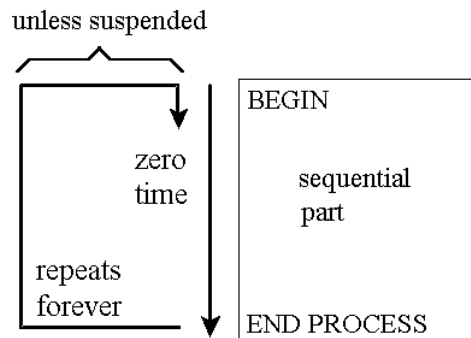- It executes in zero real and delta time
- It repeats itself forever



133

... Process Statement

- Whenever a **SIGNAL** in the *Sensitivity_List* of the Process changes, the Process is **ACTIVATED**.
- After executing the last statement, the Process is **SUSPENDED** until one (or more) signal in the Process *Sensitivity_List* changes value where it will be **REACTIVATED**.
- A Process statement *Without* a *Sensitivity_List* is **ALWAYS ACTIVE**, i.e. after the last statement is executed, execution returns to the first statement and continues (*Infinite Looping*).
- It is **ILLEGAL** to Use **WAIT-Statement** Inside a Process which has a *Sensitivity_List*.
- In case no *Sensitivity_List* exists, a Process may be activated or suspended using the *WAIT-Statement*.
- Conditional and selective signal assignments are strictly concurrent and cannot be used in a process.

134

Process Examples

Process
Begin

```
A<= `1`;  
B <= `0`;
```

End Process;

Sequential Processing:

- First A is Scheduled to have a value `1`
- Second B is Scheduled to have a value `0`
- A & B get their new values at the SAME TIME (1 Delta Time Later)

Process
Begin

```
A<= `1`;  
IF (A= `1`) Then Action1;  
Else Action2;  
End IF;
```

End Process;

Assuming a `0` Initial Value of A,

- First A is Scheduled to Have a Value `1` One Delta Time Later
- Thus, Upon Execution of IF_Statement, A Has a Value of `0` and Action 2 will be Taken.
- If A was Declared as a Process Variable, Action1 Would Have Been Taken.

135

Wait Statement

■ Syntax of Wait Statement

- WAIT; -- Forever
- WAIT ON *Signal_List*; -- On event on a signal
- WAIT UNTIL *Condition*; -- until event makes condition true;
- WAIT FOR *Time_Out_Expression*;
- WAIT FOR 0 *any_time_unit*; -- Process Suspended for 1 delta

■ When a WAIT-Statement is executed, the process suspends and conditions for its Reactivation are set.

■ Process Reactivation conditions may be Mixed as follows

- WAIT ON *Signal_List* UNTIL *Condition* FOR *Time_Expression* ;
- wait on X,Y until (Z = 0) for 70 NS; -- Process Resumes After 70 NS OR (in Case X or Y Changes Value and Z=0 is True) **Whichever Occurs First**
- Process Reactivated IF:
 - Event Occurred on the *Signal_List* while the *Condition* is True, OR
 - Wait Period Exceeds ``*Time_Expression*``

136

Positive Edge-Triggered D-FF Examples


```
D_FF: PROCESS (CLK)
  Begin
    IF (CLK' Event and CLK = `1') Then
      Q <= D After TDelay;
    END IF;
  END Process;
```

```
D_FF: PROCESS -- No Sensitivity_List
  Begin
    WAIT UNTIL CLK = `1';
    Q <= D After TDelay;
  END Process;
```

```
D_FF: PROCESS (Clk, Clr) -- FF With Asynchronous Clear
  Begin
    IF Clr= `1' Then Q <= `0' After TD0;
    ELSIF (CLK' Event and CLK = `1') Then Q <= D After TD1;
    END IF;
  END Process;
```

137

Sequential Statements

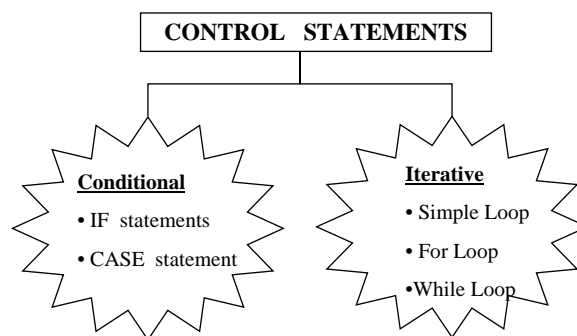

138

Conditional Control – IF Statement

- **Syntax:** 3-Possible Forms

- (i) **IF** *condition* **Then**
 statements;
 End IF;
- (ii) **IF** *condition* **Then**
 statements;
 Else
 statements;
 End IF;
- (iii) **IF** *condition* **Then**
 statements;
 Elsif *condition* **Then**
 statements;

 Elsif *condition* **Then**
 statements;
 End IF;

139

Conditional Control – Case Statement

- **Syntax:**

- (i) **CASE** *Expression* **is**
 when *value* => *statements;*
 when *value1* | *value2* | ... | *valuen* => *statements;*
 when *discrete range of values* => *statements;*
 when **others** => *statements;*
 End CASE;
- Values/Choices should not overlap (*Any value of the Expression should evaluate to only one arm of the case statement*).
- All possible choices for the *Expression* should be accounted for Exactly Once.

140

Conditional Control – Case Statement

- If ``others`` is used, It must be the last ``arm`` of the CASE statement.
- There can be any number of arms in Any Order (*Except for the others arm which should be Last*).

```
CASE x is
  when 1 => y :=0;
  when 2 | 3 => y :=1;
  when 4 to 7 => y :=2;
  when others => y :=3;
End CASE;
```

141

Loop Control ...

- Simple Loops
- Syntax:
[Loop_Label:] LOOP
 statements;
 End LOOP [Loop_Label];
- The Loop_Label is Optional.
- The exit statement may be used to exit the Loop. It has two possible Forms:
 - exit [Loop_Label]; -- This may be used in an if statement
 - exit [Loop_Label] when condition;

142

...Loop Control

Process

variable A : Integer :=0;

variable B : Integer :=1;

Begin

Loop1: LOOP

A := A + 1;

B := 20;

Loop2: LOOP

IF B < (A * A) Then

exit Loop2;

End IF;

B := B - A;

End LOOP Loop2;

exit Loop1 when A > 10;

End LOOP Loop1;

End Process;

143

FOR Loop

■ **Syntax:**

Need Not Be Declared

[Loop_Label]: FOR Loop_Variable in range LOOP
statements;
End LOOP Loop_Label;

Process

variable B : Integer :=1;

Begin

Loop1: FOR A in 1 TO 10 LOOP

B := 20;

Loop2: LOOP

IF B < (A * A) Then

exit Loop2;

End IF;

B := B - A;

End LOOP Loop2;

End LOOP Loop1;

End Process;

144

WHILE Loop

■ Syntax:

```
[Loop_Label]: WHILE condition LOOP
    statements;
End LOOP Loop_Label;
```


```
Process
    variable B:Integer :=1;
Begin
    Loop1: FOR A in 1 TO 10 LOOP
        B := 20;
        Loop2: WHILE B < (A * A) LOOP
            B := B - A;
        End LOOP Loop2;
    End LOOP Loop1;
End Process;
```

145

A Moore 1011 Detector using Wait

```
ENTITY moore_detector IS
    PORT (x, clk : IN BIT;
          z : OUT BIT);
END moore_detector;
```

 - Can use **WAIT** in a Process statement to check for events on *clk*.



```
ARCHITECTURE behavioral_state_machine OF moore_detector IS
    TYPE state IS (reset, got1, got10, got101, got1011);
    SIGNAL current : state := reset;
BEGIN
```

146

A Moore 1011 Detector using Wait

```
PROCESS
BEGIN
CASE current IS
WHEN reset => WAIT UNTIL clk = '1';
  IF x = '1' THEN current <= got1; ELSE current <= reset; END IF;
WHEN got1 => WAIT UNTIL clk = '1';
  IF x = '0' THEN current <= got10; ELSE current <= got1; END IF;
WHEN got10 => WAIT UNTIL clk = '1';
  IF x = '1' THEN current <= got101; ELSE current <= reset; END IF;
WHEN got101 => WAIT UNTIL clk = '1';
  IF x = '1' THEN current <= got1011; ELSE current <= got10; END IF;
WHEN got1011 => z <= '1'; WAIT UNTIL clk = '1';
  IF x = '1' THEN current <= got1; ELSE current <= got10; END IF;
END CASE;
WAIT FOR 1 NS; z <= '0';
END PROCESS;
END behavioral_state_machine;
```

147

A Moore 1011 Detector without Wait

```
ARCHITECTURE most_behavioral_state_machine OF moore_detector IS
TYPE state IS (reset, got1, got10, got101, got1011);
SIGNAL current : state := reset;
BEGIN
PROCESS (clk)
BEGIN
IF (clk = '1' and CLK'Event) THEN
CASE current IS
WHEN reset =>
  IF x = '1' THEN current <= got1; ELSE current <= reset; END IF;
WHEN got1 =>
  IF x = '0' THEN current <= got10; ELSE current <= got1; END IF;
WHEN got10 =>
  IF x = '1' THEN current <= got101; ELSE current <= reset; END IF;
WHEN got101 =>
  IF x = '1' THEN current <= got1011; ELSE current <= got10; END IF;
WHEN got1011 =>
  IF x = '1' THEN current <= got1; ELSE current <= got10; END IF;
END CASE;
END IF;
END PROCESS;
z <= '1' WHEN current = got1011 ELSE '0';
END most_behavioral_state_machine;
```

148

Generalized VHDL Mealy Model

Architecture Mealy of fsm is

Signal D, Y: Std_Logic_Vector(...); -- Local Signals

Begin

Register: Process(Clk)

Begin

IF (Clk`EVENT and Clk = `1`) Then Y <= D;

End IF;

End Process;

Transitions: Process(X, Y)

Begin

D <= F1(X, Y);

End Process;


Output: Process(X, Y)

Begin

Z <= F2(X, Y);

End Process;

End Mealy;

 

149

Generalized VHDL Moore Model

Architecture Moore of fsm is

Signal D, Y: Std_Logic_Vector(...); -- Local Signals

Begin

Register: Process(Clk)

Begin

IF (Clk`EVENT and Clk = `1`) Then Y <= D;

End IF;

End Process;

Transitions: Process(X, Y)

Begin

D <= F1(X, Y);

End Process;


Output: Process(Y)

Begin

Z <= F2(Y);

End Process;

End Moore;

 

150

FSM Example ...

```
Entity fsm is
port ( Clk, Reset : in Std_Logic;
      X           : in Std_Logic_Vector(0 to 1);
      Z           : out Std_Logic_Vector(1 downto 0));
End fsm;
```

```
Architecture behavior of fsm is
  Type States is (st0, st1, st2, st3);
  Signal Present_State, Next_State : States;
Begin
  register: Process(Reset, Clk)
  Begin
    IF Reset = `1` Then
      Present_State <= st0; -- Machine Reset to st0
    elsif (Clk`EVENT and Clk = `1`) Then
      Present_State <= Next_State;
    End IF;
  End Process;
```

151


... FSM Example

```
Transitions: Process(Present_State, X)
Begin
  CASE Present_State is
    when st0 =>
      Z <= ``00``;
      IF X = ``11`` Then Next_State <= st0;
      else Next_State <= st1; End IF;
    when st1 =>
      Z <= ``01``;
      IF X = ``11`` Then Next_State <= st0;
      else Next_State <= st2; End IF;
    when st2 =>
      Z <= ``10``;
      IF X = ``11`` Then Next_State <= st2;
      else Next_State <= st3; End IF;
    when st3 =>
      Z <= ``11``;
      IF X = ``11`` Then Next_State <= st3;
      else Next_State <= st0; End IF;
  End CASE;
End Process;
End behavior;
```

152

Using Wait for Two-Phase Clocking
 
```
c1 <= not c1 after 500ns;  
phase2: PROCESS  
BEGIN  
  WAIT UNTIL c1 = '0';  
  WAIT FOR 10 NS;  
  c2 <= '1';  
  WAIT FOR 480 NS;  
  c2 <= '0';  
END PROCESS phase2;  
...
```



153