

Jan. 15, 2008

# COMPUTER ENGINEERING DEPARTMENT

COE 561

Digital System Design and Synthesis

MAJOR EXAM II

(Open Book Exam)

First Semester (081)

Time: 12:00-2:30 PM

Student Name : \_\_\_\_\_

Student ID. : \_\_\_\_\_

Question	Max Points	Score
Q1	30	
Q2	15	
Q3	15	
Q4	20	
Q5	20	
Total	100	

[30 Points]

(Q1) Consider the function  $F(A, B, C, D)$  with **ON-SET**= $\Sigma m(3, 4, 5, 7)$  and **OFF-SET**= $\Sigma m(1, 9, 10, 14)$ . Note that you do not need to use the positional-cube notation in your solution.

- (i) **Expand** the minterm  $A'BC'D'$  using ESPRESSO heuristics.
- (ii) A cover of the function is given by  $F = A'B + A'C$ . **Reduce** the cube  $A'C$  using Theorem 7.4.1.
- (iii) Use Corollary 7.4.1 to check if the implicant  $A'C$  is an **essential** prime implicant.



[15 Points]

(Q2) Consider the logic network defined by the following expression:

$$x = a b d e f + a c d e f + a b d e g + a c d e g$$

Using the recursive procedure **KERNELS**, compute all the kernels and co-kernels of  $x$ . Show all the steps of the algorithm. Assume the following lexicographic order: {a, b, c, d, e, f, g}.



**[15 Points]**

**(Q3)** Consider the logic network defined by the following expression:

$$x = a b d' e' + a' c' d' e' + a b' d + a b' e + a' c d + a' c e$$

Compute the weight of the double cube divisors  $d_1 = a b + a' c'$  and  $d_2 = d + e$ . Extract the double cube divisor with the highest weight and show the resulting network after extraction and the number of literals saved.

**[20 Points]**

**(Q4)** Consider the logic network defined by the following expressions with inputs  $\{a, b, c\}$  and output  $\{y\}$ :

$$w = b' c a' + b c'$$

$$x = w \oplus c$$

$$y = w b + w a + x$$


- (i)** Simplify the function  $x$  based on the utilization of don't care conditions.
- (ii)** Based on perturbation analysis, determine if it is possible to change the implementation of  $w$  to  $w=b + c$ .





**[20 Points]**

 **(Q5)** Consider the logic network below with inputs  $\{a, b, c, d, e\}$  and output  $\{k\}$ :



Assume that the delay of the inverter gate is 1 and that the delay of the 2-input NAND gate is 2. Also, assume that the input data-ready times are zero except for input  $a$ , which is equal to 2.

- (i) Compute the data ready times and slacks for all vertices in the network.
- (ii) Determine the topological critical path.
- (iii) Suggest an implementation of the function  $k$  using only inverters and 2-input NAND gates to reduce the delay of the circuit to the minimum possible and determine the maximum propagation delay in the optimized circuit. Has the area been affected?

