

### SIS Results:

Q1 (ii)

```
{X} = A B E F + A B G' H' + A' B' C' D' + C D E F + C D G' H'  
{Y} = A B + C D  
sis> print_stats  
hw3q1.eqn pi= 8 po= 2 node= 2 latch= 0 lits(sop)= 24 lits(ff)= 16  
sis> resub -d  
sis> print  
{X} = A' B' C' D' + E F {Y} + G' H' {Y}  
{Y} = A B + C D  
sis> print_stats  
hw3q1.eqn pi= 8 po= 2 node= 2 latch= 0 lits(sop)= 14 lits(ff)= 13
```

Q2 (iii)

```
{X} = A C E + A D' E' + B C E + B D' E' + C' E' + D E  
sis> print_stats  
hw3q2.eqn pi= 6 po= 1 node= 1 latch= 0 lits(sop)= 16 lits(ff)= 10  
sis> factor -q X  
sis> print_factor  
{X} = (D' E' + C E) (B + A) + C' E' + D E  
sis> print_stats -f  
hw3q2.eqn pi= 6 po= 1 node= 1 latch= 0 lits(sop)= 16 lits(ff)= 10
```

Q3 (ii)

```
{X} = A B C D + A B C' D' + A B E F' + A B E' F + A B G + A B H + A B K + A  
B L + C D' G + C' D G + G' H' K + G' H' L  
sis> print_stats  
hw3q3.eqn pi=10 po= 1 node= 1 latch= 0 lits(sop)= 40 lits(ff)= 23  
sis> fx  
sis> print  
{X} = E F' [1] + E' F [1] + G [2] + K [3] + L [3] + [1] [2]' + [1] [4]  
[1] = A B  
[2] = C D' + C' D  
[3] = [1] + [4]'  
[4] = G + H  
sis> print_stats  
hw3q3.eqn pi=10 po= 1 node= 5 latch= 0 lits(sop)= 26 lits(ff)= 22
```

Q4 (vi)

```
{F} = A' C D' + D E
D = A + B
E = A C' + B C
sis> print_stats
hw3q4.eqn pi= 3 po= 1 node= 3 latch= 0 lits(sop)= 11 lits(ff)= 11
sis> full_simplify
sis> print
{F} = C D' + E
D = A + B
E = A C' + B C
sis> print_stats
hw3q4.eqn pi= 3 po= 1 node= 3 latch= 0 lits(sop)= 9 lits(ff)= 9
```