

# **COE 571 Digital System Testing**


**Dr. Aiman El-Maleh**

## **Test Response Compaction**

- 1. Signature analysis**
- 2. Linear feedback shift registers (LFSRs)**
- 3. Types of LFSRs**
- 4. Characteristic & reciprocal characteristic polynomials**
- 5. Periodicity of LFSRs**
- 6. Primitive polynomials**
- 7. Signature analyzers**
- 8. Multiple input signature register (MISR)**
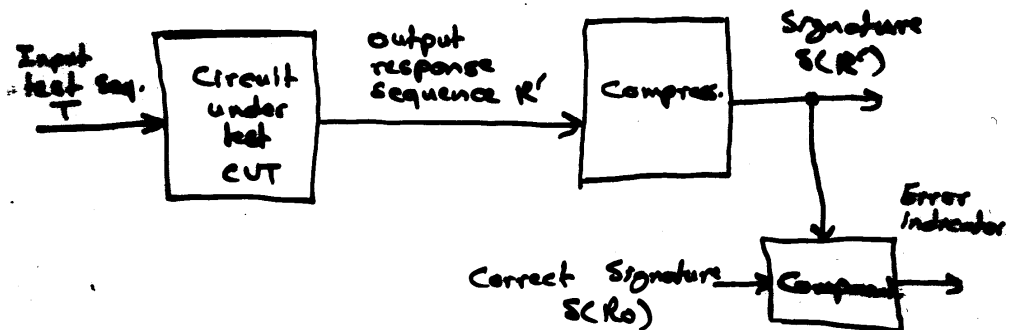
## Testing using Test-Response Compression

- Observed test responses are saved in a compressed form, called signature
- A circuit is tested by comparing observed signature with correct signature
- Process of reducing test responses to a signature is called response compacting or compressing.



- A fault is detected if signature  $S(R) \neq$  fault-free signature  $S(R_0)$
- Compression is important aspect of built-in self-test (BIST).

## Signature Analysis


- Signature analysis is a compression technique based on cyclic redundancy checking (CRC) and realized by linear feedback shift registers (LFSRs).
- LFSRs used as:
  - source of pseudorandom binary test sequence
  - carry out response compression
- A linear circuit is a logic network constructed from:
  - unit delays or D ffs
  - modulo-2 adders
  - modulo-2 scalar multipliers
- In the analysis of such circuits, all operations done are modulo-2
- Such a circuit is linear since it preserves principle of superposition:
  - its response to a linear combination of stimuli is linear combination of responses to individual stimuli

modulo-2 addition/subtraction


$\pm$	0	1
0	0	1
1	1	0

$$x+x = -x-x = x-x = 0$$


# Feedback Shift Registers

 


(a)

 

(b)

 

(c)

 

(d)

# Types of LFSRs

- $c_i = 1 \Rightarrow$  There is a connection, otherwise no connection

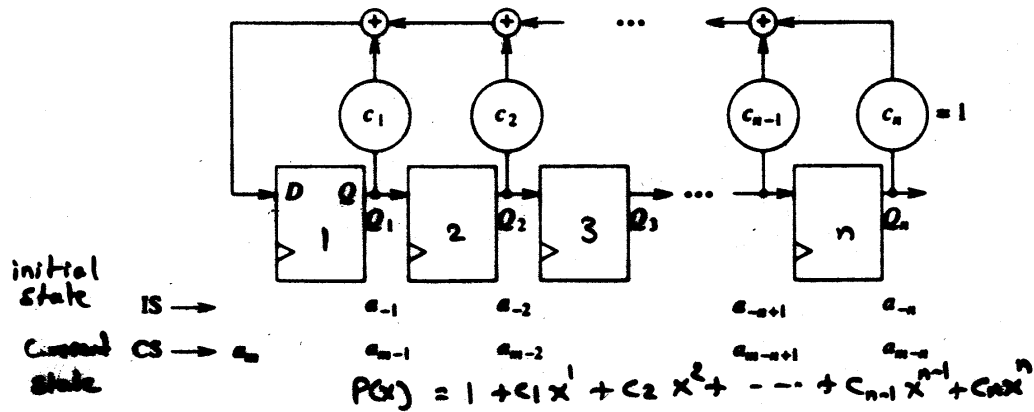


Figure 10.10 Type 1 (external-XOR) LFSR

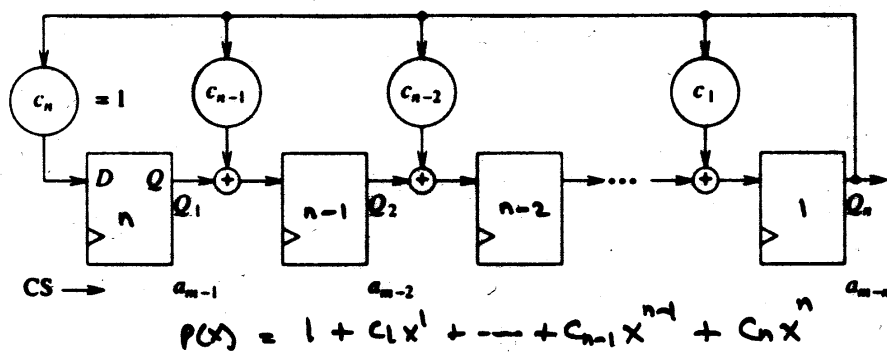


Figure 10.11 Type 2 (internal-XOR) LFSR

- A sequence of numbers  $a_0, a_1, \dots, a_m$  can be associated with a polynomial called a generating function  $G(x) = a_0 + a_1x + a_2x^2 + \dots + a_mx^m$

- Let  $\{a_m\} = a_0, a_1, a_2, \dots$  represent the output sequence generated by LFSR;  $a_i = 0$  or  $1$

- This sequence can be expressed as:

$$G(x) = \sum_{m=0}^{\infty} a_m x^m$$

- From structure of typical LFSR, if current state of  $Q_i$  is  $a_{m-i}$  for  $i=1, 2, \dots, n$

$$a_m = \sum_{i=1}^n c_i a_{m-i}$$

- Thus, the operation of LFSR can be defined by a recurrence relation

- Let initial state of LFSR be  $a_{-1}, a_{-2}, \dots, a_{-n}$

$$\begin{aligned} G(x) &= \sum_{m=0}^{\infty} a_m x^m = \sum_{m=0}^{\infty} \sum_{i=1}^n c_i a_{m-i} x^m \\ &= \sum_{i=1}^n c_i x^i \sum_{m=0}^{\infty} a_{m-i} x^{m-i} \end{aligned}$$

Let  $j = m-i$

$$\begin{aligned} \Rightarrow \sum_{m=0}^{\infty} a_{m-i} x^{m-i} &= \sum_{j=-i}^{\infty} a_j x^j \\ &= a_{-i} x^{-i} + \dots + a_{-1} x^{-1} + \sum_{j=0}^{\infty} a_j x^j \end{aligned}$$

$$\Rightarrow G(x) = \sum_{i=1}^n c_i x^i [a_{-2} x^2 + \dots + a_{-1} x^{-1} + G(x)]$$

$$\Rightarrow G(x) = \sum_{i=1}^n c_i x^i G(x) + \sum_{i=1}^n c_i x^i (a_{-2} x^2 + \dots + a_{-1} x^{-1})$$

$$\text{or } G(x) = \frac{\sum_{i=1}^n c_i x^i (a_{-2} x^2 + \dots + a_{-1} x^{-1})}{1 + \sum_{i=1}^n c_i x^i}$$

- Thus,  $G(x)$  is a function of the initial state  $a_{-1}, a_{-2}, \dots, a_{-n}$  of the LFSR and feedback coefficients.

- The denominator denoted by

$$P(x) = 1 + c_1 x + c_2 x^2 + \dots + c_n x^n$$

is the characteristic polynomial of the sequence  $\{a_m\}$  and the LFSR

- For an  $n$ -stage LFSR,  $c_n = 1$ .

- If we set  $a_{-1} = a_{-2} = \dots = a_{-n} = 0$  and  $a_{-n+1} = 1$

$$G(x) = \frac{1}{P(x)} = \sum_{m=0}^{\infty} a_m x^m$$

- Since the sequence  $\{a_n\}$  is cyclic with period  $p$

$$\begin{aligned} \frac{1}{p(x)} &= (a_0 + a_1x + \dots + a_{p-1}x^{p-1}) \\ &\quad + x^p (a_0 + a_1x + \dots + a_{p-1}x^{p-1}) \\ &\quad + x^{2p} (a_0 + a_1x + \dots + a_{p-1}x^{p-1}) + \dots \\ &= (a_0 + a_1x + \dots + a_{p-1}x^{p-1})(1 + x^p + x^{2p} + \dots) \\ &= \frac{a_0 + a_1x + \dots + a_{p-1}x^{p-1}}{1 - x^p} \end{aligned}$$

- Thus,  $p(x)$  evenly divides into  $1 - x^p$

- For type 1 LFSR  $a_m(t) = \sum_{i=1}^n c_i a_{m-i}(t)$

- Note that  $a_i(t) = a_{i+1}(t-1)$

- Let  $x$  be a shift operator such that

$$x^k a_i(t) = a_i(t-k)$$

$$\Rightarrow a_m(t) = \sum_{i=1}^n c_i a_{m-i}(t) = \sum_{i=1}^n c_i x^i a_m(t)$$

- Note that  $x a_m(t) = a_m(t-1) = a_{m-1}(t)$



$$\Rightarrow a_n + c_1 x a_n + c_2 x^2 a_n + \dots + c_n x^n a_n = 0$$

$$\text{or } \underbrace{[1 + c_1 x + c_2 x^2 + \dots + c_n x^n]}_{\text{characteristic Polynomial}} a_n = 0$$

- Let  $y^{-k} a_i(t) = a_i(t-k) = x^k a_i(t)$

$$\Rightarrow [1 + c_1 y^{-1} + c_2 y^{-2} + \dots + c_n y^{-n}] a_n = 0$$

$$\Rightarrow [y^n + c_1 y^{n-1} + c_2 y^{n-2} + \dots + c_n] a_n y^{-n} = 0$$

- Replacing  $y$  by  $x$


$$\Rightarrow p^*(x) = c_n + c_{n-1} x + c_{n-2} x^2 + \dots + c_1 x^{n-1} +$$

-  $p^*(x)$  is said to be reciprocal polynomial of  $p(x)$  since  $p^*(x) = x^n p(1/x)$


- Thus, every LFSR can be associated with two characteristic polynomials

- Note that  $p^*(x)$  produces the reverse of what  $p(x)$  produces

# Reciprocal Characteristic Polynomials

 

(a)

 

(b)


**Figure 10.12** Reciprocal characteristic polynomials

(a)  $P(x) = 1 + c_1x + c_2x^2 + \dots + c_{n-1}x^{n-1} + x^n$   
 (b)  $P^*(x) = 1 + c_{n-1}x + c_{n-2}x^2 + \dots + c_1x^{n-1} + x^n$


# Reciprocal Polynomials
 
## Example

- Let  $P(x) = 1 + x + x^3$
- Its reciprocal polynomial  $P^*(x)$   
 $= x^n P(\frac{1}{x}) = x^3 [1 + x^{-1} + x^{-3}]$   
 $= x^3 + x^2 + 1$



$P(x) = 1 + x + x^3$

 

$P(x) = 1 + x^2 + x^3$

0	0	1		1	0	0
1	0	0		0	1	0
1	1	0		1	0	1
1	1	1	↓	1	1	0
0	1	1		1	1	1
1	0	1	↑	0	1	1
0	1	0		0	0	1
0	0	1		1	0	0

Generated Sequence:

1, 0, 0, 1, 1, 0, 1, 0, 0, ...


Generated Sequence:

1, 0, 1, 1, 0, 0, 1, 0, 1, ...

## Type 2 LFSR
 
### Characteristic Polynomial

- A given characteristic polynomial can be realized by two different LFSRs.



- For  $i = 2, 3, \dots, n$

$$a_{m-i}(t+1) = a_{m-i+1}(t) + C_{n-i+1} a_{m-n}(t)$$

If we define  $a_m(t) = 0$ , the equation also holds for  $i=1$

- Let  $X$  be a shift operator such that

$$X^k a_i(t) = a_i(t-k)$$

$$\Rightarrow X^{-1} a_{m-i}(t) = a_{m-i+1}(t) + C_{n-i+1} a_{m-n}(t)$$

for  $i = 1, 2, \dots, n$

- Multiplying the  $i$ th equation by  $x^{-i+1}$  we get:

$$x^{-1} a_{m-1} = c_n a_{m-n}$$

$$x^{-2} a_{m-2} = x^{-1} a_{m-1} + c_{n-1} x^{-1} a_{m-n}$$

$$x^{-3} a_{m-3} = x^{-2} a_{m-2} + c_{n-2} x^{-2} a_{m-n}$$

⋮

$$x^{-n} a_{m-n} = x^{-n+1} a_{m-n+1} + c_1 x^{-n+1} a_{m-n}$$

- Summing these equations & canceling terms appearing on both sides:

$$\Rightarrow x^{-n} a_{m-n} = [c_1 x^{-n+1} + \dots + c_{n-2} x^{-2} + c_{n-1} x^{-1} + c_n] a_{m-n}$$

$$\text{or } [x^{-n} + c_1 x^{-n+1} + \dots + c_{n-2} x^{-2} + c_{n-1} x^{-1} + c_n] a_{m-n} = 0$$

Multiplying by  $x^n$  we get:

$$[1 + c_1 x + \dots + c_{n-2} x^{n-2} + c_{n-1} x^{-1} + c_n x^n] a_{m-n}$$

Characteristic polynomial

for type 2 LFSR

- A type 2 LFSR can be associated with two characteristic polynomials reciprocal of each other

## Periodicity of LFSRs

- The LFSR goes through a cyclic or periodic sequence of states and the output produced is also periodic
- The maximum length of this period is  $2^n - 1$  where  $n$  is the number of stages
- Theorem: If the initial state of an LFSR is  $a_1 = a_2 = \dots = a_{n-1} = 0, a_n = 1$ , then the LFSR sequence  $\{a_n\}$  is periodic with a period that is the smallest integer  $k$  for which  $P(x)$  divides  $(1 - x^k)$
- Example:  $P(x) = 1 + x + x^3$

$$\begin{array}{r}
 \underline{1+x+x^3} \overline{) x^3+x+1} \\
 \underline{1-x^6} \\
 x^3+x^4+x^6 \\
 \underline{1+x^3+x^4} \\
 x+x^2+x^4 \\
 \underline{1+x+x^2+x^3} \\
 \underline{1+x+x^3} \\
 x^2
 \end{array}$$

So,  $P(x)$  does not divide  $(1-x^6)$

$$\begin{array}{r}
 \underline{1+x+x^3} \overline{) x^4+x^2+x+1} \\
 \underline{1-x^7} \\
 x^4+x^5+x^7 \\
 \underline{1+x^4+x^5} \\
 x^2+x^3+x \\
 \underline{1+x^2+x^3+x} \\
 x+x^2+x^4 \\
 \underline{1+x+x^3} \\
 \underline{1+x+x^3} \\
 0
 \end{array}$$

$P(x)$  divides  $(1-x^7)$   
 $\Rightarrow$  period is  $\underline{7}$ .

- Definition: If the sequence generated by an  $n$ -stage LFSR has period  $2^n - 1$ , then it is called maximal-length sequence.
- Definition: The characteristic polynomial associated with a maximal-length sequence is called a primitive polynomial.
- Definition: An irreducible polynomial is one that cannot be factored (i.e., not divisible by any other polynomial other than 1 and itself).
- Theorem: An irreducible polynomial  $P(x)$  of degree  $n$  satisfies the conditions:
  1. For  $n \geq 2$ ,  $P(x)$  has an odd number of terms including the 1 term
  2. For  $n \geq 4$ ,  $P(x)$  must divide (evenly) into  $1 + x^k$ , where  $k = 2^n - 1$
- Theorem: An irreducible polynomial is primitive if the smallest positive integer  $k$  that allows the polynomial to divide evenly into  $1 + x^k$  occurs for  $k = 2^n - 1$ , where  $n$  is the degree of the polynomial.

# Primitive Polynomials

## Examples

$n$	$\lambda_2(n)$
1	1
2	1
4	2
8	16
16	2048
32	67108864

Figure 10.13 Number of primitive polynomials of degree  $n$

1: 0	13: 4 3 1 0	25: 3 0
2: 1 0	14: 12 11 1 0	26: 8 7 1 0
3: 1 0	15: 1 0	27: 8 7 1 0
4: 1 0	16: 5 3 2 0	28: 3 0
5: 2 0	17: 3 0	29: 2 0
6: 1 0	18: 7 0	30: 16 15 1 0
7: 1 0	19: 6 5 1 0	31: 3 0
8: 6 5 1 0	20: 3 0	32: 28 27 1 0
9: 4 0	21: 2 0	33: 13 0
10: 3 0	22: 1 0	34: 15 14 1 0
11: 2 0	23: 5 0	35: 2 0
12: 7 4 3 0	24: 4 3 1 0	36: 11 0

Figure 10.14 Exponents of terms of primitive polynomials



## LFSRs as Signature Analyzers


$$- P(x) = 1 + \sum_{i=1}^n c_i x^i$$

$$- P^*(x) = 1 + \sum_{i=1}^n c_i x^{n-i}$$

$$- \frac{G(x)}{P^*(x)} = Q(x) + \frac{R(x)}{P^*(x)}$$

$$\text{or } G(x) = Q(x) P^*(x) + R(x)$$

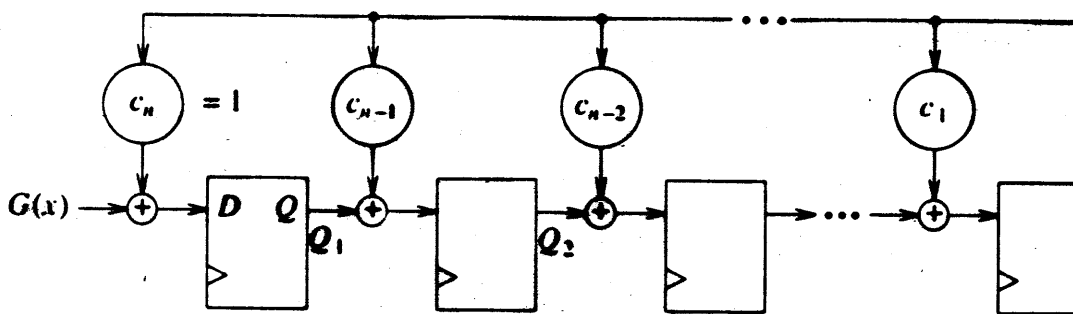- The input sequence  $\{a_m\}$  is represented by  $G(x)$  and output sequence by  $Q(x)$
  - Highest degree of  $G(x)$  is first bit to enter LFSR
  - Highest degree of  $Q(x)$  is first output bit produced  $n$  clock cycles later
- Type 2 LFSR




Initial state:  $I(x) = 0$

Final state:  $R(x)$

# Shift Register Polynomial
 
## Division

- Type 1 LFSR performs polynomial division & produces correct quotient. However, contents of LFSR is not the remainder.



(a)

→  
Input sequence: 11110101 (8 bi)  
 $G(x) = x^7 + x^6 + x^5 + x^4 + x^2 + 1$

(b)

Time	Input stream	Register contents	Output stream
		1 2 3 4 5	
0	1 0 1 0 1 1 1 1	0 0 0 0 0	← Initial state
1	1 0 1 0 1 1 1 1	1 0 0 0 0	
⋮	⋮	⋮	
5	1 0 1	0 1 1 1 1	
6	1 0	0 0 0 1 0	1
7	1	0 0 0 0 1	0 1
8	Remainder →	0 0 1 0 1	1 0 1
		$\underbrace{1 \ x \ x^2 \ x^3 \ x^4}$	$\underbrace{\hspace{2cm}}$
		Remainder	Quotient
		$R(x) = x^2 + x^4$	$1 + x^2$

(c)

**Figure 10.16** Polynomial division

## Error Polynomial & Masking

- Let  $E(x)$  be an error polynomial i.e. each non-0 coefficient represents an error in corresponding bit position
- Example:
  - Assume correct response  $R_0 = 10111$
  - Let erroneous response be  $R' = 11101$
  - Difference or error polynomial is 01010
  - Thus,  $G_0(x) = x^4 + x^2 + x + 1$
  - $G'(x) = x^4 + x^3 + x^2 + 1$
  - $E(x) = x^3 + x$
- $G'(x) = G(x) + E(x)$  (modulo 2)
- Since  $G(x) = Q(x)P^*(x) + R(x)$ , an undetectable response sequence satisfies
$$G'(x) = G(x) + E(x) = Q'(x)P^*(x) + R(x)$$
$$\Rightarrow G(x) \text{ and } G'(x) \text{ produce same remainder}$$

Theorem: Let  $R(x)$  be generated signature for an input  $Q(x)$  using LFSR with charact. polyn.  $p(x)$ . For an error polynomial  $E(x)$ ,  $Q(x)$  and  $Q'(x) = Q(x) + E(x)$  have the same signature  $E(x)$  is a multiple of  $p(x)$ .

- Both type 1 & type 2 LFSRs can be used to generate a signature  $R(x)$ .

Theorem: For an input data stream of length  $m$ , if all possible error patterns are equally likely, then the probability of masking in  $n$ -bit signature is:

$$P(M) = \frac{2^{m-n} - 1}{2^m - 1}$$


for  $m \gg n$ ,  $P(M) \approx 2^{-n}$

- Note that  $P(x)$  has  $2^{m-n} - 1$  non-0 multiples of degree less than  $m$

Theorem An LFSR signature analyzer based on a polynomial with two or more non-0 coefficients detects all single-bit errors.
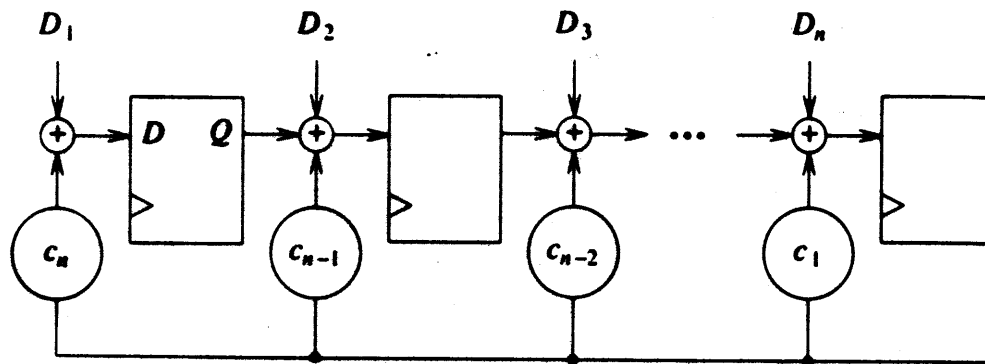
## Multiple-Input Signature Register


- Signature analysis can be extended to testing multiple-output circuits
- Operates as  $n$  single-input signature analyzers



- Assuming all error patterns are equally likely, prob. of error masking is  $\approx 2^{-n}$ .
- Increasing effectiveness of signature analysis:
  - Increase MISR length
  - test can be repeated using different feedback polynomial
  - test can be repeated after changing test vectors order, thus producing different error polynomial
  - periodically sampling signature analyzer output
 
## Implementation Issues

- Often desirable to modify a functional reg to operate as signature analyzer



- clocking  $C \leftarrow B \Rightarrow$  parallel load (b)
- when  $S/T = 0$ , clocking  $A \leftarrow B \Rightarrow$  scan reg
- when  $S/T = 1$ ,  $S = \dots \Rightarrow$  MISR

- LDD double-latch SRL as a storage cell for signature analyzer based on type1 LFSR

