

Name: Key


Id#

COE 464, Term 042
Testing of Digital Circuits

Quiz# 1

Date: Sunday, Feb. 27, 2005

Q1. Consider the circuit given below:

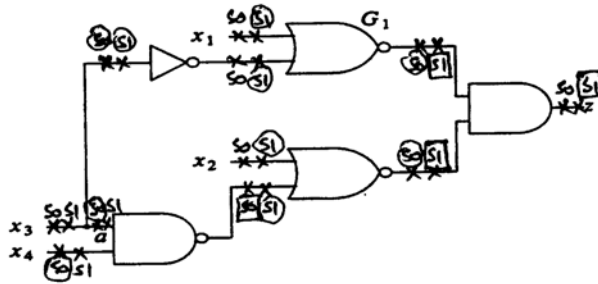

- Find a Boolean expression for the set of all tests that detect the fault x_3 s-a-0.
- Mark on the circuit all the possible **single stuck-at faults** using the symbol s_0 for stuck-at-0 faults and the symbol s_1 for stuck-at-1 faults.
- Mark on the circuit all the single stuck-at faults that can be eliminated due to **Fault Equivalence** relation by drawing a circle around them.
- Mark on the circuit all the single stuck-at faults that can be eliminated due to **Fault Dominance** relation by drawing a square around them.

$$(c) \quad Z = (x_1 + \bar{x}_3) \cdot (x_2 + \overline{x_3 x_4}) = (\bar{x}_1 \cdot x_3) \cdot (\bar{x}_2 \cdot x_3 \cdot x_4) \\ = \bar{x}_1 \bar{x}_2 x_3 x_4$$

$$Z_f = 0$$

Set of all test sets that detect the fault x_3 s-a-0

$$= Z \oplus Z_f = \bar{x}_1 \bar{x}_2 x_3 x_4$$