


# COE 571 Digital System Testing

Term 072

HW# 2

Due date: Tuesday, March 25

 - Q.1.** Given a manufacturing process with a certain yield  $Y=70\%$ . Determine the minimum required fault coverage for achieving a defect level of 1 chip per a 1000. Use the Williams and Brown model and assume that fault coverage is equal to the defect coverage as an approximation.
- Q.2.** Considering the circuit shown below and the following fault list  $\{a_0, a_1, b_0, b_1, c_1, d_1, g_0, g_1, e_1, h_1, i_1, f_1, j_1, k_1, l_1, l_0\}$ , determine the faults detected by the test vector 11 based on each of the following methods. Show the details of each method.



- (i) Deductive fault simulation.
- (ii) Critical path tracing.
- (iii) Parallel fault simulation.
- (iv) Verify your answer of part (ii) using the CPT implementation given in class using the following command: `hope -t circuit.hope -C circuit.log -L 7 circuit.bench`. Note that `circuit.hope` is the file containing the test vectors, `circuit.log` is the file that will contain the results, and `circuit.bench` is the file containing the circuit.
- (v) Verify your answer of parts (i) & (iii) by simulating the given test vector using PROOFS.