


# COE 571 Digital System Testing

Term 072

HW# 5


Due date: Wednesday, June 4, 2008

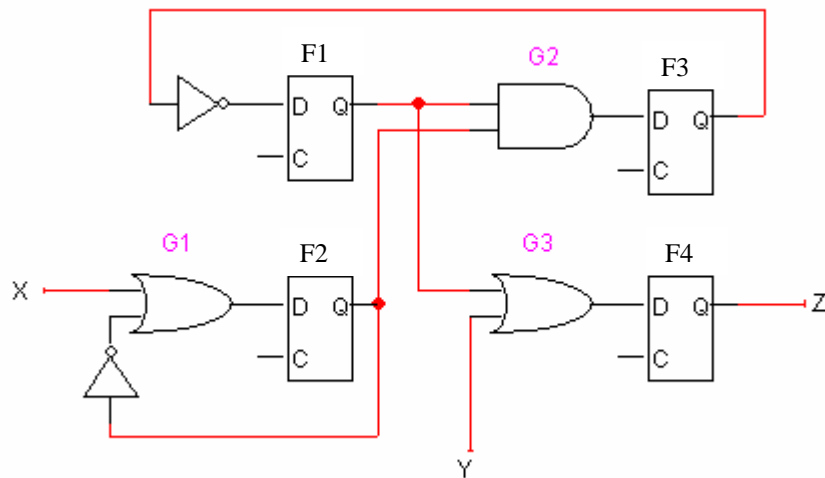- Q.1.** Consider the sequential circuit shown below, which has two primary inputs X and Y, and one primary output Z, and four D-FFs:



- (i) Convert the circuit into a full-scanned circuit using multiplexed data FF. Then, explain how the fault G2 stuck-at-0 can be detected by the full-scanned circuit.
- (ii) Suppose that a partial scan design is to be constructed by scanning a single flip flop. Which of the flip-flops you will select to be scanned? Justify your answer. What type of scan flip flop you will use for partial scan design?
- (iii) Assume that to enhance the testability of the circuit, it is required to add an observation point on the Q output of F2, a 0-injection control point on the output of G2, and both a 0 and 1 injection on the output of G3. Modify the design so that it has the desired features such that the control and observation points are driven by a scan register. Assume that during the scan operation, the normal state of the circuit should not be disturbed.
- (iv) Show a boundary scan implementation of the circuit including scanning all the flip-flops in the design.

 - Q.2.** Given the characteristic polynomial  $p(x)=1+x^2+x^3$ :
- (i) Is  $p(x)$  a primitive polynomial? Justify your answer.
  - (ii) Show a Type 1 LFSR implementation of  $p(x)$ , and determine the sequence generated by the LFSR.
  - (iii) Show a Type 2 LFSR implementation of  $p(x)$ , and determine the sequence generated by the LFSR.
  - (iv) Determine the reciprocal polynomial  $p^*(x)$ .
  - (v) Show a Type 2 LFSR implementation of  $p^*(x)$ , and determine the sequence generated by the LFSR. Verify that it produces the reverse of the sequence generated by the one in (iii).
- Q.3.** Consider a type-2 SISR with characteristic polynomial  $p(x)=1+x+x^2$ . Suppose that the following fault free output response is generated by a circuit: 10110111. Determine whether the following erroneous output sequences will be detected or not. Justify your answer:
- (i) 10110000.
  - (ii) 10111010.
  - (iii) 01110111.
- Q.4.** Consider the circuit shown below, where a 3-stage LFSR is feeding a scan chain of length 8. Assume that the scan chain drives the gate G1 as shown and that G1 is connected to a primary output. Determine whether the indicated single stuck-at fault can be detected by the LFSR or not. If a fault can be detected, determine the seed of the LFSR to generate the test for the fault.



- Q.5.** OPUS is a partial scan package based on cycle breaking and testability measures. Consider the sequential circuit s15850.bench with 77 inputs, 150 outputs and 534 FFs.
- (i) Perform full scan of the circuit using the command *fullscan* and determine the fault coverage and CPU time. This command converts scanned FFs into PIs and POs.
  - (ii) Perform full scan of the circuit using the command *addmux -scan*. This command adds MUXs to scanned FFs and places them in a single scan chain. Determine the obtained fault coverage and CPU time, and compare them to what you obtained in (i). Comment on your observations.
  - (iii) Perform partial scan of the circuit scanning 20%, 30%, and 50% using each of the following commands. Compare the fault coverage and CPU time for each case. Use the *makescan* command to convert selected FFs to PIs and POs.

*One.*      *Opus -n -i*

*Two.*     *Opus -t -i*

*Three.*    *Opus -t*