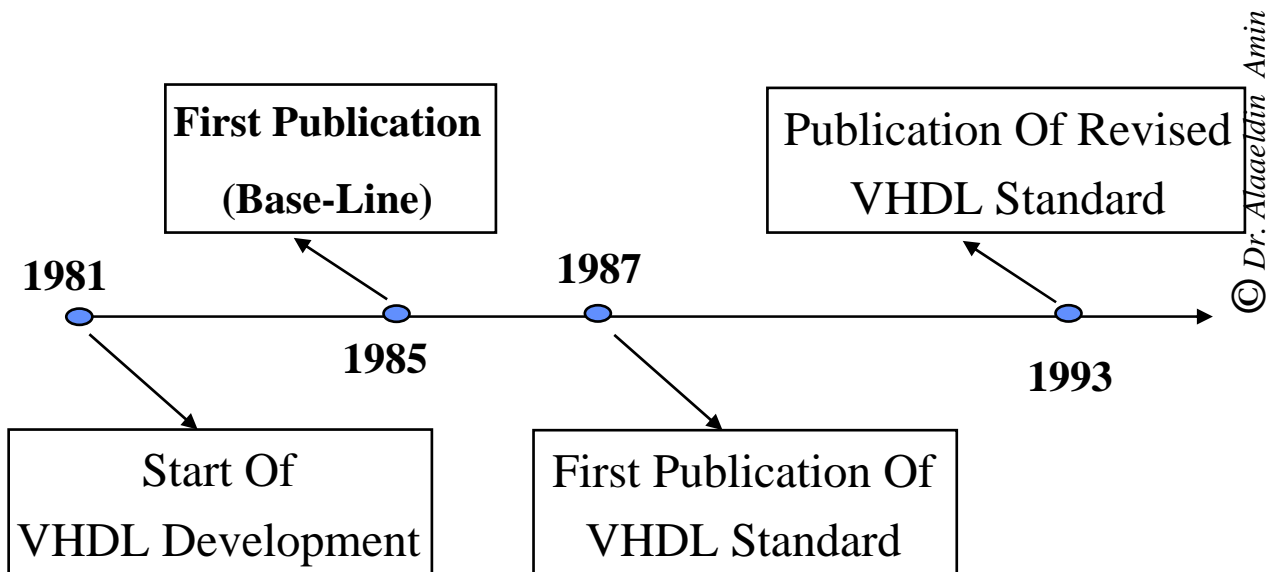


Hardware Modeling & Synthesis Using VHDL

- **VHDL = VHSIC Hardware Description Language**

Very **H**igh **S**peed **I**ntegrated **C**ircuits




Background

- **OBJECTIVES: Provide a Standard Medium For**
 - Design Modeling
 - Design Documentation
- VHDL is an **IEEE Standard (Language Standard)**
 - IEEE VHDL-87
 - IEEE VHDL-93
- VHDL-93 is Upward Compatible with the VHDL-87 (Minor Differences May Require Code Modification)
- Requires **Simulation** and **Synthesis** Tools
- By The End of 1995, Most Simulation Tools Have Incorporated Support for the VHDL-93
- VHDL Is Also Used For Design Synthesis

VHDL Advantages


- **Modular**
- **Hierarchical**, Allows Design Description :
 - TOP - DOWN,
 - BOTTOM - UP,
- **Portable**
- Can Describe the Same Design Entity using More than one View (Domain):
 - The Behavioral View (e.g. as an algorithm, Register-Transfer (Data Flow), Input-Output Relations, etc)
 - The Structural View.
- This Allows Investigation of Design Alternatives of the Same Entity
- It Also Allows Delayed Detailed Implementations.
- Can Model Systems at Various **Levels of Abstraction** (System, chip RTL, Logic (Gate))
- VHDL Can be Made to **Simulate Timing** At Reasonable Accuracy.

VHDL synthesis

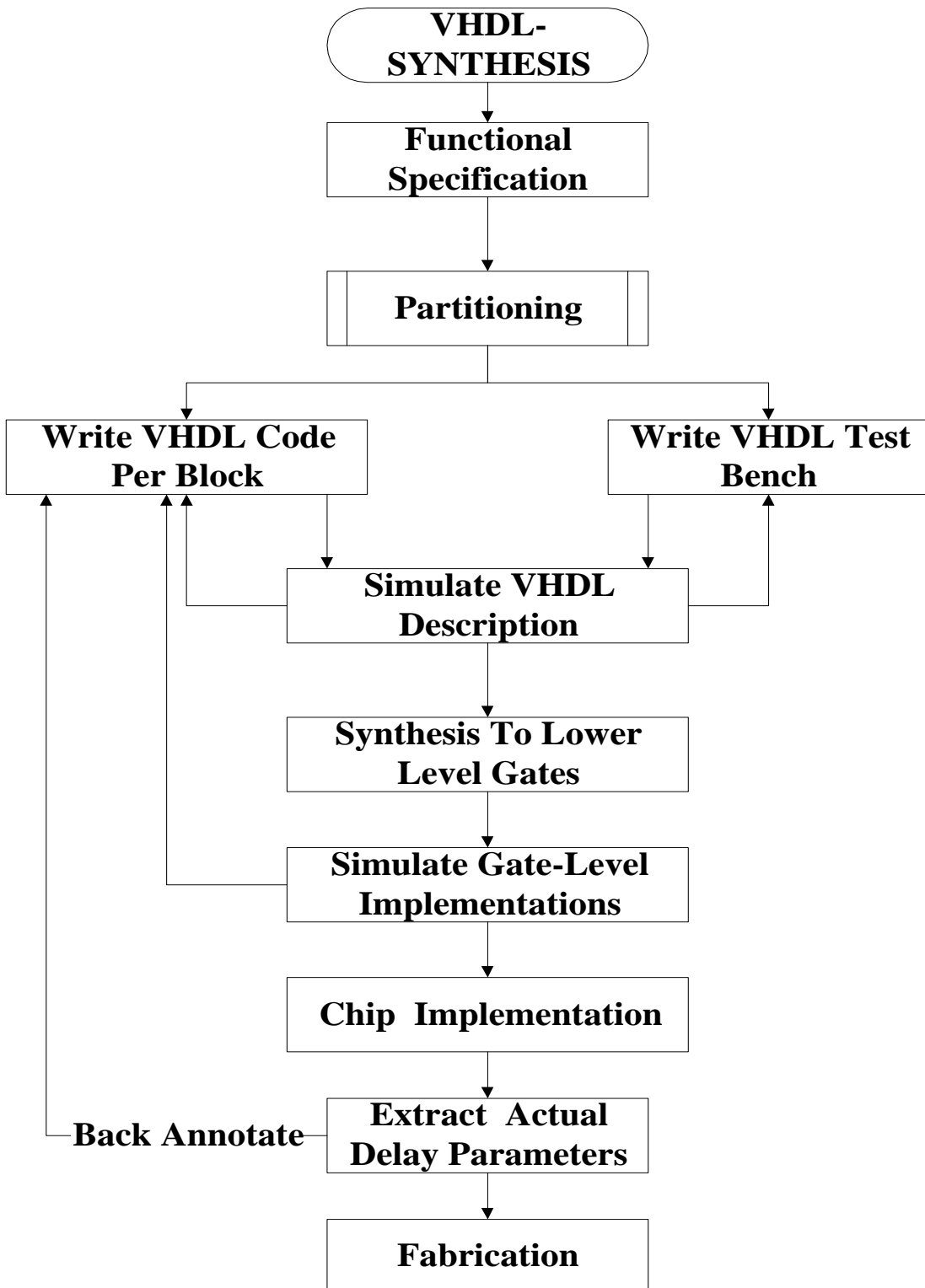


Hardware MOdeling using vhdl

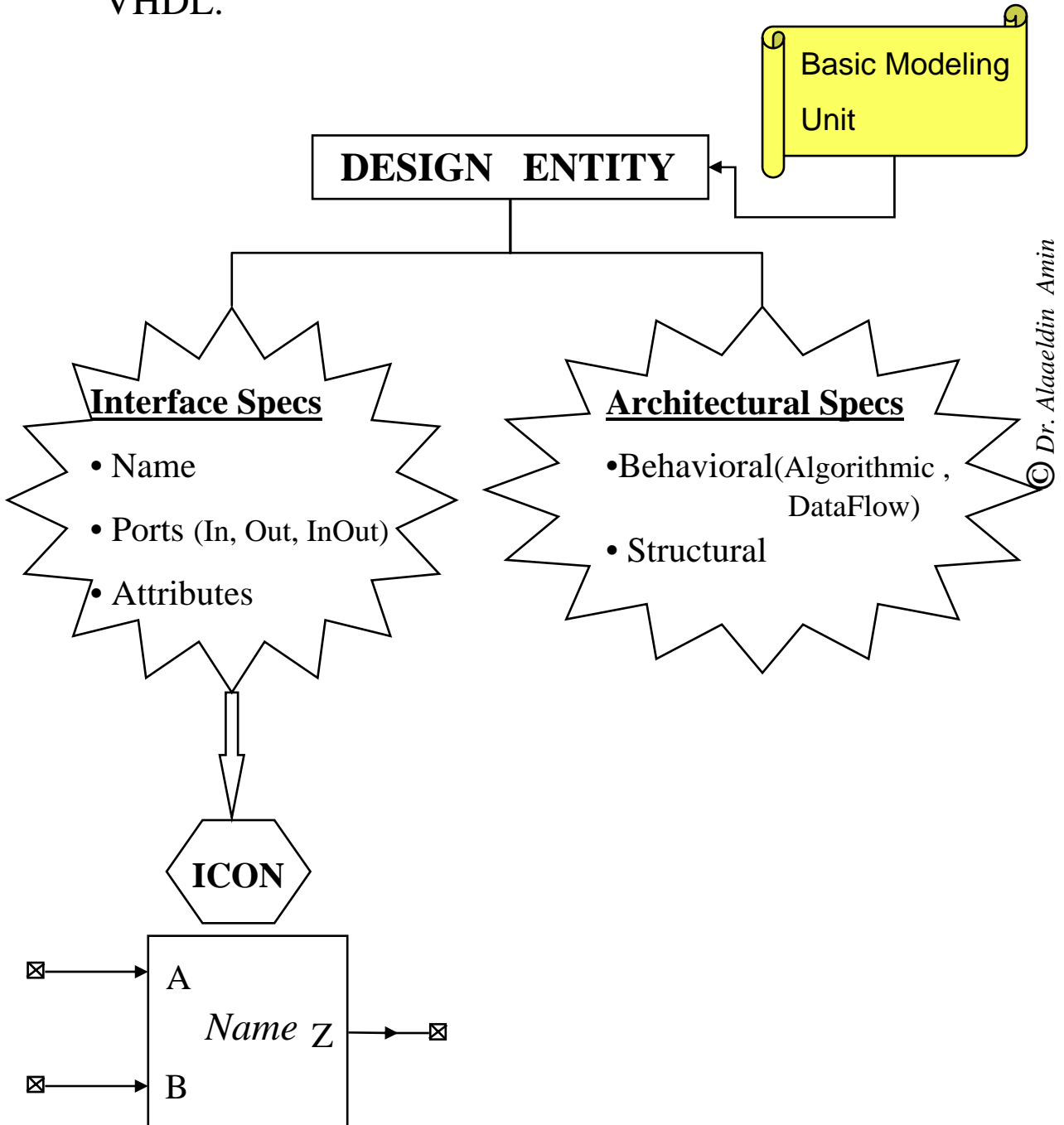- VHDL is NOT CaSe-SeNsItIvE , Thus:
Begin = begin = beGiN
- Semicolon “ ; ” Terminates Declarations or Statements.
- Line Feeds and Carriage Returns are not Significant in VHDL.




Example

“Ones Count CIRCUIT”

 


- Value of **C1 C0** = No. of Ones in the Inputs **A2, A1, and A0**
- **C1** is the Majority Function (=1 *IFF* Two or More Inputs =1)
- **C0** is a 3-Bit Odd-Parity Function (OPAR3))
- $C1 = A1 A0 + A2 A0 + A2 A1$
- $C0 = A2 A1' A0' + A2' A1' A0 + A2 A1 A0 + A2' A1 A0'$

© Dr. Alaaeldin Amin

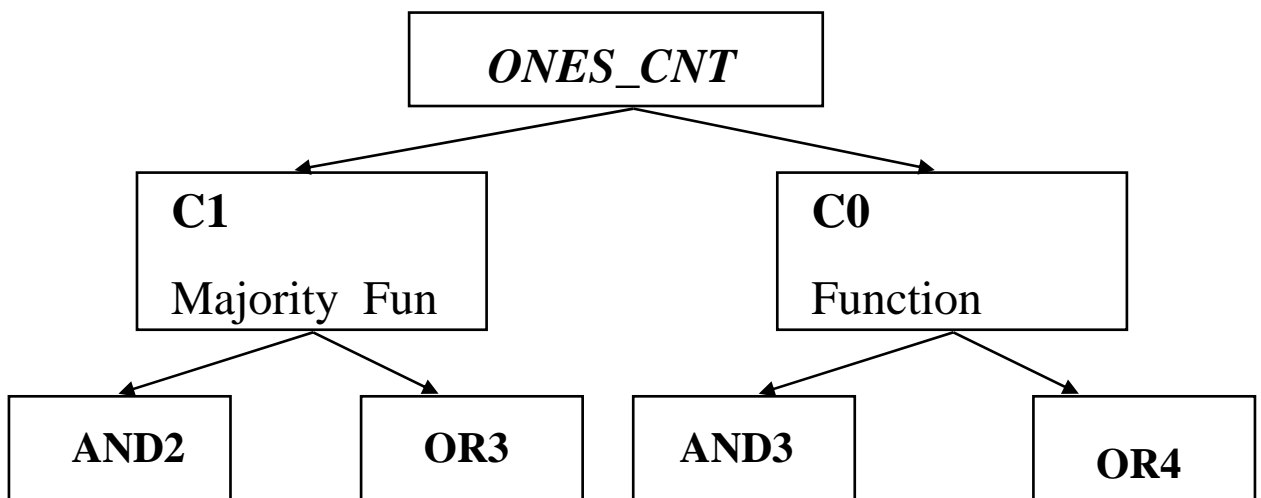

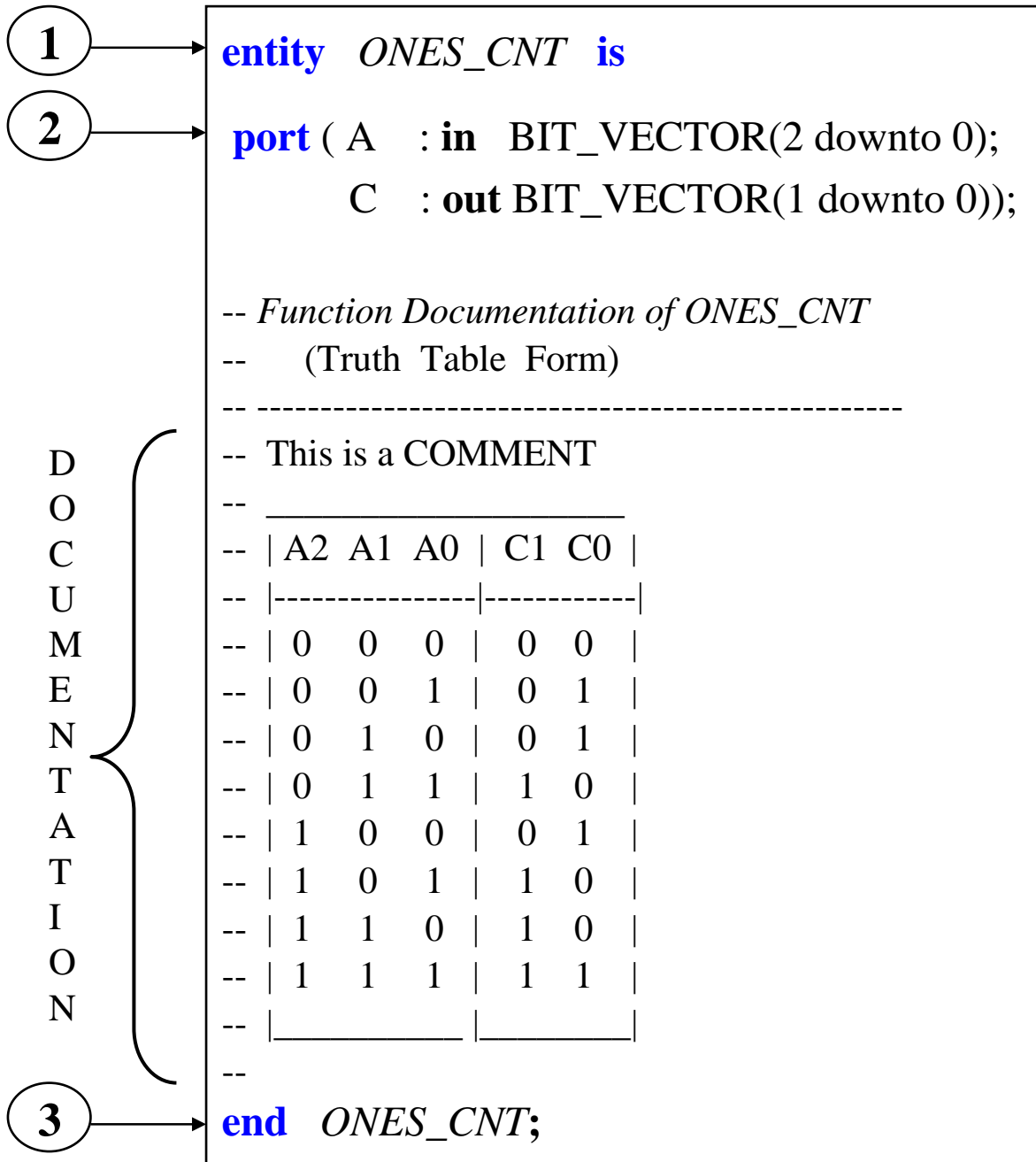Example “Ones Count CIRCUIT INTERFACE SPECS



**example "Ones Count CIRCUIT
Architectural Body
((((Behavioral view-1))))**

architecture *Algorithmic* of *ONES_CNT* is

begin

Process(A) -- Sensitivity List Contains only Vector A
Variable num: INTEGER range 0 to 3;

begin

num :=0;

For i in 0 to 2

Loop

IF A(i) = '1' **then**

num := num+1;

end if;

end Loop;

--

-- Transfer "num" Variable Value to a SIGNAL

--

CASE num **is**

→ **WHEN** 0 => C <= "00";

→ **WHEN** 1 => C <= "01";

→ **WHEN** 2 => C <= "10";

→ **WHEN** 3 => C <= "11";

end CASE;

--

end process;

end *Algorithmic*;

example “Ones Count CIRCUIT

Architectural Body (Behavioral (Data Flow) view - 2)

- $C1 = A1 A0 + A2 A0 + A2 A1$
- $C0 = A2 A1' A0' + A2' A1' A0 + A2 A1 A0 + A2' A1 A0'$

architecture *Two_Level* of *ONES_CNT* is

begin

```
C(1) <=(A(1) and A(0)) or (A(2) and A(0))
      or (A(2) and A(1));
```

--

```
C(0) <= (A(2) and not A(1) and not A(0))
      or (not A(2) and not A(1) and A(0))
      or (A(2) and A(1) and A(0))
      or (not A(2) and A(1) and not A(0));
```

end *Two_Level*;

Example “Ones Count CIRCUIT

Architectural Body (Behavioral (Data Flow) view - 3) Using Functions

```
architecture Macro of ONES_CNT is  
  
begin  
  
    C(1) <= MAJ3(A);  
    --  
    C(0) <= OPAR3(A);  
  
end Macro ;
```

© Dr. Alaaeldin Amin

- Functions OPAR3 and MAJ3 Must Have Been Declared and Defined Previously

example "Ones Count CIRCUIT

Architectural Body ((((Behavioral view -4))))

architecture *Truth_Table* of *ONES_CNT* is

```
begin
```

```
--
```

```
Process(A) -- Sensitivity List Contains only Vector A  
Variable num: BIT_VECTOR(2 downto 0);
```

```
begin
```

```
num :=A;
```

```
CASE num is
```

```

→ WHEN "000" => C <= "00";
→ WHEN "001" => C <= "01";
→ WHEN "010" => C <= "01";
→ WHEN "011" => C <= "10";
→ WHEN "100" => C <= "01";
→ WHEN "101" => C <= "10";
→ WHEN "110" => C <= "10";
→ WHEN "111" => C <= "11";
```

```
end CASE;
```

```
--
```

```
end process;
```


```
end Truth_Table;
```

VHDL STRUCTURAL DESCRIPTION

“Ones Count CIRCUIT example ”

- $C1 = A1 A0 + A2 A0 + A2 A1 = \mathbf{MAJ3}(A)$
- $C0 = A2 A1' A0' + A2' A1' A0 + A2 A1 A0 + A2' A1 A0' = \mathbf{OPAR3}(A)$

Structural Design Hierarchy

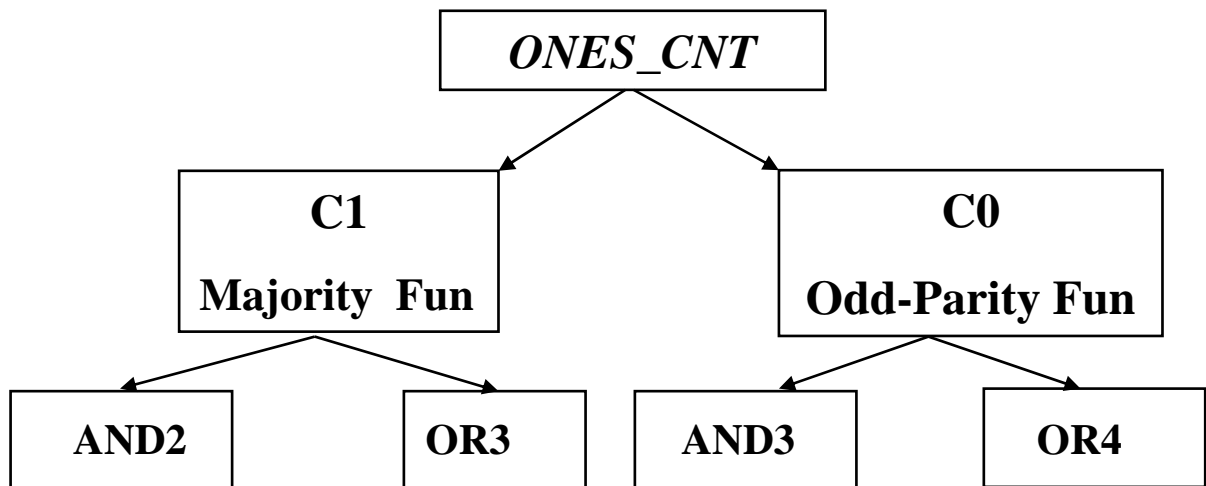

© Dr. Alaaeldin Amin


```

entity MAJ3 is
  PORT( X: in BIT_Vector(2 downto 0);
        Z: out BIT);
end MAJ3;
  
```

```

entity OPAR3 is
  PORT( X: in BIT_Vector(2 downto 0);
        Z: out BIT);
end OPAR3;
  
```

VHDL STRUCTURAL DESCRIPTION

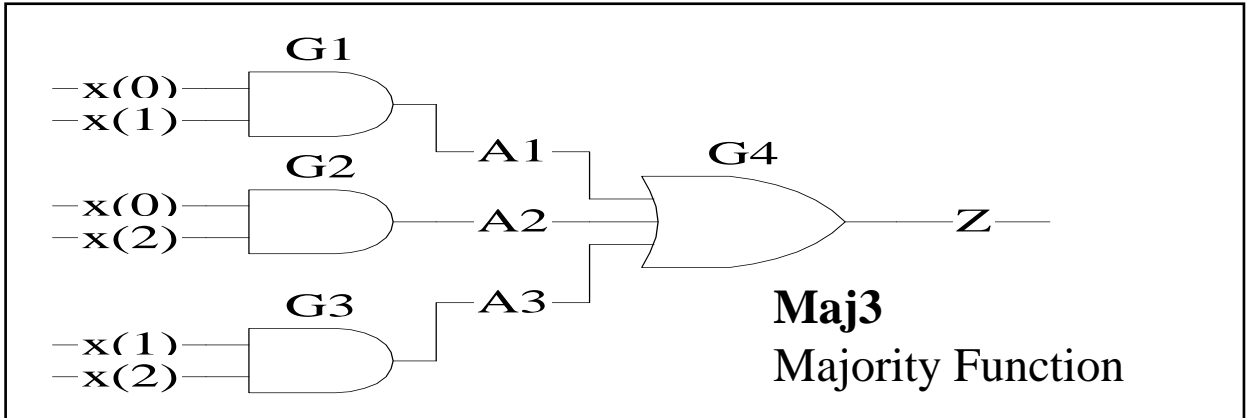

architecture Structural of MAJ3 is

COMPONENT AND2

PORT(I1, I2: in BIT;
O: out BIT);

END COMPONENT;

COMPONENT OR3

PORT(I1, I2, I3: in BIT;
O: out BIT);

END COMPONENT;

--

SIGNAL A1, A2, A3: BIT; *Declare Maj3 Local Signals*

begin

-- *Instantiate Gates*

g1: AND2 PORT MAP (X(0), X(1), A1);

g2: AND2 PORT MAP (X(0), X(2), A2);

g3: AND2 PORT MAP (X(1), X(2), A3);

g4: OR3 PORT MAP (A1, A2, A3, Z);

end Structural;

*Declare Components
To Be Instantiated*

*Wiring of
Maj3
Compts.*

entity *OPAR3* is

**PORT(X: in BIT_Vector(2 downto 0);
Z: out BIT);**

end *OPAR3*;

architecture Structural of *OPAR3* is

COMPONENT INV

**PORT(Ipt: in BIT;
Opt: out BIT);**

END COMPONENT;

COMPONENT NAND3

**PORT(I1, I2, I3: in BIT;
O: out BIT);**

END COMPONENT;

COMPONENT NAND4

**PORT(I1, I2, I3, I4: in BIT;
O: out BIT);**

END COMPONENT;

SIGNAL A1B, A2B, A0B, Z1, Z2, Z3, Z4: BIT;

begin

-- Instantiate Gates

g1: INV PORT MAP (X(0), A0B);

g2: INV PORT MAP (X(1), A1B);

g3: INV PORT MAP (X(2), A2B);

g4: NAND3 PORT MAP (X(2), A1B, A0B, Z1);

g5: NAND3 PORT MAP (X(0), A1B, A2B, Z2);

g6: NAND3 PORT MAP (X(0), X(1), X(2), Z3);


g7: NAND3 PORT MAP (X(1), A2B, A0B, Z4);

g8: NAND4 PORT MAP (Z1, Z2, Z3, Z4, Z);

end Structural;

Interface Specs

*Architecture
Body*

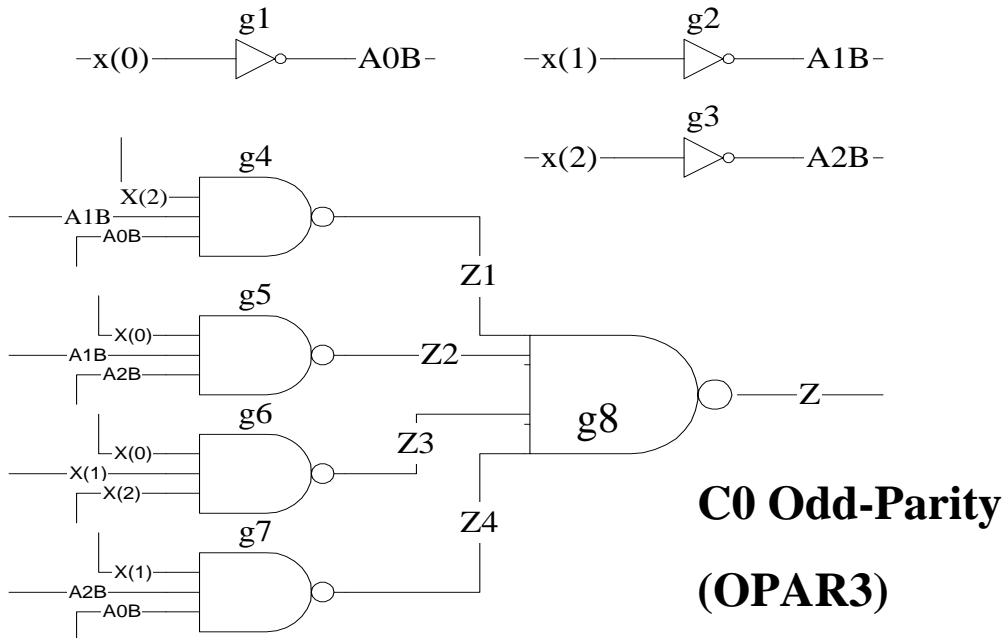

architecture Structural of *OPAR3* is
Component INV

PORT(Ipt: in BIT; Opt: out BIT);

end Component ;

Component NAND3

PORT(I1, I2, I3: in BIT; O: out BIT);

end Component ;

Component NAND4

PORT(I1, I2, I3, I4: in BIT; O: out BIT);

end Component ;

--

SIGNAL A1B, A2B, A0B, Z1, Z2, Z3, Z4: BIT;

begin

g1: INV PORT MAP (X(0), A0B);

g2: INV PORT MAP (X(1), A1B);

g3: INV PORT MAP (X(2), A2B);

g4: NAND3 PORT MAP (X(2), A1B, A0B, Z1);

g5: NAND3 PORT MAP (X(0), A1B, A2B, Z2);

g6: NAND3 PORT MAP (X(0), X(1), X(2), Z3);

g7: NAND3 PORT MAP (X(1), A2B, A0B, Z4);

g8: NAND4 PORT MAP (Z1, Z2, Z3, Z4, Z);

end Structural;

Top Structural level of ones_cnt

architecture Structural of *ONES_CNT* is
COMPONENT MAJ3

PORT(X: in BIT_Vector(0 to 2);
 Z: out BIT);

END COMPONENT;

COMPONENT OPAR3

PORT(X: in BIT_Vector(0 to 2);
 Z: out BIT);

END COMPONENT;

--

begin

-- Instantiate Components

--

c1: MAJ3 PORT MAP (A, C(1));

c2: OPAR3 PORT MAP (A, C(0));

end Structural;

Behavioral definition of lower level components

```
entity INV is
    PORT( Ipt: in BIT; Opt: out BIT);
end INV;
--
architecture behavior of INV is
begin
    Opt <= not Ipt;
end behavior;
```

```
entity NAND2 is
    PORT( I1, I2: in BIT; O: out BIT);
end NAND2;
--
architecture behavior of NAND2 is
begin
    O <= not (I1 and I2);
end behavior;
```

⋮

Similarly Other Lower Level Gates Are Defined