


COE 202, Term 162

Digital Logic Design

Assignment# 1

Due date: Saturday, March 18, 2017

 - Q.1.** Consider the combinational circuit given below which has three inputs C1, C0, and X, three outputs C1+, C0+ and Y:



- (i) Write a Verilog model to model the combinational circuit using either primitive gates or assign statement.
- (ii) Write a test bench to test the correctness of your Verilog model by applying all the input patterns to the circuit. Apply consecutive inputs patterns after a delay of 100ps. Verify the correct functionality of your circuit by deriving the truth table and comparing it with what you got from simulations.
- (iii) Write a Verilog model that instantiates four copies of this circuit and connects C1 and C0 of the first instance to 00, C1+ and C0+ of the first instance to C1 and C0 of the 2nd instance, C1+ and C0+ of the 2nd instance to C1 and C0 of the 3rd instance, and C1+ and C0+ of the 3rd instance to C1 and C0 of the 4th instance.
- (iv) Write a test bench that tests the 4-bit circuit modeled in (iii) that applies the following input patterns to your circuit $(X_3X_2X_1X_0) = \{0001, 0010, 0011, 0100, 0101\}$ and observes the obtained outputs $Y_3Y_2Y_1Y_0$. Can you guess the functionality of the 4-bit circuit?

*This assignment can be solved based on a group of two students. The solution should be well organized. Submit a soft copy of your solution in a zip file including your Verilog models. Your solution should be submitted in a **pdf file** that contains the following items:*

- i. Your name and ID*
- ii. Assignment number*
- iii. Problem statement*
- iv. Your solution*
- v. Include snapshots of simulation output to illustrate the correctness of your models.