


## COE 202, Term 162

### Digital Logic Design

#### Assignment# 1 Solution

Due date: Saturday, March 18, 2017

 - Q.1.** Consider the combinational circuit given below which has three inputs C1, C0, and X, three outputs C1+, C0+ and Y:



- (i) Write a Verilog model to model the combinational circuit using either primitive gates or assign statement.

```
module Cell3XM1 (output C1P, C0P, Y, input C1, C0, X);
```

```
    assign Y = X ~^ C0;
```

```
    assign C0P = C1 ^ (~X & C0);
```

```
    assign C1P = X | (C1 & C0);
```

```
endmodule
```

- (ii) Write a test bench to test the correctness of your Verilog model by applying all the input patterns to the circuit. Apply consecutive inputs patterns after a delay of 100ps. Verify the correct functionality of your circuit by deriving the truth table and comparing it with what you got from simulations.

```

module Cell3XM1_Test();

reg C1, C0, X;
wire C1P, C0P, Y;

Cell3XM1 M1 (C1P, C0P, Y, C1, C0, X);


initial begin
C1=0; C0=0; X=0;
#100 C1=0; C0=0; X=1;
#100 C1=0; C0=1; X=0;
#100 C1=0; C0=1; X=1;
#100 C1=1; C0=0; X=0;
#100 C1=1; C0=0; X=1;
#100 C1=1; C0=1; X=0;
#100 C1=1; C0=1; X=1;
end
endmodule

```

The expected truth table is as follows:

| C1 | C0 | X | C1P | C0P | Y |
|----|----|---|-----|-----|---|
| 0  | 0  | 0 | 0   | 0   | 1 |
| 0  | 0  | 1 | 1   | 0   | 0 |
| 0  | 1  | 0 | 0   | 1   | 0 |
| 0  | 1  | 1 | 1   | 0   | 1 |
| 1  | 0  | 0 | 0   | 1   | 1 |
| 1  | 0  | 1 | 1   | 1   | 0 |
| 1  | 1  | 0 | 1   | 0   | 0 |
| 1  | 1  | 1 | 1   | 1   | 1 |

 The simulation waveform given below matches the expected values shown in the truth table.



- (iii) Write a Verilog model that instantiates four copies of this circuit and connects C1 and C0 of the first instance to 00, C1+ and C0+ of the first instance to C1 and C0 of the 2nd instance, C1+ and C0+ of the 2nd instance to C1 and C0 of the 3rd instance, and C1+ and C0+ of the 3rd instance to C1 and C0 of the 4th instance.

```

module D3XM1 (output Cout1, Cout0, output [3:0] Y, input [3:0] X);

wire [2:0] C1P, C0P;

Cell3XM1 M1 (C1P[0], C0P[0], Y[0], 0, 0, X[0]);
Cell3XM1 M2 (C1P[1], C0P[1], Y[1], C1P[0], C0P[0], X[1]);
Cell3XM1 M3 (C1P[2], C0P[2], Y[2], C1P[1], C0P[1], X[2]);
Cell3XM1 M4 (Cout1, Cout0, Y[3], C1P[2], C0P[2], X[3]);

endmodule

```

- (iv) Write a test bench that tests the 4-bit circuit modeled in (iii) that applies the following input patterns to your circuit  $(X_3X_2X_1X_0) = \{0001, 0010, 0011, 0100, 0101\}$  and observes the obtained outputs  $Y_3Y_2Y_1Y_0$ . Can you guess the functionality of the 4-bit circuit?

```

module D3XM1_Test();

reg [3:0] X;
wire Cout1, Cout0;
wire [3:0] Y;

D3XM1 M1 (Cout1, Cout0, Y, X);

initial begin
X=4'b0001;
#100 X=4'b0010;
#100 X=4'b0011;
#100 X=4'b0100;
#100 X=4'b0101;
end
endmodule

```

The simulation results are shown below and it can be deduced from simulations that the circuit is computing the function  $Y = 3 * X - 1$ .

|                   |      |      |      |      |      |      |
|-------------------|------|------|------|------|------|------|
| /D3XM1_Test/X     | 0101 | 0001 | 0010 | 0011 | 0100 | 0101 |
| /D3XM1_Test/Y     | 1110 | 0010 | 0101 | 1000 | 1011 | 1110 |
| /D3XM1_Test/Cout1 | St0  |      |      |      |      |      |
| /D3XM1_Test/Cout0 | St1  |      |      |      |      |      |