

COE 202, Term 142

Digital Logic Design

Assignment# 2

Due date: Tuesday, March 31

- Q.1.** It is required to design a combinational circuit that computes the equation $Y=3*X$, where X is a 4-bit unsigned number.
- (i) Determine the number of outputs needed for your circuit.
 - (ii) Derive the truth table of your circuit.
 - (iii) Derive minimized equations for your circuit using K-Map method.
 - (iv) Write a Verilog model for modeling your design by using an assign statement for each output.
 - (v) Write a Verilog test bench to test the correctness of your design for the following input values: $X=1$, $X=3$, $X=5$, $X=10$ and $X=15$.

This assignment can be solved based on a group of two students. The solution should be well organized. Submit a soft copy of your solution in a zip file including your Verilog models. Your solution should be submitted in a word file that contains the following items:

- i. Your name and ID
- ii. Assignment number
- iii. Problem statement
- iv. Your solution
- v. Include snapshots of simulation output to illustrate the correctness of your models.