

COE 202, Term 131

Digital Logic Design

Assignment# 2

Due date: Thursday Nov. 28

Q.1. It is required to design a circuit that receives a 4-bit number $A=A_3A_2A_1A_0$ and produces 7-bit output $C= C_7C_6C_5C_4C_3C_2C_1C_0$. The circuit implements the following functions based on the values of the two selection inputs: S1 and S0.

S1 S0	Function
0 0	$C = 2 * A$
0 1	$C = 3 * A$
1 0	$C = 4 * A$
1 1	$C = 5 * A$

- (i) Show the block diagram design of your circuit using MSI components like Adder, Multiplexor, as needed.
- (ii) Model your design in logic works.
- (iii) Test your design and verify its correctness by simulation. Show snapshots of your simulation to demonstrate its correctness. For each function, test at least 2 input combinations of your choice to demonstrate correct functionality.

Include snapshots of simulation output to illustrate the correctness of your circuit. Submit your solution as a word document along with the circuits in one zipped file.