

**COE 202, Term 151**


**Digital Logic Design**

**Assignment# 2 Solution**

**Due date: Sunday, Oct. 31**

**Q.1.** It is required to design an iterative combinational circuit that computes the equation  $Z=3*X-Y$ , where X and Y are n-bit unsigned numbers.

 (i) Determine the number of inputs and outputs needed for your 1-bit cell.



The meaning of the values of  $C_{1i-1}$  and  $C_{0i-1}$  is given in the table below:

$C_{1i-1}$	$C_{0i-1}$	Meaning
0	0	There is no carry or borrow
0	1	There is a carry of 1
1	0	There is a carry of 2
1	1	There is a borrow of 1

(ii) Derive the truth table of your 1-bit cell.

$C_{i-1}$	$C_{0i-1}$	$X_i$	$Y_i$	$C_{1i}$	$C_{0i}$	$Z_i$
0	0	0	0	0	0	0
0	0	0	1	1	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	0	1	1
1	0	0	0	0	1	0
1	0	0	1	0	0	1
1	0	1	0	1	0	1
1	0	1	1	1	0	0
1	1	0	0	1	1	1
1	1	0	1	1	1	0
1	1	1	0	0	1	0
1	1	1	1	0	0	1

(iii) Derive minimized equations for your 1-bit using K-Map method.

	00	01	11	10
00	0 0	1 1	0 3	1 2
01	1 4	0 5	1 7	0 6
11	1 12	0 13	1 15	0 14
10	0 8	1 9	0 11	1 10

$$\begin{aligned}
 Z_i &= C_{0i-1} X_i' Y_i' + C_{0i-1} X_i Y_i + C_{0i-1}' X_i' Y_i + C_{0i-1}' X_i Y_i' \\
 &= C_{0i-1} (X_i' Y_i' + X_i Y_i) + C_{0i-1}' (X_i' Y_i + X_i Y_i') \\
 &= C_{0i-1} (X_i \oplus Y_i)' + C_{0i-1}' (X_i \oplus Y_i) \\
 &= C_{0i-1} \oplus X_i \oplus Y_i
 \end{aligned}$$

	00	01	11	10
00	0 0	1 1	1 3	1 2
01	0 4	0 5	1 7	0 6
11	1 12	1 13	0 15	1 14
10	1 8	0 9	0 11	0 10

$$C0i = C1i-1' C0i-1' Xi + C1i-1' C0i-1' Yi + C1i-1 C0i-1 Xi' + C1i-1 C0i-1 Yi' + C1i-1 Xi' Yi' + C1i-1' Xi Yi$$

$$= C1i-1' C0i-1' (Xi + Yi) + C1i-1 C0i-1 (Xi' + Yi') + C1i-1 Xi' Yi' + C1i-1' Xi Yi$$

	00	01	11	10
00	0 0	1 1	0 3	0 2
01	0 4	0 5	0 7	1 6
11	1 12	1 13	0 15	0
10	0 8	0 9	1 11	1 10

$$C1i = C1i-1 C0i-1 Xi' + C1i-1 C0i-1' Xi + C1i-1' C0i-1' Xi' Yi + C1i-1' C0i-1 Xi Yi'$$

$$= C1i-1 (C0i-1 \oplus Xi) + C1i-1' (C0i-1' Xi' Yi + C0i-1 Xi Yi')$$

- (iv) Write a Verilog model for modeling your 1-bit cell by using an assign statement for each output.

```

module OneBit3X_Y (input C1i_1, C0i_1, Xi, Yi, output C1i,
                  C0i, Zi);

    assign Zi = C0i_1 ^ Xi ^ Yi ;

    assign C0i = ~C1i_1 & ~C0i_1 & (Xi | Yi) | C1i_1 & C0i_1 &
                (~Xi | ~Yi) | C1i_1 & ~Xi & ~Yi | ~C1i_1 & Xi & Yi;

    assign C1i = C1i_1 & (C0i_1 ^ Xi) | ~C1i_1 & (~C0i_1 & ~Xi
                & Yi | C0i_1 & Xi & ~Yi);

endmodule

```

- (v) Write a Verilog model for modeling a 4-bit circuit based on the 1-bit model you have.

```

module FourBit3X_Y (input [3:0] X, Y, output [3:0] Z, output
                  C1_out, C0_out);

    wire [3:0] C1, C0;

    assign C1_out = C1[3];

```

```

assign C0_out = C0[3];

OneBit3X_Y M0 (1'b0, 1'b0, X[0], Y[0], C1[0], C0[0], Z[0]);
OneBit3X_Y M1 (C1[0], C0[0], X[1], Y[1], C1[1], C0[1], Z[1]);
OneBit3X_Y M2 (C1[1], C0[1], X[2], Y[2], C1[2], C0[2], Z[2]);
OneBit3X_Y M3 (C1[2], C0[2], X[3], Y[3], C1[3], C0[3], Z[3]);

endmodule

```

- (vi) Write a Verilog test bench to test the correctness of your design for the following input values: {X=1,Y=1}, {X=3, Y=5}, {X=5, Y=1}, {X=4, Y=15}, and {X=15, Y=0}.

```

module FourBit3X_Ytest();

reg [3:0] X, Y;
wire [3:0] Z;
wire C1_out, C0_out;

FourBit3X_Y M1 (X, Y, Z, C1_out, C0_out);

initial begin
    X=4'd1; Y=4'd1;
    #10 X=4'd3; Y=4'd5;
    #10 X=4'd5; Y=4'd1;
    #10 X=4'd4; Y=4'd15;
    #10 X=4'd15; Y=4'd0;
end
endmodule

```

+/FourBit3X_Ytest/X	1111	0001	0011	0101	0100	1111
+/FourBit3X_Ytest/Y	0000	0001	0101	0001	1111	0000
+/FourBit3X_Ytest/Z	1101	0010	0100	1110	1101	1101
FourBit3X_Ytest/C0_out	St0					
FourBit3X_Ytest/C1_out	St1					