

**COE 202, Term 162**

**Digital Logic Design**

**Assignment# 2 Solution**


**Due date: Sunday, April 9**

**Q.1.** It is required to design an iterative combinational circuit that computes the equation  $Z=2*X-Y$ , where X and Y are n-bit unsigned numbers.

 (i) Determine the number of inputs and outputs needed for your 1-bit cell.

This circuit requires the following 3 pieces of information, which can be encoded using 2 signals:

- No carry or borrow ( $C=0, B=0$ )
- Carry = 1 ( $C=1, B=0$ )
- Borrow = 1 ( $C=0, B=1$ )



(ii) Derive the truth table of your 1-bit cell.

Bin	Cin	X	Y	Bout	Cout	Z
0	0	0	0	0	0	0
0	0	0	1	1	0	1
0	0	1	0	0	1	0
0	0	1	1	0	0	1
0	1	0	0	0	0	1
0	1	0	1	0	0	0
0	1	1	0	0	1	1
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	0	0
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

(iii) Derive minimized equations for your 1-bit using K-Map method.

	00	01	11	10
00	0 0	1 1	1 3	0 2
01	1 4	0 5	0 7	1 6
11	? 12	? 13	? 15	? 14
10	1 8	0 9	0 11	1 10

$$Z = \text{Bin}' \text{Cin}' Y + \text{Cin} Y' + \text{Bin} Y' = \text{Bin}' \text{Cin}' Y + Y' (\text{Cin} + \text{Bin}) = Y \oplus (\text{Cin} + \text{Bin})$$

	00	01	11	10
00	0 0	0 1	0 3	1 2
01	0 4	0 5	1 7	1 6
11	? 12	? 13	? 15	? 14
10	0 8	0 9	0 11	0 10

$$\text{Cout} = \text{Cin} X + \text{Bin}' X Y'$$

	00	01	11	10
00	0 0	1 1	0 3	0 2
01	0 4	0 5	0 7	0 6
11	? 12	? 13	? 15	? 14
10	1 8	1 9	0 11	0 10

$$\text{Bout} = \text{Bin} X' + \text{Cin}' X' Y$$

(iv) Write a Verilog model for modeling your 1-bit cell by using an assign statement for each output.

```
module Cell2XMY (output Bout, Cout, Z, input Bin, Cin, X, Y);
```

```
    assign Z = Y ^ (Cin | Bin);
    assign Cout = Cin & X | ~Bin & X & ~Y;
```

```
assign Bout = Bin & ~X | ~Cin & ~X & Y;
```

```
endmodule
```

- (v) Write a Verilog model for modeling a 4-bit circuit based on the 1-bit model you have.

```
module D2XMY (output Bout, Cout, output [3:0] Z, input [3:0] X, Y);
```

```
wire [2:0] C, B;
```

```
Cell2XMY M1 (B[0], C[0], Z[0], 1'b0, 1'b0, X[0], Y[0]);  
Cell2XMY M2 (B[1], C[1], Z[1], B[0], C[0], X[1], Y[1]);  
Cell2XMY M3 (B[2], C[2], Z[2], B[1], C[1], X[2], Y[2]);  
Cell2XMY M4 (Bout, Cout, Z[3], B[2], C[2], X[3], Y[3]);
```

```
endmodule
```

- (vi) Write a Verilog test bench to test the correctness of your design for the following input values: {X=1,Y=1}, {X=3, Y=2}, {X=5, Y=1}, {X=4, Y=5}, and {X=15, Y=15}.

```
module D2XMY_Test();
```

```
reg [3:0] X, Y;  
wire Bout, Cout;  
wire [3:0] Z;
```

```
D2XMY M1 (Bout, Cout, Z, X, Y);
```

```
initial begin  
X=4'b0001; Y=4'b0001;  
#100 X=4'b0011; Y=4'b0010;  
#100 X=4'b0101; Y=4'b0001;  
#100 X=4'b0100; Y=4'b0101;  
#100 X=4'b1111; Y=4'b1111;  
end  
endmodule
```

The simulation results are shown below and it is clear that the circuit is implementing the function  $Z=2*X-Y$  correctly.

	1111	0001	0011	0101	0100	1111
/D2XMY_Test/X	1111	0001	0011	0101	0100	1111
/D2XMY_Test/Y	1111	0001	0010	0001	0101	1111
/D2XMY_Test/Z	1111	0001	0100	1001	0011	1111
/D2XMY_Test/Cout	St0					
/D2XMY_Test/Bout	St0					