

*King Fahd University of Petroleum and Minerals*  
*College of Computer Science and Engineering*  
*Computer Engineering Department*

**COE 202: Digital Logic Design (3-0-3)**

**Term 151 (Fall 2015)**

**Final Exam**

**Sunday Dec. 20, 2015**

**7:00 p.m. – 9:30 p.m.**

**Time: 150 minutes, Total Pages: 12**

**Name: KEY ID: \_\_\_\_\_ Section: \_\_\_\_\_**

**Notes:**

- Do not open the exam book until instructed
- Calculators are not allowed (basic, advanced, cell phones, etc.)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

<b>Question</b>	<b>Maximum Points</b>	<b>Your Points</b>
<b>1</b>	<b>12</b>	
<b>2</b>	<b>14</b>	
<b>3</b>	<b>10</b>	
<b>4</b>	<b>8</b>	
<b>5</b>	<b>9</b>	
<b>6</b>	<b>7</b>	
<b>Total</b>	<b>60</b>	

**Question 1.**

**(12 Points)**

The shown synchronous sequential circuit has a single input X and a single output Y. Answer the following questions:

(i) The circuit is MOORE  
(Moore / Mealy)


**(1 point)**

(ii) Derive Boolean expressions for the flip-flop D-inputs, i.e. D<sub>A</sub> and D<sub>B</sub> and the output Y.


**(3 points)**

$D_A = XA + XB = X.(A+B)$   
 $D_B = XA + XB' = X.(A+B')$   
 $Y = AB$

 (iii) Fill in the state table of this circuit and draw the corresponding state diagram **(6 Points)**



PS AB	NS (A <sup>+</sup> B <sup>+</sup> )		Y	
	X=0	X=1	X=0	X=1
00	0 0	0 1	0	0
01	0 0	1 0	0	0
11	0 0	1 1	1	1
10	0 0	1 1	0	0

 

(iv) For a starting state of (10), what is the resulting output sequence (Y) for an applied input sequence (X) of {1→1→0}? **(2 points)**

PS	(10)	(11)	(11)	(00)
X	1	1	0	Don't care
Y	0	1	1	0

**Question 2.**

**(14 Points)**

Consider the following state transition table for a synchronous sequential circuit that increments a binary number by two, i.e.  $Z=X+2$ . The circuit has a single input  $X$ , a single output  $Z$ , and two state variables  $Y_1$ , and  $Y_0$ . The states are encoded using binary codes **00**, **01**, **10**. The **reset state** is **10**.

PS ( $Y_1 Y_0$ ) <sup>t</sup>	NS ( $Y_1 Y_0$ ) <sup>t+1</sup>		Z	
	X = 0	X = 1	X = 0	X = 1
0 0	0 0	0 0	0	1
0 1	0 0	0 1	1	0
1 0	0 1	0 1	0	1

(i)

- Using D-FFs and **minimal** combinational logic, determine the equations for the D-FF inputs and the output Z for this circuit.
- Draw the resulting circuit and add the required logic to achieve **Synchronous Reset**, to reset the machine to state  $Y_1Y_0=10$  when a Reset input is asserted.

**(7 points)**


	00	01	11	10
0	0 0	1 1	? 3	0 2
1	1 4	0 5	? 7	1 6

$$Z = X' Y_0 + X Y_0' = X \oplus Y_0$$

	00	01	11	10
0	0 0	0 1	? 3	1 2
1	0 4	1 5	? 7	1 6

$$D_0 = Y_1 + X Y_0$$

$$D_1 = 0$$

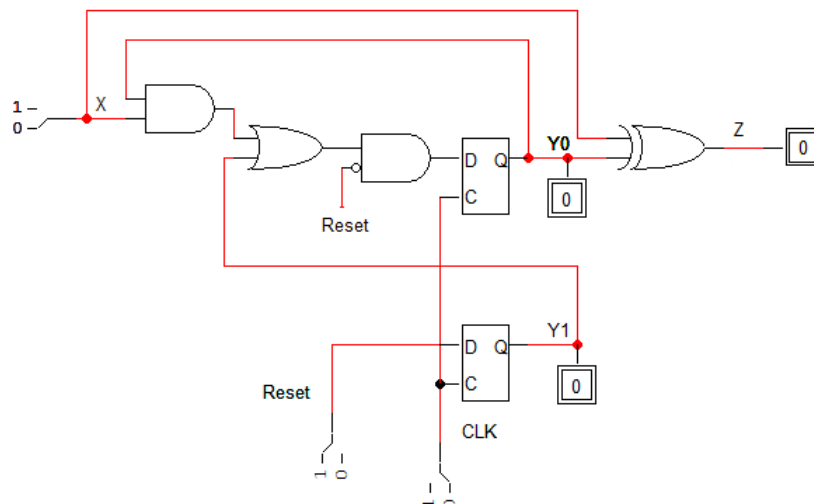


(ii) You are required to implement the above circuit using a **ROM** and a **register** with minimum sizes.

- a. What is the minimum size of the ROM (number of memory locations  $\times$  number of memory bits per location)? **(2 points)**

Since  $D1=0$ , we do not need to store it. Thus, the ROM size is  $2^3 \times 2$  bits

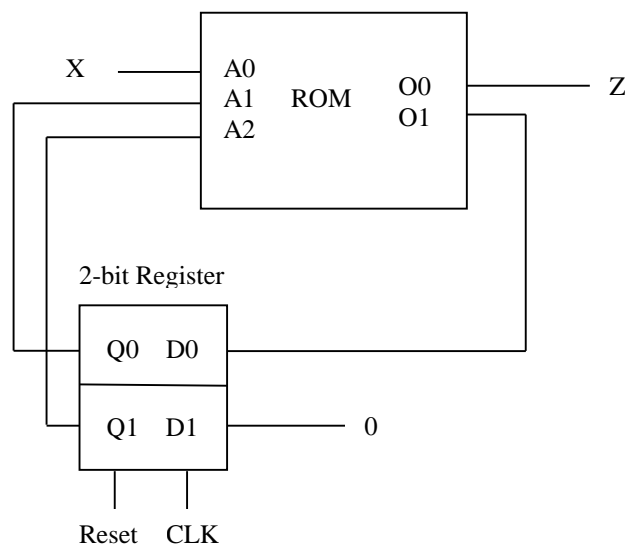- b. Draw the block diagram for such implementation. Add **Asynchronous Reset** to the register to reset the machine to state  $Y_1Y_0=10$ . (**Label all components inputs and outputs together with various signals**) **(3 points)**



Note that the Reset will be connect to Set input for Q1 and to CLR inputs for Q0.

- c. Starting from address **0**, fill in the following table to show the data stored in the first four memory locations in the ROM device.

**(2 points)**


Binary Address	Binary Stored Data
000	00
001	01
010	01
011	10

**Question 3.****(10 Points)**

- (i) Using minimum number of states, show the state diagram of a circuit that counts the number of 1's in an input stream (not necessarily consecutive). The circuit has one input X and one output Y. Y remains 0 until 4 ones are received on X, then Y becomes 1 and the circuit starts counting the number of 1s in the input stream again and Y return to 0. The asynchronous Reset input resets the circuit to an initial state where no 1 has been received yet. An example of an input sequence and the corresponding output sequence is shown below: **(5 points)**

	t = 0	
	↓	time →
X	0 0 1 0 1 1 0 0 1 0 0 1 1 0 1 0 1	
Y	0 0 0 0 0 0 0 0 0 1 0 0 0 0 0 0 0 1	

 
**(NOTE:** You are *only* required to draw the state diagram **Nothing MORE**)




- (ii) Show the **Moore-Model** state diagram of a sequential circuit that has two inputs  $X_1, X_2$  and one output  $Z$ . The asynchronous Reset input resets the circuit to an initial state with  $Z=0$ . If  $X_1=X_2$  (i.e.  $X_2X_1 = 00$  or  $11$ ), the circuit remains at the initial state. While in the initial state, if  $X_2X_1$  become  $01$ , the circuit produces an output of 1 then goes back to the initial state. If  $X_2X_1$  become  $10$ , the circuit produces the output sequence  $\{1,1\}$  then goes back to the initial state. **If the inputs change while the circuit is producing an output sequence, these changes are ignored until the circuit goes back to the initial state.** An example of an input sequence and the corresponding output sequence is shown below: **(5 points)**

	t = 0	time											
	↓	→											
$X_2$	0	1	1	1	1	0	0	0	1	...			
$X_1$	0	1	0	0	0	0	1	1	0	...			
$Z$	0	0	0	1	1	0	0	1	0	1	1	0	...

 **(NOTE: You are *only* required to draw the state diagram Nothing MORE)**



**Another solution—S1 and S3 are the same**

 


**Question 4.**

**(8 Points)**

- (i) Using minimum number of D-FFs and other needed components, show the design of a 3-bit register Q that has two control inputs: Load and Shift. The register has a 3-bit external input  $I_2I_1I_0$  and a serial input  $S_{in}$ . The table below shows the functionality of the register. **(4 points)**

Load	Shift	Action
0	0	No change in Q
1	X	Load parallel input (i.e. $Q_2Q_1Q_0 \leftarrow I_2I_1I_0$ )
0	1	Shift Q to the right with $S_{in}$ inserted from the left (i.e., most significant bit)

 

- (ii) Complete the following table by showing the content of register Q after each clock cycle:

**(4 points)**

Clock #	Load	Shift	$S_{in}$	$D_2 D_1 D_0$	$Q_2 Q_1 Q_0$
1	0	0	0	0 0 0	0 0 0
2	1	0	0	1 0 1	0 0 0
3	0	1	1	1 1 1	1 0 1
4	0	0	1	0 0 1	<b>1 1 0</b>
5	0	1	0	0 0 0	<b>1 1 0</b>
6	1	1	0	1 0 0	<b>0 1 1</b>
7	0	0	1	1 1 0	<b>1 0 0</b>

Inputs in a cycle affect the register in the next cycle

**Question 5**


**(9 Points)**

*In this question, you are to use only a 4-bit register and MSI parts, and minimum number of gates.*

- (i) Design a modulo-16 counter that can increment by 3, i.e.  $(0 \rightarrow 3 \rightarrow 6 \dots 13 \rightarrow 0)$ . **(3 points)**
- (ii) Show how to modify the above counter such that it can count either up (by 3) or down (by 3) based on the value of an additional control input **U** (if  $U=1$  counting is up otherwise it is down) **(2 points)**
- (iii) Show how to modify the above counter to have synchronous clear, parallel load and count enable capabilities as follows: **(4 points)**

CLR	CE	LD	Operation
1	X	X	Counter is Cleared
0	1	X	Counting (Up or down depending on the value of U)
0	0	1	Parallel Load of external input Data
0	0	0	No Change

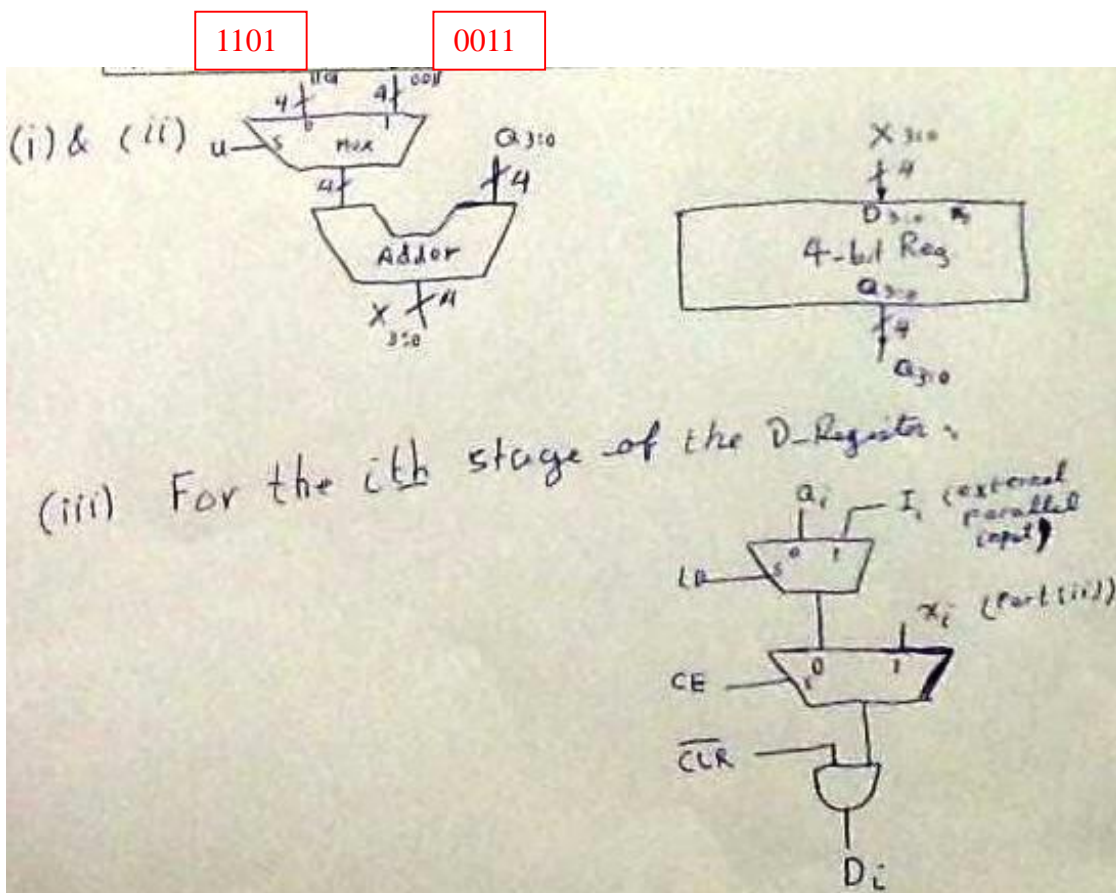**Note that you have the option to show the final design to implement all the requirements without showing a step-by-step design.**





 
## Question 6

(7 Points)

Write a Verilog module for modeling the behavior of the sequential circuit represented by the state diagram given below which has a single input X and a single output Z. Assume the state assignment: S0=00, S1=01, and S2=10. Assume the availability of **Synchronous Reset** input that resets the machine to state S0.



```
module FSM(output reg Z, input X, Reset, CLK);
```

```
parameter S0 = 2'b00, S1=2'b01, S2=2'b10;
reg [1:0] state, next_state;
```

```
always @(posedge CLK)
  if (Reset) state <= S0; else state <= next_state;
```

```
always @(state, X) begin
```

```
Z=0;
```

```
case (state)
```

```
  S0: if (X) begin Z=1; next_state=S1; end else next_state=S0;
```

```
  S1: if (X) next_state=S2; else begin Z=1; next_state=S0; end
```

```
  S2: if (X) begin Z=1; next_state=S2; end else next_state=S1;
```

```
  default: begin Z='bx; next_state='bx; end
```

```
endcase
```

```
end
```

```
endmodule
```

## Verilog Primitives

### ❖ Basic logic gates only

- ❖ **and**
- ❖ **or**
- ❖ **not**
- ❖ **buf**
- ❖ **xor**
- ❖ **nand**
- ❖ **nor**
- ❖ **xnor**

These gates are expandable: 1st node is O/P node, followed by 1, 2, 3 ... number of input nodes

## Verilog Operators

{ }	concatenation	~	bit-wise NOT
+ - * / **	arithmetic	&	bit-wise AND
%	modulus		bit-wise OR
> >= < <=	relational	^	bit-wise XOR
!	logical NOT	^~ ~^	bit-wise XNOR
&&	logical AND	&	reduction AND
	logical OR		reduction OR
==	logical equality	~&	reduction NAND
!=	logical inequality	~	reduction NOR
===	case equality	^	reduction XOR
!==	case inequality	~^ ^~	reduction XNOR
? :	conditional	<<	shift left
		>>	shift right