

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 162 (Winter 2017)**  
**Final Exam**  
**Wednesday, May 24th, 2017**

**Time: 120 minutes, Total Pages: 10**

**Name:** KEY **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated


Question	Maximum Points	Your Points
<b>1</b>	<b>6</b>	
<b>2</b>	<b>8</b>	
<b>3</b>	<b>10</b>	
<b>4</b>	<b>7</b>	
<b>5</b>	<b>9</b>	
<b>6</b>	<b>8</b>	
<b>7</b>	<b>13</b>	
<b>Total</b>	<b>61</b>	

**Question 1:****(6 points)**


A **Moore** *Odd parity detector* circuit has a single input  $x$  and a single output signal *parity*. The input consists of 2-bit data chunks that are *serially received* at the input  $x$ . The *parity* output is 1 whenever the received 2-bit stream has an odd number of 1's, and 0 otherwise. Draw the state diagram of this circuit. **The circuit has an asynchronous reset input to reset the machine to a reset state with an output of 0.** You are *only* required to draw the state diagram **Nothing MORE**)

Example:

		$t = 0$	time
		↓	→
Input	$x$	1 1 _ 1 0 _ 0 0 _ 0 1 _ 0 0 _ 1 0 _	
Output	<i>parity</i>	0 0 _ 0 0 _ 1 0 _ 0 0 _ 1 0 _ 0 0 _ 1	

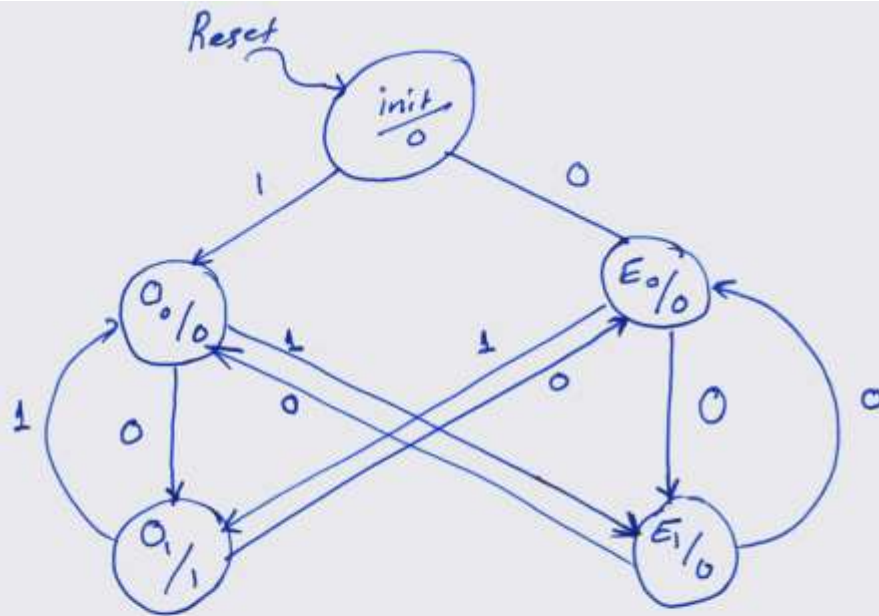


\* Alternative Solution

 


**Question 2:**

**(8 points)**

 1. The shown state diagram is for a **Moore** FSM of a sequence detector with a single input **X** and a single output **Y**. The circuit can detect **overlapping** (overlapping/non-overlapping) versions of the sequence **0110** (write the sequence). **(3 points)**



 2. It is required to design a sequence detector that detects the sequence {10110} (i.e., 1 followed by 0 followed by 1 followed by 1 followed by 0) in a serial input **Z** and produces 1 at the output **W** when the sequence is detected. Assuming overlapping sequences derive the state diagram of the circuit assuming a **MEALY** model. Also, assume the existence of an asynchronous *reset* input to reset the circuit to a reset state. You are *only* required to draw the state diagram **Nothing MORE**.



**(5 points)**

**Question 3:**

**(10 points)**

The state transition table below is for a sequential circuit with one input **X** and one output **Y**. The circuit has two state variables **A** and **B**, and an asynchronous input Reset that resets the circuit to state 00:

Reset State →	Present State		Next State		Output	
	A	B	X=0	X=1	X=0	X=1
			A <sup>+</sup> B <sup>+</sup>	A <sup>+</sup> B <sup>+</sup>	Y	Y
0 0	0	0	0 0	0 1	0	1
0 1	0	1	0 0	1 0	1	0
1 0	1	0	0 0	1 0	0	1
1 1	1	1	0 1	1 0	1	0

1. Does this circuit has any unused states? Briefly explain your answer (2 points)

**Yes, state 11, no normal input sequence can get the circuit to that state**

2. Design the above circuit using minimum number of logic gates and D-FFs (with asynchronous reset inputs) and draw the logic diagram of the designed circuit. The circuit should have asynchronous reset that reset it to state 00 (8 points)

	00	01	11	10
0	0	1	?	?
1	4	5	?	6


$D_A = X(A+B)$

	00	01	11	10
0	0	1	?	?
1	1	4	5	6

$D_B = XA'B'$


	00	01	11	10
0	0	1	?	?
1	1	4	5	6

$Y = X \oplus B$

 

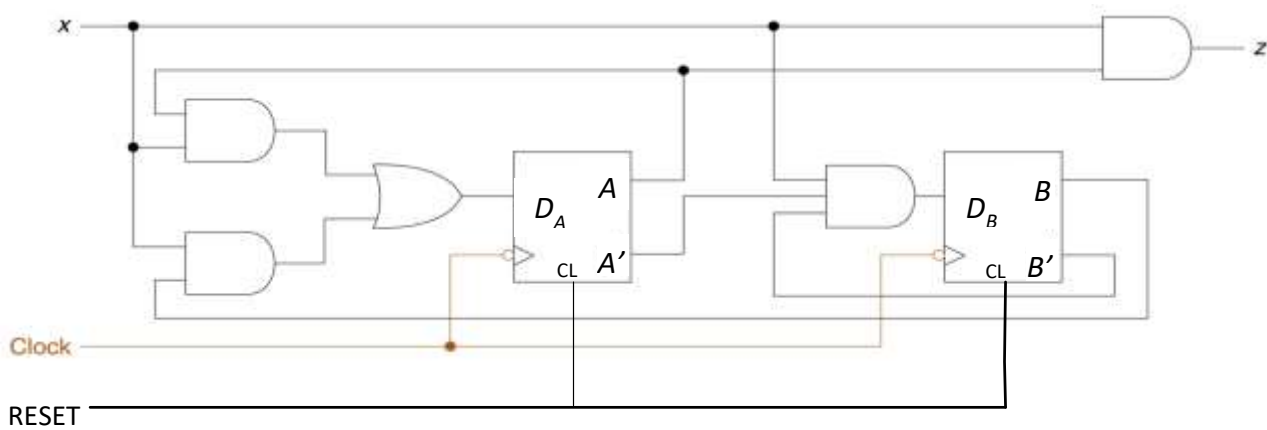**Question 4:****(7 points)**

The sequential circuit shown below has a single input  $x$  together with a **RESET** input to initialize the circuit. The used D-FFs have direct/asynchronous Clear inputs (shown in the figure as CLR).



- a. Obtain the Boolean expressions for the  $D_A$ ,  $D_B$  (flip flop inputs) and the output  $z$ . **(3 points)**

$$D_A = (A + B)x$$

$$D_B = A'B'x$$

$$z = Ax$$


- b. Derive the state transition table of the circuit (fill the table below).

**(4 points)**

Present State		Input	Next State		Output
A	B	x	A+	B+	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	0	1

 **Question 5:****(9 points)**

The state diagram below is for a sequential circuit that one input **X** (in addition to an **asynchronous Reset** input), one output **Y**, and state variables **A** and **B**.



1. Obtain the state transition table of this circuit. **(2 points)**

<i>A</i>	<i>B</i>	<i>X</i>	<i>A+</i>	<i>B+</i>	<i>Y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	0	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	0

2. Specify whether this circuit is a Mealy or Moore Machine? Explain **(1 point)**


**Moore, the output in each and every state is constant (i.e. does not depend on the input)**

3. If the circuit is in state **00**, what is minimum number of clock cycles required to reach state **11**?  
**3 clock cycles (00→01→10→11)** **(1 point)**

What is the required input sequence? **(1 point)**

**1-1-1**

4. Complete the following timing diagram of the circuit for the inputs shown assuming that the FFs are **positive edge triggered**: **(4 points)**

 




**Question 6:**

**(8 Points)**

- (i) Using minimum number of D-FFs and other needed standard components and logic gates, show the design of a 3-bit register Q that has two control inputs: S1 and S0. The register has a 3-bit external input  $I_2I_1I_0$ . The table below shows the functionality of the register. **(4 points)**

S1	S0	Action
0	0	No change in Q
1	X	Load parallel input (i.e. $Q_2Q_1Q_0 \leftarrow I_2I_1I_0$ )
0	1	$Q_2 \leftarrow Q_1, Q_1 \leftarrow Q_0, Q_0 \leftarrow Q_2 \oplus Q_0$

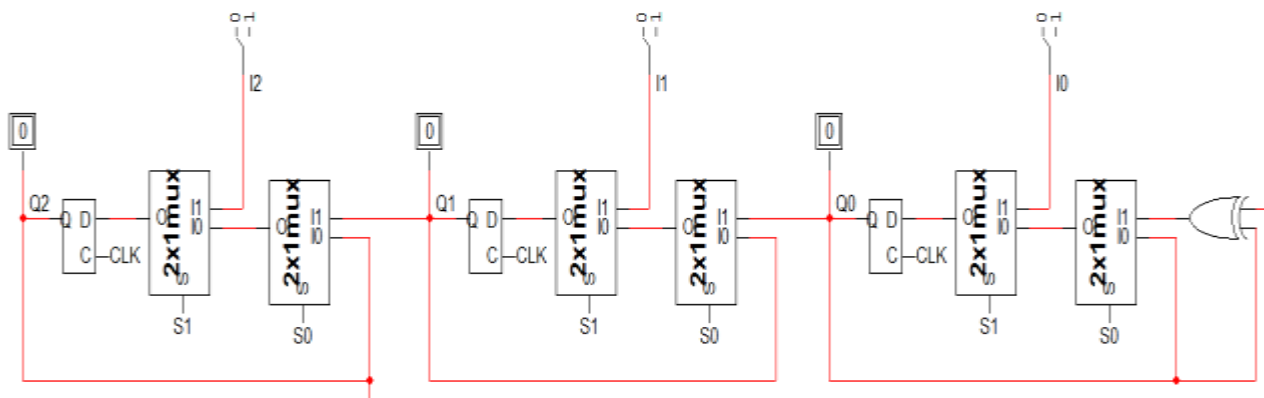

- (i) Complete the following table by showing the content of register Q after each clock cycle:

**(4 points)**


Inputs in a cycle affect the register in the next cycle

Clock #	S1	S0	$I_2 I_1 I_0$	$Q_2 Q_1 Q_0$
1	1	0	1 1 1	0 0 0
2	0	1	1 0 1	1 1 1
3	0	1	1 1 1	1 1 0
4	0	1	0 1 1	1 0 1
5	0	0	1 0 1	0 1 0
6	1	0	1 1 0	0 1 0
7	0	0	1 1 1	1 1 0

**Question 7**

**(13 Points)**

 
- I) It is required to design a **mod 8 up/down counter** that has the following control inputs:
- **LD** (parallel load), together with its associated inputs  $I_2, I_1, I_0$ .
  - **CE** (Count Enable)
  - **DIR** (when 0 counting up and when 1 counting down)



The counter produces an output signal ( $C_{out}$ ) which equals 1 when its output equals 7 when  $DIR=0$  and  $CE=1$  OR when its output equals 0 when  $DIR=1$  and  $CE=1$ . Design the counter using D-FFs and **minimum** number of logic gates and minimum-size Multiplexers. **Note: Do not use an adder in your solution.**

**(6 Points)**

LD	CE	DIR	Counter Next Content after the clock pulse ( $Q_2Q_1Q_0$ ) <sup>+</sup>
1	X	X	$I_2 I_1 I_0$ (load)
0	1	0	$(Q_2Q_1Q_0)+1$ (Increment up by 1)
0	1	1	$(Q_2Q_1Q_0)-1$ (Decrement up by 1)
0	0	X	$Q_2Q_1Q_0$ (no change)

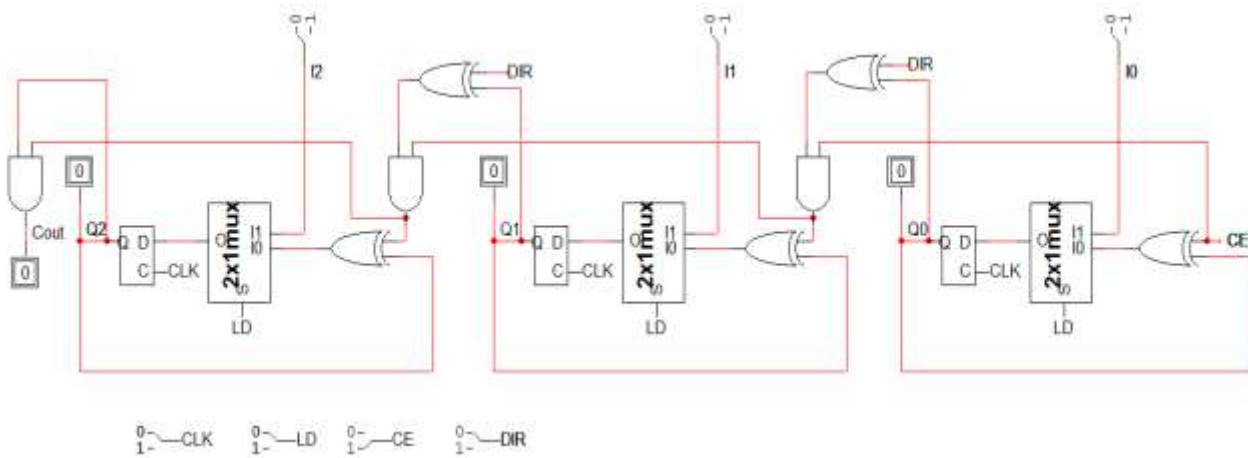

- II) Given that the clock frequency of the **mod-8 up/down counter** is 32 MHz, what is the clock frequency of the  $Q_2$  output of the counter when the counter is set as an up counter? **(1 Point)**

The clock frequency of  $Q_2$  will be  $32 \text{ MHz} / 8 = 4 \text{ MHz}$ .

