

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 102 (Spring 2011)**  
**Major Exam II**  
**Thursday April 28, 2011**

**Time: 120 minutes, Total Pages: 9**

Name: KEY ID: \_\_\_\_\_ Section: \_\_\_\_\_

**Notes:**

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	26	
2	16	
3	12	
4	26	
5	20	
<b>Total</b>	<b>100</b>	

## Question 1.

(26 points)

(A). For the following Boolean function  $F(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 12, 13)$ 

		C D			
		00	01	11	10
A B	00	1	1	0	1
	01	0	1	1	1
	11	1	1	0	0
	10	1	1	0	1

- (i) Identify all the prime implicants and the essential prime implicants of F. (7+2=9 points)
- (ii) Simplify the Boolean function **F** into a minimal sum-of-products expression. (5 points)

(i) Prime Implicants:

$$\bar{C}D, A\bar{C}, \bar{B}\bar{C}, \bar{B}\bar{D}, \bar{A}BD, \bar{A}BC, \bar{A}C\bar{D}$$

Essential Prime Implicants:

$$A\bar{C}, \bar{B}\bar{D}$$

(ii)  $F = A\bar{C} + \bar{B}\bar{D} + \bar{A}BC + \bar{C}D$


- (B) Consider the following Boolean function **F** together with the don't care conditions **d**  
 $F(A, B, C, D) = \sum m(0, 2, 5, 8, 10)$ ,  $d(A, B, C, D) = \sum m(1, 4, 7, 9, 11, 12, 14, 15)$

AB \ CD	00	01	11	10
	00	1	X	0
01	X	1	X	0
11	X	0	X	X
10	1	X	X	1


- (i) Simplify the Boolean function **F** together with the don't care conditions **d**, into minimal sum-of-products expression. (4 points)
- (ii) Starting with the sum-of-products expression, implement the function using only **NAND** gates and **Inverters**. (4 points)
- (iii) Starting with the sum-of-products expression, implement the function using only **NOR** gates and **Inverters**. (4 points)

(i) 
$$F = \overline{A} \overline{C} + \overline{B} \overline{D}$$

(ii)

 

(iii)

 


**Question 2.****(16 Points)**

Design a 3-bit decremter using only basic gates (AND, OR, and NOT). The circuit takes a 3-bit unsigned number  $\mathbf{I} = \mathbf{I}_2\mathbf{I}_1\mathbf{I}_0$  as input and generates a 3-bit output number  $\mathbf{Z} = \mathbf{Z}_2\mathbf{Z}_1\mathbf{Z}_0$  and a **Valid** output  $\mathbf{V}$ . Whenever  $\mathbf{I} > \mathbf{0}$  the output  $\mathbf{Z} = \mathbf{I} - \mathbf{1}$  and  $\mathbf{V} = \mathbf{1}$ . If  $\mathbf{I} = \mathbf{0}$ , the output is invalid which is indicated by an output  $\mathbf{V} = \mathbf{0}$ . Derive the simplified Boolean expressions of all outputs.

## Question 3.

(12 Points)

 

It is required to design a 7-segment display **driver** whose input is a Hexadecimal digit such that the resulting 7-seg display is as shown above (**Note that** HEX digits larger than 9 are displayed as **A** → **A**, **B** → **b**, **C** → **C**, **D** → **d**, **E** → **E**, **F** → **F**). The driver circuit should generate the 7-segment control signals (**a** to **g**).

If a single **decoder** and number of **OR** gates are used to build this driver circuit;

- What is the minimum size of the decoder? (3 points)
- What is the minimum a number of OR gates required to build the 7-segment display driver circuit (3 points)
- Draw the block diagram of the circuit showing in details how the control signals **g** and **c** are generated. (6 points)



**Question 4.**

**(26 Points)**

(A)

i. Determine the decimal value of the 7-bit binary number (1011010) when interpreted as:

An unsigned number	A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
90	-26	-37	-38


ii. Represent the decimal value (-21) in binary using a total of 7 bits in the following notations:

A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
1010101	1101010	1101011

iii. Perform the following signed-2's complement arithmetic operations in binary using 5 bits. All numbers given are represented in the signed-2's complement notation. Indicate clearly the carry values from the last two stages. For each of the three operations, check and indicate whether overflow occurred or not.

<p>01010</p> <p>a. <math>\begin{array}{r} \overset{1\leftarrow 1\leftarrow}{01101} \quad +13 \\ +10110 \quad +(-10) \\ \hline 00011 \quad +3 \checkmark \end{array}</math></p>	<p>b. <math>\begin{array}{r} 01010 \quad +10 \\ -11001 \quad 00111 \quad -(-7) \\ \hline 10001 \end{array}</math> <del>15</del></p>	<p>c. <math>\begin{array}{r} 11010 \quad 00110 \quad -6 \\ -00100 \quad -+4 \\ \hline 11010 \\ +11100 \\ \hline 10110 \\ = -01010 \\ = -10 \checkmark \end{array}</math></p>	
Overflow Occurred? (Yes/No)	No	Yes	NO

 (B) Consider the 2's complement 4-bit adder/subtractor hardware shown (FA = full adder).



i. Fill in the spaces in the table below.

Inputs			Outputs			
A	B	Control	S (binary)	C <sub>4</sub>	C <sub>3</sub>	Overflow
0111	0101	0	1100	0	1	1
1010	1101	1	1101	0	0	0

Handwritten calculations for the table entries:  
 For (0111, 0101, 0):  

$$\begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array}$$
  
 For (1010, 1101, 1):  



$$\begin{array}{r} 1010 \\ - 1101 \\ \hline 1101 \end{array}$$

ii. What type of 4-bit adder is used in this design? (Circle the correct answer):

- Carry-ripple adder
- Carry-look-ahead adder

b. Consider a 2-bit version of the hardware above which is shown below. Shown also is full adder used. Given that each basic gate (i.e. AND, OR, NOT) has a delay of  $\tau$  ns and the XOR gate has a delay of  $3\tau$ :

The Full Adder (FA)

  

i. Express, as a function of  $\tau$ , the longest time interval needed for the hardware to perform an operation on the two 2-bit numbers.

$$(3 + 3 + 2 + 3)\tau = 11\tau$$

ii. If such an operation must be performed in no longer than 33 ns, calculate the maximum basic gate delay allowed.

$$33 \text{ ns} / 11 = 3 \text{ ns}$$




## Question 5.

(20 Points)


(A) Given the function

$$F(A,B,C) = \prod M(0,2,4,5,6)$$

 i. Implement F using one (1) 3-to-8 decoder, and one (1) **NOR** gate. Properly label all input and output lines.



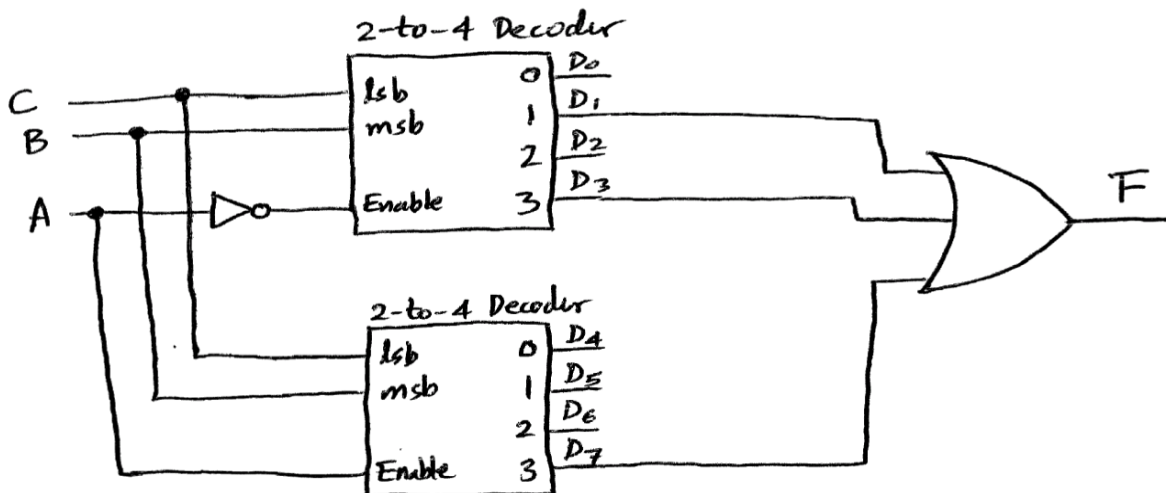
ii. Implement F using two (2) 2-to-4 decoders with enable, one (1) inverter, and one (1) **OR** gate. Properly label all input and output lines.



(B) Given the function

$$F(A,B,C) = \sum m(1,3,7)$$

 i. Implement F using an 8-to-1 MUX. Properly label all input and output lines.



ii. Implement F using a 4-to-1 MUX. Show how you obtained your solution, and properly label all input and output lines.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$\left. \begin{array}{l} \text{Row 1} \\ \text{Row 2} \end{array} \right\} I_0 = C$   
 $\left. \begin{array}{l} \text{Row 3} \\ \text{Row 4} \end{array} \right\} I_1 = C$   
 $\left. \begin{array}{l} \text{Row 5} \\ \text{Row 6} \end{array} \right\} I_2 = \phi$   
 $\left. \begin{array}{l} \text{Row 7} \\ \text{Row 8} \end{array} \right\} I_3 = C$

OR

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}$	0	2	4	6
C	①	③	5	⑦
	$I_0 = C$	$I_1 = C$	$I_2 = \phi$	$I_3 = C$

