

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 112 (Spring 2012)
Major Exam II
Thursday April 12, 2012

Time: 150 minutes, Total Pages: 13

Name: KEY _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	23	
2	22	
3	10	
4	20	
5	15	
6	15	
Total	105	

Question 1.

(23 points)

(a) For the following Boolean function shown in the K-map:

$$F(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 7, 10, 12, 13, 14, 15)$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	1	1	1
	11	1	1	1	1
	10	0	0	0	1

(i) Identify all the prime implicants and the essential prime implicants of F.Prime Implicants:

$$AB, \quad C\bar{D}, \quad BC, \quad BD, \quad \bar{A}\bar{B}\bar{C}, \quad \bar{A}\bar{B}\bar{D}, \quad \bar{A}\bar{C}D$$

Essential Prime Implicants:

$$AB, \quad C\bar{D}$$

(ii) Simplify the Boolean function F into a minimal sum-of-products expression.

$$F = AB + C\bar{D} + BD + \bar{A}\bar{B}\bar{C}$$

- (b) Consider the following Boolean function F together with the don't care conditions d shown in the k-map:


$$F(A, B, C, D) = \sum m(0, 10, 15), d(A, B, C, D) = \sum m(1, 2, 4, 8, 11, 14)$$

AB \ CD	00	01	11	10
	00	1	X	0
01	X	0	0	0
11	0	0	1	X
10	X	0	X	1


- (i) Simplify the Boolean function F together with the don't care conditions d , into minimal sum-of-products expression.

$$F = AC + \bar{B}\bar{D}$$

 - (ii) Starting with the sum-of-products expression, implement the function using only **NAND** gates and **Inverters**.



- (iii) Starting with the sum-of-products expression, implement the function using only **NOR** gates and **Inverters**.

 

Question 2.**(22 Points)**

Design a circuit that accepts two 2-bit unsigned numbers $A = A_1A_0$ and $B = B_1B_0$. The circuit produces $A - B$ when $A > B$, and produces $A + B$ otherwise. Find the following:

(a) The number of outputs produced by the circuit.

$A - B$ result is at most 2 bits, $A + B$ result is at most 3 bits \Rightarrow # outputs = 3

(b) The truth table of the circuit.

A_1	A_0	B_1	B_0	O_2	O_1	O_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	0	1	0
1	1	1	0	0	0	1
1	1	1	1	1	1	0

(c) The minimal product-of-sums expression for each output.

		B ₁ B ₀			
		00	01	11	10
A ₁ A ₀	00	0	0	0	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	1

$$O_2 = (A_1 + A_0)(\overline{A_0} + B_0)B_1$$

		B ₁ B ₀			
		00	01	11	10
A ₁ A ₀	00	0	0	1	1
	01	0	1	0	1
	11	1	1	1	0
	10	1	0	0	0

$$O_1 = (A_1 + A_0 + B_1)(A_1 + B_1 + B_0)(\overline{A_1} + A_0 + \overline{B_0})(\overline{A_1} + \overline{B_1} + B_0)(A_1 + \overline{A_0} + \overline{B_1} + \overline{B_0})$$

		B ₁ B ₀			
		00	01	11	10
A ₁ A ₀	00	0	1	1	0
	01	1	0	0	1
	11	1	0	0	1
	10	0	1	1	0



$$O_0 = (A_0 + B_0)(\overline{A_0} + \overline{B_0})$$

Question 3.

(10 Points)


- (a) Use the shown circuit on the right to build a 4-bit **adder-subtractor** which can add or subtract two 4-bit numbers X and Y . A mode control input signal M is used to define the operation to be performed; if $M=0$, output is $(X+Y)$ while if $M=1$, output is $(X-Y)$.

CLEARLY label ALL inputs and outputs

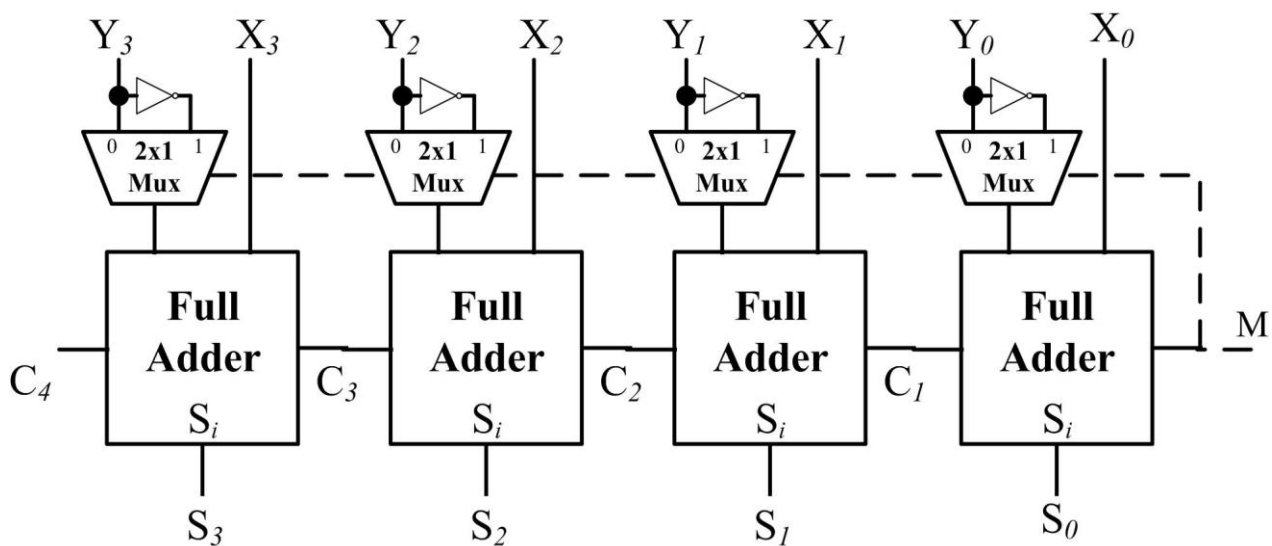 

- (b) The Full-Adder circuit is shown to the right. Given the following gate delays;

Gate/ Circuit	Propagation Delay
Inverter	1τ
AND, OR	2τ
XOR	4τ
2x1 Mux	5τ

 

- (i) What is the carry propagation delay per Full adder stage?

$$T(\text{CP}) = T_{\text{AND}} + T_{\text{OR}} = 4\tau$$

- (ii) For an n -bit Ripple-Carry Adder-Subtractor using the circuit of part (a), what is the total delay for the n^{th} sum bit and the $(n+1)^{\text{th}}$ carry-out bit?

(Clearly identify each delay component)

$$\text{Delay of the } n^{\text{th}} \text{ Sum output} = (1\tau + 5\tau + 4\tau + (n-1) * 4\tau + 4\tau) = 4n\tau + 10\tau$$

$$\text{Delay of the } (n+1)^{\text{th}} \text{ Carry output} = (1\tau + 5\tau + 4\tau + (n) * 4\tau) = 4n\tau + 10\tau$$

Question 4.

(20 Points)

- (a) If **6-bit registers** are used, show the binary number representation of the decimal numbers (+23), (-23), (+11), and (-11) using the following representation systems:

	+23	-23	+11	-11
Signed magnitude system	010111	110111	001011	101011
Signed 1's complement system	010111	101000	001011	110100
Signed 2's complement system	010111	101001	001011	110101

- (b) Provide the decimal equivalent of each of the following **signed 2's complement** numbers:

Signed 2's Complement Number	Equivalent Decimal Number
001101	+13
010011	+19
101101	-19
110011	-13


- (c) If **6-bit registers** are used, perform the following **signed 2's complement** arithmetic operations on the provided signed 2's complement numbers. For each case, state whether the result is correct or an **overflow** has occurred.

Signed 2's Complement Arithmetic Operation	Correct Answer or Overflow?
<p>(i) 001101 - 101101</p> $\begin{array}{r} 001101 \\ - 101101 \\ \hline \end{array} \Rightarrow \begin{array}{r} 001101 \\ + 010011 \\ \hline 100000 \end{array}$	Overflow
<p>(ii) 010011 - 001101</p> $\begin{array}{r} 010011 \\ - 001101 \\ \hline \end{array} \Rightarrow \begin{array}{r} 010011 \\ + 110011 \\ \hline 000110 \end{array}$	<i>Correct</i>
<p>(iii) 101101 + 110011</p> $\begin{array}{r} 101101 \\ + 110011 \\ \hline 100000 \end{array}$	<i>Correct</i>

Question 5.**(15 Points)**


Given the function $F(A, B, C) = A B + \bar{A} C$

 - (a) Implement F using a single 2-to-1 MUX with no additional gates. Properly label all input and output lines.



 
- (b) Implement F using a 4-to-1 MUX. Properly label all input and output lines.

$$F = \bar{A} \bar{B} (C) + \bar{A} B(C) + A \bar{B} (0) + A B (1)$$




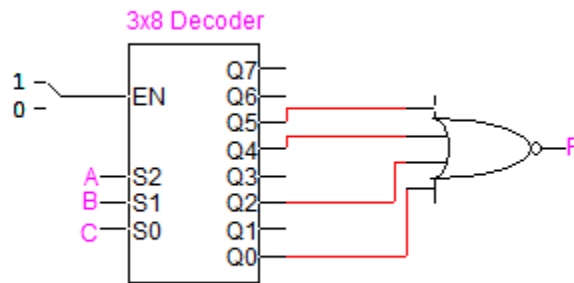- (c) Implement F using a single 3-to-8 decoder, and a single NOR gate. Properly label all input and output lines.

$$F = \sum m(1,3,6,7) = \prod M(0,2,4,5)$$



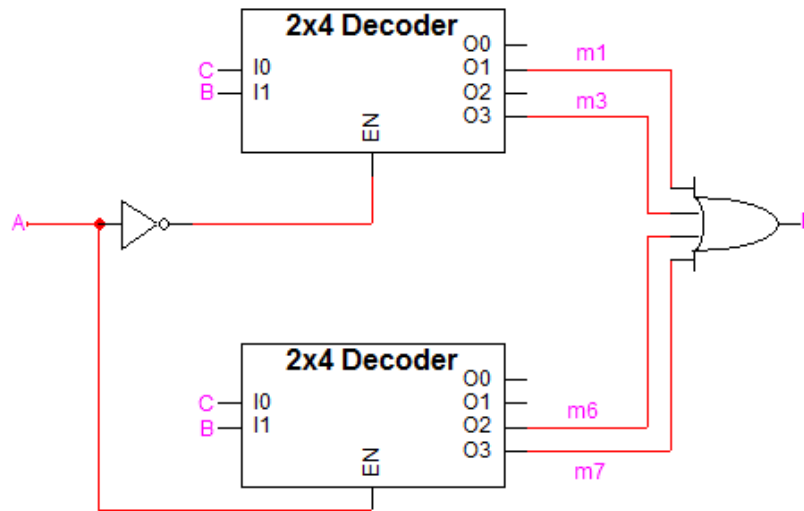- (d) Implement F using two 2-to-4 decoders with enable, one inverter, and one OR gate. Properly label all input and output lines.



(15 points)

Question 6.

(a) Given two 4-bit signed 1's complement numbers **A** and **B**; for $A = 1010$ and $B = 1101$;

(i) What are the corresponding decimal values of **A** and **B**?


$$\mathbf{A=1010} = (-5)_{\text{Decimal}} \quad \mathbf{B=1101} = (-2)_{\text{Decimal}}$$

(ii) If these values of **A** and **B** are applied to the shown magnitude comparator circuit, what are the values of the resulting outputs?

$$(\mathbf{X} > \mathbf{Y}) = \underline{\mathbf{0}}$$

$$(\mathbf{X} = \mathbf{Y}) = \underline{\mathbf{0}}$$
 
$$(\mathbf{X} < \mathbf{Y}) = \underline{\mathbf{1}}$$



(b) Given two 4-bit signed 1's complement numbers **A** and **B**, design the following circuits using any number of the following components: XOR gates, decoders, encoders, multiplexers, adders, and/or magnitude comparators:

(i) A circuit whose 4-bit output **Z** equals the larger of either **A** or **B** given that both **A** and **B** are positive values.

(ii) A circuit whose 4-bit output **Z** equals the larger of either **A** or **B** given that both **A** and **B** are negative values (*Hint: use conclusions of part (a)*).

(iii) A circuit whose 4-bit output **Z** equals the larger value of either **A** or **B** given that **A** and **B** may be +ive or -ive in any possible combination.

(You **must** clearly label the MSI parts used together with all inputs and outputs)

