

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 121 (Fall 2012)
Major Exam II
Thursday Nov. 22, 2012

Time: 150 minutes, Total Pages: 9

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	15	
2	14	
3	9	
4	15	
5	11	
6	13	
7	8	
Total	85	

Question 1.

(15 points)

The logic function $F(W,X,Y,Z)$ is plotted on the K-map shown below. Z is the LSB. **(15 Points)**

a. The function F can be expressed in the canonical form as a product of maxterms as follows: **(2 points)**

$F(W,X,Y,Z) = \prod M(\underline{\hspace{10em}})$

b. Indicate whether each of the following is True or False: **(2 Points)**

- $W\bar{X}Z$ is a prime implicant for the function
- $\bar{W}XY$ is an essential prime implicant for the function

	YZ	00	01	11	Y 10	
WX						
00				1		
01		1		1	1	
11				1		X
W						
10		1	1	1		
						Z

c. The function F can be minimized to an optimal algebraic sum of products as: **(3 points)**

$F(W,X,Y,Z) = \underline{\hspace{10em}}$

d. The function F can be minimized to an optimal algebraic product of sums as: **(5 points)**

$F(W,X,Y,Z) = \underline{\hspace{10em}}$

e. If we are told that we should not care about the output of the circuit implementing F for the input combination $WXYZ = 1010$. **(3 Points)**

- i) Indicate this condition on the K-map
- ii) If this information leads to a more optimal expression for F than that obtained in part (c) above, then give that more optimal expression.

Question 2.

(14 Points)

We would like to design a combinational circuit that multiplies two unsigned integers X and Y and produces the product as output Z, i.e. $Z = XY$. Each of the two integers X and Y is 2 bits. The binary representations of the input and output numbers are $X_1 X_0$ for X (X_0 is the LSB), $Y_1 Y_0$ for Y (Y_0 is the LSB), $Z_n \dots Z_2 Z_1 Z_0$ for Z (Z_0 is the LSB).

a. (8 points) Fill in all the required information in the table below.

Circuit Input $X_1 X_0 Y_1 Y_0$ (Binary)	Circuit Output $Z_n \dots Z_2 Z_1 Z_0$	
	(Binary)	(Decimal)

b. (6 points) Use a K-map of the appropriate size to minimize the binary output **Z1** and express the minimized function as a sum of products in terms of the binary inputs $X_1, X_0, Y_1,$ and Y_0 . Show all your work.

Question 3.

(9 Points)

- (a) (5 points) Draw the multi-level NAND logic diagram for the following Boolean expression, *don't simplify*:

$$(\overline{A}B + \overline{C}D)E + A\overline{D}(B + C)$$

- (b) (4 points) Using the minimum number of logic gates, draw the 2-level NOR logic diagram for the following Boolean expression:

$$F(A,B,C) = \Sigma m(0, 3, 5, 6)$$

Question 4.**(15 Points)**

- (a) **(6 points)** Determine the decimal value of the **7-bit** binary number (1001100) when interpreted as:

Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number

- (b) **(3 points)** Find the **smallest** 7-bit signed-2's complement number that can be added to the 7-bit signed-2's complement number (1001100) **without causing an overflow**. Note that negative numbers are considered to be smaller than positive numbers.

- (c) **(6 points)** Perform the following **signed-2's complement arithmetic** operations in binary using **5 bits**. All numbers given are represented in the signed-2's complement notation. Indicate clearly the **carry values out of the last two bits**. For each of the two operations, check and indicate whether an overflow has occurred or not.

Operation	Carry value out of the 4 th bit	Carry value out of the 5 th bit	Overflow occurred? (Yes/No)
a. 01011 +11110 <u> </u>			
b. 01001 -10010 <u> </u>			

Question 5.

(11 Points)

- (a) (6 points) You are given one 3-to-8 decoder, one NOR gate and one OR gate to implement the two functions given below.

$$F_1(A,B,C) = \prod M(0, 1, 4, 5, 6)$$

$$F_2(A,B,C) = \sum m(0, 4, 6) + \sum d(1, 3)$$

Draw the circuit and properly label all input and output lines.


- (b) (5 points) Given the truth table below for a function with four inputs (A, B, C and D) and one output F, implement F using a 4-to-1 MUX (with 2 select lines) and additional logic. Show how you obtained your solution, and properly label all input and output lines. Apply A and B to the select inputs.

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Question 6.**(13 points)**

Assume that the delay of a 2-input XOR gate is $3ns$ while the delay of other gates is equal to the gate's number of inputs, i.e. the delay of an inverter is $1ns$, the delay of a 2-input AND gate is $2ns$, the delay of a 2-input OR is $2ns$, the delay of a 3-input AND gate is $3ns$, the delay of a 3-input OR gate is $3ns$, etc.

 (a) (6 points) A 4-bit **Ripple Carry Adder** (RCA) is given below:



Determine and compute the **longest delay** in the **4-bit Ripple Carry Adder** (RCA).

(b) (4 points) Show the design of a **2-bit Carry Look-Ahead Adder (CLA)** by drawing its logic diagram.

(c) (3 points) Using the delay assumptions given in the beginning of the question, determine and compute the **longest delay** in the **2-bit Carry Look-Ahead Adder (CLA)**.

Question 7.

(8 points)

Using a **minimal** number of **MSI** components such as: **decoders, encoders, multiplexers, adders, magnitude comparators** and other necessary logic gates, design a circuit that takes two **4-bit** binary numbers $A=A_3A_2A_1A_0$ and $B=B_3B_2B_1B_0$ and a 2-bit user selection input $S=S_1S_0$. The circuit should produce a 5-bit output $O=O_4O_3O_2O_1O_0$ according to the following table:

S_1S_0	O is equal to
00	$A+B$
01	$A-B$
10	$A+1$
11	$2*A$