

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 122 (Spring 2013)
Major Exam II
Thursday April 18, 2013

Time: 150 minutes, Total Pages: 12

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	14	
2	15	
3	17	
4	8	
5	12	
6	8	
7	18	
Total	92	

(14 points)

Question 1.

For the following Boolean function shown in the K-map:

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6, 8, 10, 13, 15)$$


- Identify all the *prime implicants* and the *essential prime implicants* of F.
- Simplify the Boolean function **F** into a minimal **sum-of-products** expression.
- Simplify the Boolean function **F** into a minimal **product-of-sums** expression.

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	1	0	1
	11	0	1	1	0
	10	1	0	0	1


Question 2.**(15 Points)**

It is required to design a Tripler circuit. The circuit receives an n -bit number X and computes the result $Y=3*X$.

 
- a. If the input is an n -bit unsigned number, what is the size of the output “ y ” in bits?



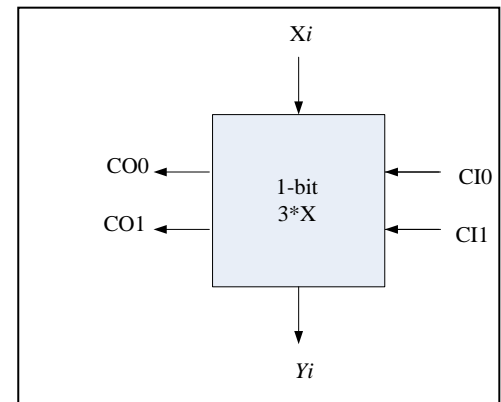- b. The circuit can be constructed using n identical copies of the basic 1-bit cell shown to the right. The cell processes one input bit (X_i) and produces one output bit (Y_i) and two output carry bits (CO_0 and CO_1). To allow for cascading n such cells to implement an n -bit Tripler, the basic cell also accepts two input carry bits (CI_0 and CI_1). **When the output carry equals 1 then $CO_1 CO_0 = 01$ while when it equals 2 then $CO_1 CO_0 = 10$.**



 The Figure below shows how a 4-bit Tripler circuit is implemented using 4 copies of the basic 1-bit cell.



Derive the truth table for the basic one-bit cell.

(Hint: *As the initial input carries = 00, the maximum carry from one cell to the next is 2*)

- c. Derive a minimized sum-of-product expressions for the outputs of the basic one-bit cell.

Question 3.

(17 Points)

- a. Fill in all blank cells in the two tables below. All binary representations use 7 bits

Binary	Equivalent decimal value with the binary interpreted as:			
	Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number
1011010				

Decimal	Binary representation in:		
	Signed-magnitude notation	Signed-1's complement notation	Signed-2's complement notation
- 59			

- b. Using 2's-complement signed arithmetic in **5 bits**, perform the following operations in binary. Show all your work. Verify that you get the expected decimal results.

Check for overflow and mark clearly any occurrences of it.

$\begin{array}{r} 11010 \\ + 11001 \\ \hline \end{array}$	(i)	$\begin{array}{r} 00101 \\ - 10100 \\ \hline \end{array}$	(ii)
$\begin{array}{r} (+5) \\ + (-9) \\ \hline \end{array}$	(iii)	$\begin{array}{r} (-6) \\ - (+8) \\ \hline \end{array}$	(iv)

- c. When doing signed 2's complement arithmetic in **6 bits**, the *smallest* binary number **that will cause overflow** when *subtracted* from 101000_2 is _____.


Question 4.**(8 Points)**

a. Show the logic diagrams that implement the given logic circuit using the minimum number of:

i. **2-input** NOR gates only. Use the following symbol for this NOR gate: 

 ii. **2-input** NAND gates only. Use the following symbol for this NAND gate: 


Note: Complements of the input variables are readily available.



b. In the logic circuit shown below, with **A** being any 4-bit input value,


- Output 1 = _____ (0 / 1 / Depends on A), and
- Output 2 = _____ (0 / 1 / Depends on A).

Note: *The odd function gives a 1 output when the number of 1s in the input is odd.*

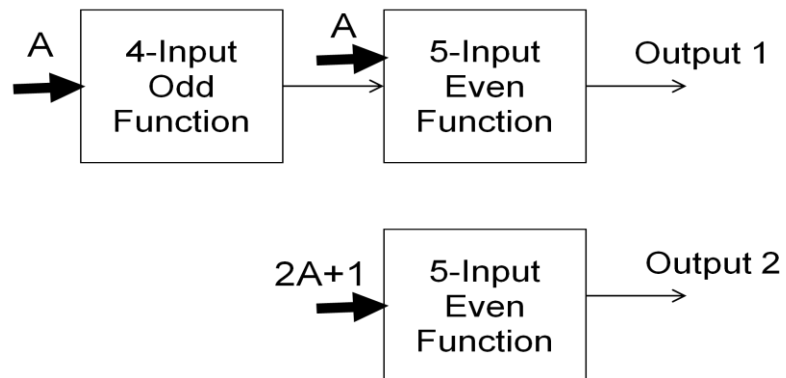

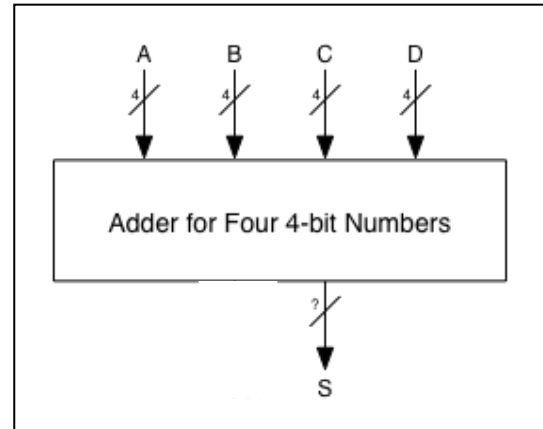Question 5.**(12 Points)**

You are required to design a circuit that adds **four unsigned 4-bit numbers**. The following is the high-level diagram of the circuit.



a. What is the size of the output sum (S) in bits? [2 pts]

b. Using ONLY 4-bit adders, show how the above circuit can be constructed? [10 pts]

Question 6.

Assuming the availability of the true and complement of signals A, B and C, implement the following Boolean function.



$$F(A, B, C) = \bar{A}\bar{B}C + B\bar{C} + AB$$

- a. Using a single minimum size multiplexer. [4 pts]
- b. Using a single minimum size decoder and **minimum other** gates. [4 pts]

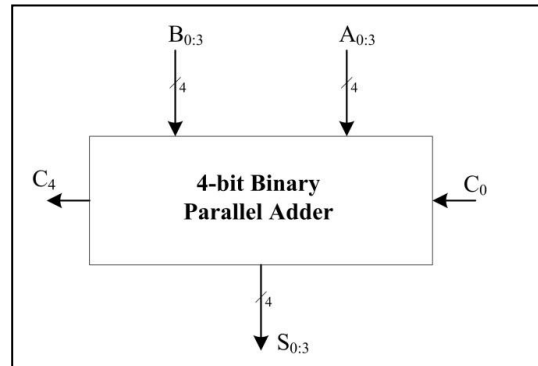 Question 7.**(18 Points)**

It is required to build a 4-bit binary parallel adder which adds two 4-bit numbers **A** ($A_3 A_2 A_1 A_0$), and **B** ($B_3 B_2 B_1 B_0$) together with an input carry bit C_0 (which may be 0 or 1).

The full adder circuit shown below will be used as a main building block of this adder.



a. Write the Boolean expressions of the P_i , G_i , S_i and C_{i+1} *full adder* signals. (2 Points)

b. If the 4-bit adder is implemented as a **Ripple Carry Adder** (RCA), draw the block diagram implementation of this adder. (1 Point)

c. Assuming gate delays of **3ns** for XOR gates and **1ns** for other gates; (3 Points)

- I. What are the delays of the P_0 and G_0 signals?
- II. What are the delays of the P_3 and G_3 signals?
- III. What is the carry-propagation delay of a single full adder (i.e., delay from C_i to C_{i+1})?

d. What is the worst case delay of the 4-bit **RCA**?

(4 Points)

e. If the 4-bit adder is implemented as a **Carry Lookahead Adder** (CLA), derive the Boolean expressions of the *four* Carry signals C_1 , C_2 , C_3 , and C_4 .

(2 Points)

f. Draw a block diagram (no detailed 2-level gate implementations) of the **CLA** adder implementation
(2 Points)

g. What is the worst case delay of the CLA?

(4 Points)