

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)

Term 131 (Fall 2013)

Major Exam II

Saturday November 30, 2013

Time: 120 minutes, Total Pages: 12

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	14	
2	8	
3	20	
4	12	
5	15	
6	16	
Total	85	

Question 1.

(14 points)

Question 1.

(14 points)

For the following Boolean function shown in the K-map:

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 10, 11, 13, 14, 15)$$

		CD			
AB		00	01	11	10
		1	1	1	1
01		0	1	1	0
11		0	1	1	1
10		1	0	1	1

- Identify all possible prime implicants of F and indicate which of these is essential.
- Simplify the Boolean function F into a minimal sum-of-products expression.
- Simplify the Boolean function F into a minimal product-of-sums expression.

a. Prime Implicants:

$$A'B', CD, A'D, BD, AC, B'C, B'D'$$

Essential Prime Implicants:


$$BD, AC, B'D'$$

b. $F = BD + AC + B'D' + A'B'$ OR $F = BD + AC + B'D' + A'D$

c. $F = (B' + C + D)(A + B' + D)(A' + B + C + D')$

 Question 2.**(8 Points)**

It is required to design a circuit to compute the equation $Z=2*X-Y$, where X and Y are two n -bit unsigned numbers. The circuit can be designed in a modular manner where it is designed for one bit and replicated n times. A 1-bit circuit block diagram is given below:




The meaning of the values of B_i and C_i is given in the table below:

B_i	C_i	Meaning
0	0	There is no carry or borrow
0	1	There is a carry of 1
1	0	There is a borrow of 1
1	1	This condition does not occur

For example, if $X_i=1$ and $Y_i=1$, then we should have $Z_i=1$, $B_{i+1}=0$ and $C_{i+1}=0$. If $X_i=0$ and $Y_i=1$, then we should have $Z_i=1$, $B_{i+1}=1$ and $C_{i+1}=0$.

 The figure below shows how a 4-bit $Z=2*X-Y$ circuit is implemented using 4 copies of the basic 1-bit cell.



Derive the truth table for the basic one-bit cell. You do not need to derive the equations for the circuit.

X_i	Y_i	B_i	C_i	B_{i+1}	C_{i+1}	Z_i
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	1	0	1
0	0	1	1	X	X	X
0	1	0	0	1	0	1
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	X	X	X
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	0	1
1	0	1	1	X	X	X
1	1	0	0	0	0	1
1	1	0	1	0	1	0
1	1	1	0	0	0	0
1	1	1	1	X	X	X

Question 3.

(20 Points)

a. Fill in all blank cells in the two tables below.

Binary	Equivalent decimal value with the binary interpreted as:				
	Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number	BCD number
10000000	128	-0	-127	-128	80

Decimal	Binary representation in 8 bits:		
	Signed-magnitude notation	Signed-1's complement notation	Signed-2's complement notation
-75	11001011	10110100	10110101

b. Using 2's-complement signed arithmetic in 5 bits, do the following operations in binary. Show all your work, and:

- Verify that you get the expected decimal results.
- Check for overflow and mark clearly any overflow occurrences.

<p>(i)</p> $\begin{array}{r} 00111 \\ - 10101 \\ \hline \end{array}$ $\begin{array}{r} 00111 \rightarrow +7 \\ - 01011 \rightarrow -11 \\ \hline +18 > 15 \end{array}$ $\begin{array}{r} 00111 \\ + 01011 \\ \hline 010010 \end{array}$ <p>overflow occurred</p>	<p>(ii)</p> $\begin{array}{r} 10110 \\ - 10011 \\ \hline \end{array}$ $\begin{array}{r} 10110 \rightarrow -10 \\ - 01101 \rightarrow -13 \\ \hline +3 \end{array}$ $\begin{array}{r} 10110 \\ + 01101 \\ \hline 00011 = +3 \checkmark \end{array}$
<p>(iii)</p> $\begin{array}{r} (+6) \quad 00110 \rightarrow 00110 \\ + (-11) \quad + -01011 \rightarrow +10101 \\ \hline -5 \end{array}$ $\begin{array}{r} 00110 \\ + 10101 \\ \hline 11011 = -00101 \\ = -5 \checkmark \end{array}$	<p>(iv)</p> $\begin{array}{r} (-9) \quad -01001 \rightarrow 10111 \\ - (+7) \quad - +00111 \rightarrow -00111 \\ \hline -16 \end{array}$ $\begin{array}{r} 10111 \\ + 11001 \\ \hline 11000 = -16 \checkmark \end{array}$

c. Consider the signed 2's complement arithmetic operation $A - B$ in 6 bits. With $B = 101100$, the largest value allowed for A in order to avoid the occurrence of overflow is $(001011)_2$.

$$B = -010100 = -20$$

$$A - B \leq 31 \rightarrow A \leq B + 31$$


$$A \leq -20 + 31$$

$$A \leq +11$$

Question 4.



(12 Points)

 1. (4 points) Considering the following circuit, provide a minimized SOP expression of $F(A, B, C, D)$.



$$\begin{aligned}
 F &= \overline{AB \oplus (B+C)} \cdot \overline{D} = \overline{AB \oplus (B+C)} + D = [AB \square (B+C)] + D \\
 &= AB(B+C) + \overline{AB} \cdot \overline{(B+C)} + D \\
 &= AB + ABC + (\overline{A} + \overline{B}) \cdot \overline{B} \cdot \overline{C} + D \\
 &= A \overline{B} + \overline{B} \overline{C} + D
 \end{aligned}$$

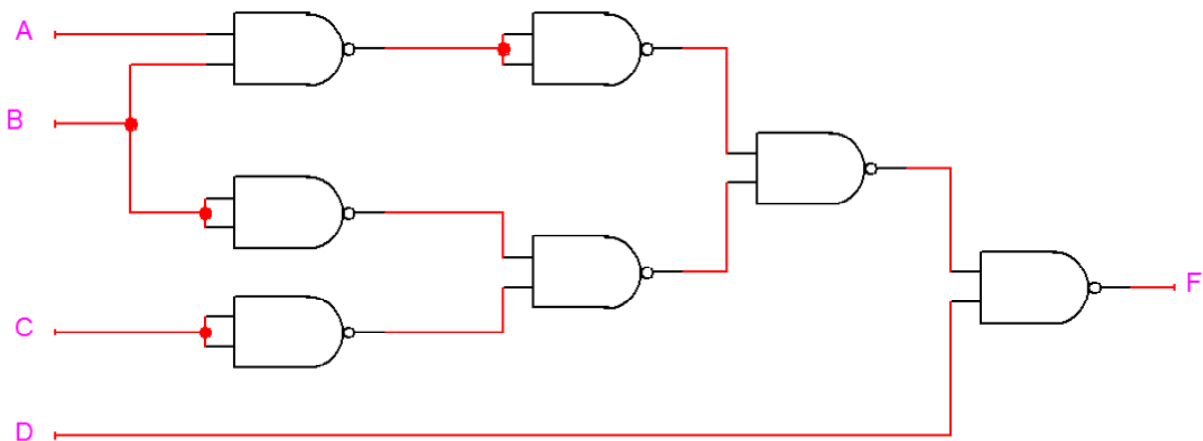 
2. (4 points) Using only NAND gates, redraw the following circuit to show a multi-level NAND circuit. Only the **true** form of each input variable is available.



3. (4 points) Implement $F(A, B, C) = \prod M(0,1,4)$ using a 4-to-1 MUX. Show how you obtained your solution, and properly label all input and output lines.

Connecting A and B to the MUX select lines S_1 and S_0 , respectively, yield the following:

A	B	C	F	MUX Inputs
0	0	0	0	$D_0 = 0$
0	0	1	0	
0	1	0	1	$D_1 = 1$
0	1	1	1	
1	0	0	0	$D_2 = C$
1	0	1	1	
1	1	0	1	$D_3 = 1$
1	1	1	1	

 

Question 5.**(15 Points)**

A Triple adder **circuit** adds three n -bit numbers a , b , and d . The triple adder circuit consists of n -stages of the single bit circuit slice shown in Fig. (i) (called 3-Add). The i^{th} stage receives 5 inputs 3 of which are the i^{th} bits of a , b , and d and the other two are carry-in inputs $C0_i$ and $C1_i$. It has 3 outputs; one sum bit (S_i) and two carry-out bits $C0_{i+1}$ and $C1_{i+1}$.

Fig. (ii) shows the n -bit Triple adder circuit



 
 


Fig. (iii) shows an example for such addition.

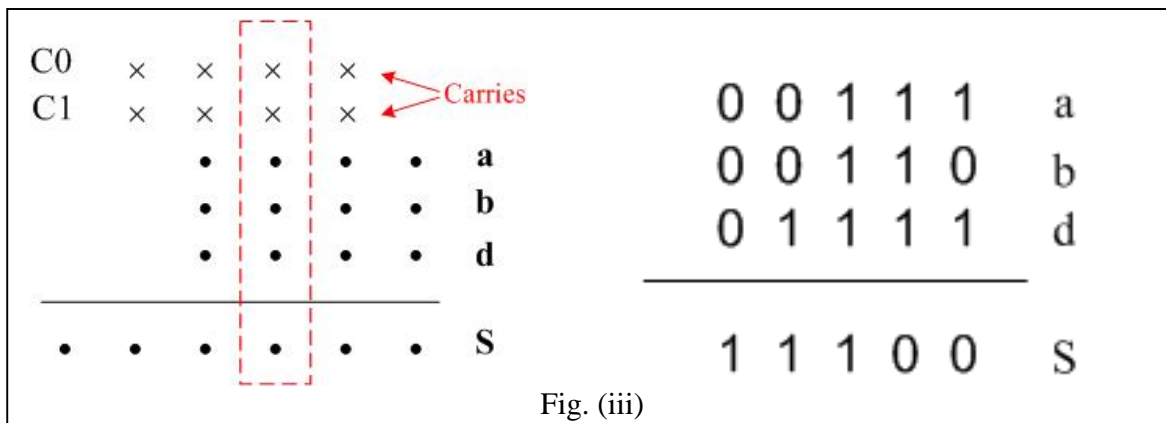

 The circuits used to generate the output carry bits are shown in Fig. (iv). answer the following:



- (I) Using the gate propagation delays of Table (i), what is the carry propagation delay *per single stage* **for both of the output carries (C0 and C1)?** (5 Points)

Gate	Delay
AND , NAND	1 ns
OR , NOR	3 ns
XOR	4 ns

Table (i)

Solution

Propagation Delay ($C0_i \rightarrow C0_{i+1}$) = $2 T_{\text{NAND}} + \text{Max} (T_{\text{AND}} , T_{\text{OR}}) = 2 \times 1 \text{ ns} + 3 \text{ ns} = 5 \text{ ns}$.


Propagation Delay ($C1_i \rightarrow C1_{i+1}$) = $2 T_{\text{NOR}} + \text{Max} (T_{\text{AND}} , T_{\text{OR}}) = 2 \times 3 \text{ ns} + 3 \text{ ns} = 9 \text{ ns}$.

- (II) For the n -bit triple adder circuit of Fig. (ii), assuming a 12ns delay from the i^{th} input carries to the i^{th} sum signal (S_i), calculate the worst case delay to generate the n -bit sum ($S_{n-1} S_{n-2} \dots S_1 S_0$) of the three n -bit operands. (5 Points)

Solution

W. Case Carry propagation delay for the 1st ($n-1$) stages = $(n-1) \times 9\text{ns} = 9(n-1) \text{ ns}$
 Delay to get the $S_{n-1} = 9(n-1) \text{ ns} + 12 \text{ ns} = (9n+3) \text{ ns} = 3(3n+1) \text{ ns}$

 - (III) The i^{th} output sum bit is given by $S_i = a_i \oplus b_i \oplus d_i \oplus C0_i \oplus C1_i$, select one of the following logic implementations of S_i to yield the fastest n -bit triple adder. You must Label the 5-inputs of this circuit (as $a_i, b_i, d_i, C0_i, C1_i$) and **justify** your answer. (5 Points)



Configuration (c) yields the fastest output because of the following:


1. a_i , b_i , and d_i are all ($\forall i$) available at time **0**, thus at the n^{th} stage these signals should have propagated through gates and S_{n-1} would only be waiting for the incoming carry signals ($C0_{n-1}$, $C1_{n-1}$) to be computed.
2. $C0_{n-1}$ arrives **4ns earlier** than $C1_{n-1}$. Thus, inputs of the last XOR gate are available at the same time. Thus Delay from $C1_{n-1}$ to S_{n-1} is only 4 ns.

(16 Points)


Question 6.

- a. Design a circuit that has a three-bit input X and three-bit output Y . Both X and Y represent the integers 0 to 7 (i.e., $X, Y \in \{0, 1, \dots, 7\}$). Using a *single* decoder and a *single* encoder of appropriate sizes, show how can you build a circuit that performs the function $[Y = 3X \bmod 8]$. Make sure you label all signals. The truth table for this circuit is shown in decimal notation. [4 pts]

X	Y
0	0
1	3
2	6
3	1
4	4
5	7
6	2
7	5

 

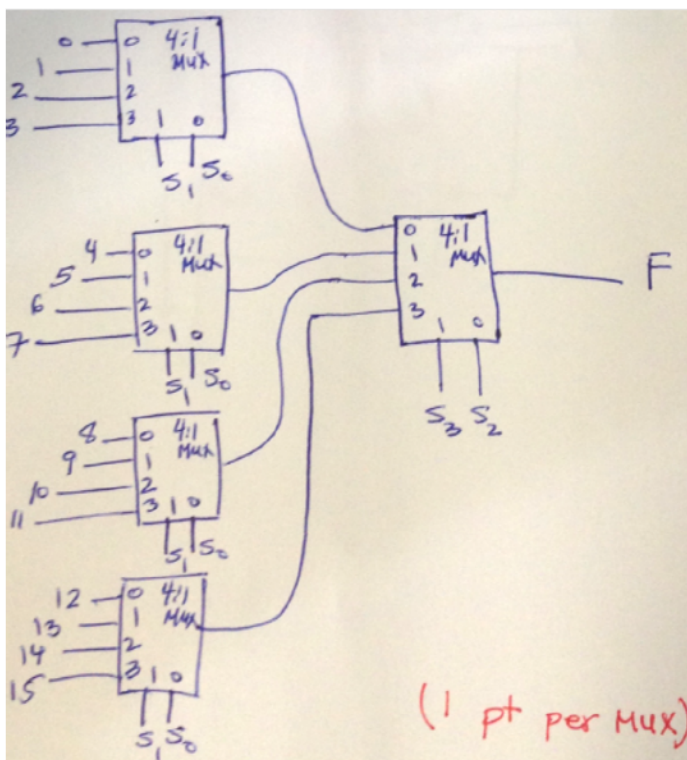- b. Construct a 16-to-1 multiplexer using the minimum number of 4-to-1 multiplexers. [5 pts]



- c. Using only MSI parts, design a circuit that takes two 4-bit binary numbers $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$ together with a 2-bit selection input $S = S_1S_0$. The circuit produces a 5-bit output $O = O_4O_3O_2O_1O_0$ according to the shown table:

S_1S_0	O
00	A+B
01	A-B
10	A+1
11	A-1

Clearly label all inputs and outputs of the MSI parts.

[7 pts]

Note:

- Many solutions are possible. However, you must use one adder. You will lose 2 points if you do not do that.
- Instead of using a constant (like 0001), use $S_0S_0S_0S_1$ for $A \rightarrow A+1$

↑ notice A is common
Also, whenever there is a subtraction operation, $S_0 = 1$

