

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 162 (Winter 2016)**  
**Major Exam 2**  
**Saturday, April 29th, 2017**

**Time: 120 minutes, Total Pages: 9**

Name: \_\_\_\_\_ ID: \_\_\_\_\_ No: \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phone*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

Clearly label all inputs and outputs of any circuit

Question	Points
1	
2	
	8
6	7
7	8
<b>Total</b>	<b>58</b>

## Question 1:

(8 marks)

- a) Show the binary representations of the signed numbers shown in the table below using 8-bits signed-magnitude, 1's complement and 2's complement representations (record your answers in the table below). (4 marks)

<i>Number</i>	<i>Signed-magnitude</i>	<i>1's complement</i>	<i>2's complement</i>
+19	<b>00010011</b>	<b>00010011</b>	<b>00010011</b>
-36	<b>10100100</b>	<b>11011011</b>	<b>11011100</b>

- b) Perform the following operations on 6-bits signed numbers using 2's complement representation. Check for overflow and mark clearly any overflow occurrences. (4 marks)

<p>(1) <math>011001 + 110010</math></p> <pre> 11 011001 (+25) + 110010 (-14) ----- 1 001011 (+11) </pre> <p>Overflow? (NO)</p>	<p>(2) <math>001110 - 100010 = 001110 + 011110</math></p> <pre> 01 001110 (+14) + 011110 (- - 30) ----- 101100 (-20) </pre> <p>Overflow? (YES)</p>
--	--

## Question 2.

For the following Boolean function shown in the K-map below:

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	1	1	1	0
	11	1	1	1	1
	10	1	0	1	1

- a. Identify all the prime implicants and the essential prime implicants of F. (6 marks)

Prime Implicants:  $A' C'$ ,  $B C'$ ,  $B D$ ,  $A C$ ,  $C' D'$ ,  $A B$ ,  $A D'$ ,  $B' D'$

Essential Prime Implicants:  $A' C'$ ,  $B D$ ,  $A C$ ,  $B' D'$

- b. Simplify the Boolean function F into a minimal sum-of-products expression. (2 marks)

$$F = A' C' + B D + A C + B' D' + A B$$

OR  $F = A' C' + B D + A C + B' D' + C' D'$


OR  $F = A' C' + B D + A C + B' D' + B C'$

OR  $F = A' C' + B D + A C + B' D' + A D'$

- c. Implement the function F using only NOR gates with minimum number of NOR gates. (3 marks)

$$F' = A' B' C D + A' B C D' + A B' C' D$$



$$\Rightarrow F = (A + B + C' + D')(A + B' + C' + D)(A' + B + C + D')$$

 

**Question 3:**

**(4 marks)**

  **Convert the circuit below to 2-input NAND gates only. Redraw the circuit to obtain a multi-level NAND circuit implementation. Assume that only the true form of each input variable is available. Use the given circuit structure as is and do not attempt to simplify it.**



## Question 4:

(12 marks)

It is required to design a circuit that receives a 3-bit signed number in 2's complement representation,  $X$ , and computes the equation  $Y = 3*X - 2$ .

- a. Determine the number of bits needed for the output  $Y$ . Justify your answer. (2 marks)

The smallest negative value is -4. Thus,  $3*(-4) - 2 = -14$ . This implies that we need **5 bits** to represent the output correctly.

- b. Derive the truth table for the circuit.

(5 marks)

X2 X1 X0	Y4 Y3 Y2 Y1 Y0	Decimal Value
0 0 0	1 1 1 1 0	-2
0 0 1	0 0 0 0 1	+1
0 1 0	0 0 1 0 0	+4
0 1 1	0 0 1 1 1	+7
1 0 0	1 0 0 1 0	-14
1 0 1	1 0 1 0 1	-11
1 1 0	1 1 0 0 0	-8
1 1 1	1 1 0 1 1	-5

- c. Derive the equation for the least significant output  $Y_0$  into a minimal sum-of-products expression. (3 marks)

$$Y_0 = X_0$$

- d. If the output of the circuit  $Y$  is fed as input to another circuit that will compute the equation  $Z = Y^2$ , what will be the don't care conditions for  $Z$ . (2 marks)

The don't care conditions include all the values that do not occur at the output of  $Y$ , i.e. 0, +2, +3, +5, +6, +8 to +15, -1, -3, -4, -6, -7, -9, -10, -12, -13, -15, -16

Question 5:


(8 marks)

It is required to design a 4-bit arithmetic Unit circuit with two 4-bit unsigned data inputs A and B, and two control inputs M1 and M0 and produce output C according to the following table:

M1	M0	Function Description	F(A, B)
0	0	If A is even, then $C=A+B$ , else $C=A-B$	If A is even then $C \leftarrow A+B$ ; else $C \leftarrow A-B$
0	1	Increment A	$C \leftarrow A + 1$
1	0	Decrement B	$C \leftarrow B - 1$
1	1	Multiply A by 3	$C \leftarrow A \times 3$

Design this circuit with minimum number of standard components (MUX, Decoders, Adders, Comparators, Logic Gates ...etc.).

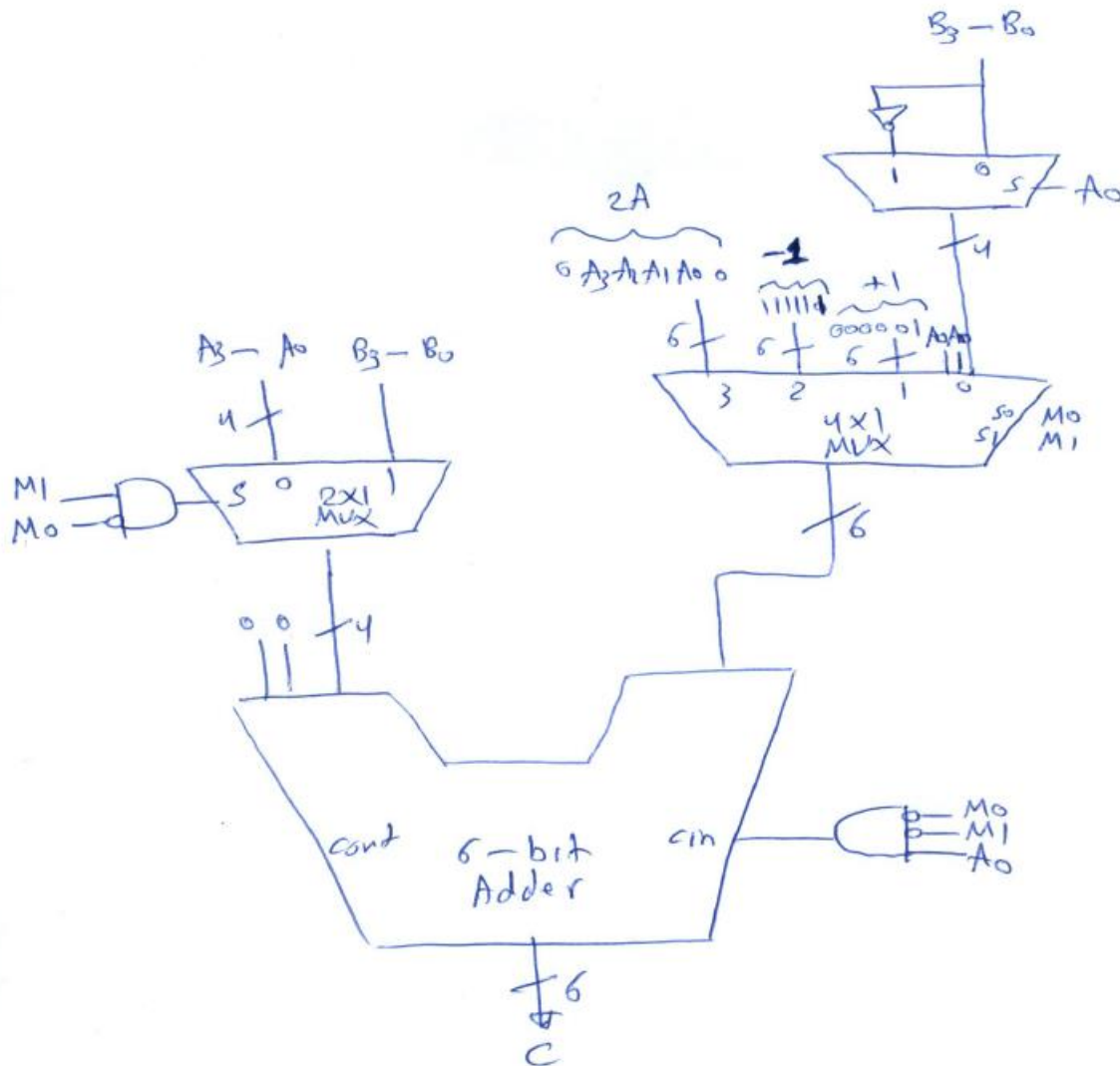
Properly label all components, their inputs and outputs.



(7 marks)

## Question 6:

 - a. Consider the combinational circuit shown with inputs X, Y, Z, and W, and outputs A, A\_b and B :



Assuming that all input/output ports have been declared properly; Write Verilog *assign* statement(s) to describe the circuit above (including worst case delays of the outputs).

Outputs A\_b and B should be expressed as functions of the output A and other inputs.

Assume the following gate delays; inverter's delay= 1 (time unit), AND's delay= 2, and OR's delay=3.

(4 marks)

```
assign #5 A = X & Y | X & Z;
```

```
assign #1 A_b = ~A;
```

```
assign #2 B = A & W;
```

- b. Write a parametrized *behavioral* Verilog description of a circuit that takes an  $n$ -bit signed number input  $A$  represented in 2's complement and produce its absolute value  $Y=|A|$  at the output.

(3 marks)


```
module ABS_Val #(parameter n=8)
    (input [n-1:0] A, output wire [n-2:0] Y);
    assign Y = A[n-1] ? -A : A ;
    // or assign Y = A[n-1] ? (1+~A[n-1:0]) : A ;
endmodule
```

Question 7:

(8 marks)

 - a. Given  $F(A, B, C, D) = \prod M(0, 2, 12, 15)$ , implement F using minimum number of 2-to-4 decoders and a single logic gate with minimum number of inputs. Clearly label all your circuit components, their inputs and their outputs. (5 marks)

Note that we do not need minterms  $m_4$ - $m_{11}$ , so we are not going to generate them!



- b. Given  $(A, B, C) = \sum m(0, 3, 5, 7)$ , implement F using a single *minimum size Multiplexor*. Assume inputs are available in true and complement form. Clearly label all your circuit components, their inputs and their outputs. (3 marks)

A	B	C	F	
0	0	0	1	C'
0	0	1	0	
0	1	0	0	C
0	1	1	1	
1	0	0	0	C
1	0	1	1	
1	1	0	0	C
1	1	1	1	

