

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)

Term 131 (Fall 2013)

Final Exam

Monday December 30, 2013

7:00 p.m. – 9:30 p.m.

Time: 150 minutes, Total Pages: 12

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- Calculators are not allowed (basic, advanced, cell phones, etc.)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated



Question	Maximum Points	Your Points
1	13	
2	12	
3	10	
4	10	
5	10	
6	10	
7	15	
Total	80	

Q1

(13 Points)

 
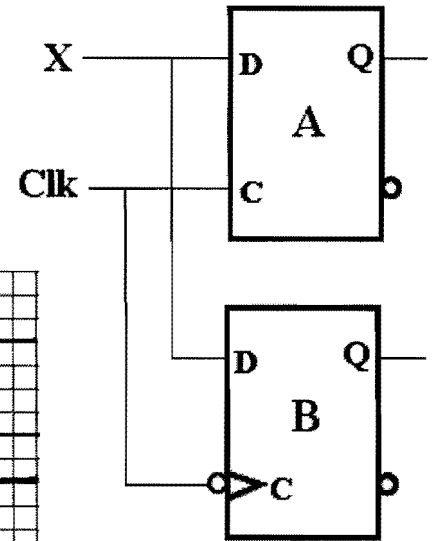
a.
In the circuit shown, A is a D-type latch and B is a D-type flip flop. For the input waveforms for the clock signal (Clk) and the input X, accurately draw the resulting waveforms at outputs Q_A and Q_B .

Assume that both Q_A and Q_B are initially at 0.



b.
The state diagram shown is for a sequential state that has an input X, and output Y, and state Q_1Q_0 . The circuit uses positive edge triggered D-type flip flops and operates from a 2 kHz clock.

  i. Starting with the circuit in state $Q_1Q_0=11$, complete the missing waveforms in the timing diagram below.



ii. Let the circuit be in state 00 with input X held permanently at 0. The circuit will end up being stuck at state 11. This state transition requires a minimum time duration of 1.5 ms.

$$3 \times T = 3 \times 0.5 \text{ ms}$$

Q2

(12 Points)

Consider the sequential circuit opposite and then answer the following questions:

a. Is the circuit Mealy or Moore?


Mealy

b. Provide logical expressions for the flip flop D inputs and the external output

$$D_{Q_0} = Q_1$$

$$D_{Q_1} = Q_0 Q_1 + X$$


$$Y = Q_0 Q_1 + X$$

 

c. Give both the state table and the state diagram. Use the layout given below for the state diagram.

Note: Q0 represents the LSB of the binary value of the state.

Q_1	Q_0	X	Q_1^+	Q_0^+	Y
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

 


Question 3.


(10 Points)

It is required to design a synchronous sequential circuit that receives a serial sequence of **3-bit codes** through input **X** and produces **1** through output **Y** when the received 3-bit code equals either 010 or 110 (i.e., either 0 followed by 1 followed by 0, or 1 followed by 1 followed by 0). Assume the availability of an asynchronous reset input to reset the machine to a reset state. Draw the state diagram of the circuit assuming a Mealy model with minimum number of states. *You are not required to derive the equations and the circuit.* The following is an example of an input and output sequence:

Example:

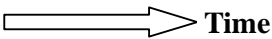


Input	X	0 1 0 0 0 1 0 0 1 1 0 1 1 1 0
Output	Y	0 0 1 0 0 0 0 0 0 0 0 0 0 0 1

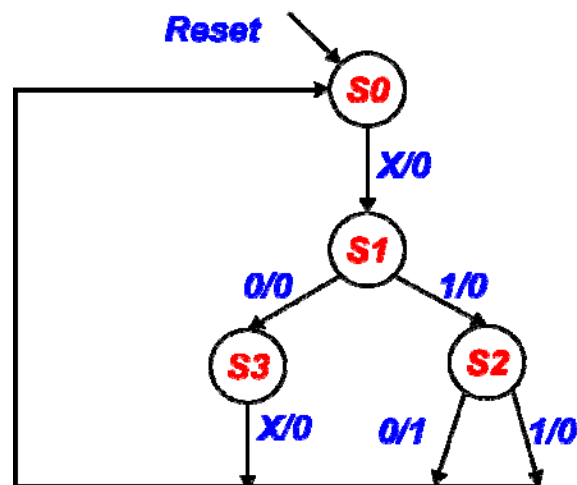

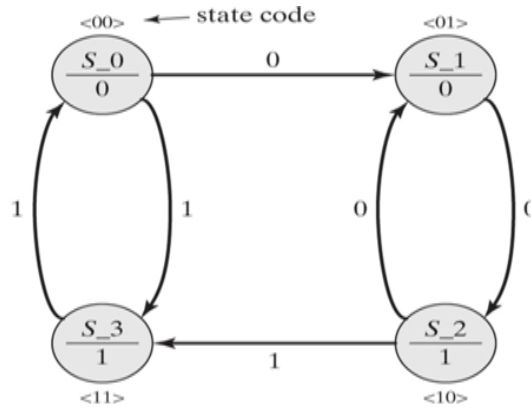Question 4.

(10 Points)

The following state diagram represents a synchronous sequential circuit having a single input **X** and a single output **Y**. Note that the unspecified (missing) transitions in the state diagram do not occur (i.e. don't care). The states are assigned the following state codes **S_0=00**, **S_1=01**, **S_2=10** and **S_3=11**. Assume the existence of an **asynchronous reset** input to reset the machine to state **S_0**.



- (i) Draw the state transition table for the sequential circuit.
- (ii) Using D-FFs and **minimal** combinational logic determine the equations for the D-FFs and output **Y** for this sequential circuit.
- (iii) Draw the resulting circuit.

(i) State Transition Table:

Current State		Input	Next State		Output
F1	F0		F1+	F0+	
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	1	0	0
0	1	1	X	X	0
1	0	0	0	1	1
1	0	1	1	1	1
1	1	0	X	X	1
1	1	1	0	0	1

(ii) FF and Output Equations:

	Q0X			
Q1 \	00	01	11	10
0	0	1	X	1
1	0	1	0	X

$$Q1+ = Q0' X + Q0 X' = Q0 \oplus X$$


	Q0X			
Q1	00	01	11	10
0	1	1	X	0
1	1	1	0	X

$Q0+ = Q0'$

	Q0	
Q1	0	1
0	0	0
1	1	1

$Y = Q1$

(iii) Circuit:

 


Question 5.**(10 Points)**

Using only D flip-flop(s), MUX(s), and **XOR gate(s)**, draw the logic diagram for a 4-bit register with 2 mode selection inputs M_1M_0 and 4 load inputs $I_3I_2I_1I_0$. Note that D flip-flop outputs include both the state and its complement (i.e., Q and \bar{Q}) available for use. The register should operate according to the following table:

M_1M_0	Register operation
00	No change.
01	Parallel Load.
1x	Shift <u>right</u> while feeding in an ODD parity bit for the 3 bits that remain in the register <u>after</u> shifting. (Examples: 1. register content <u>before</u> shifting = 0110, register content <u>after</u> shifting = 1011 2. register content <u>before</u> shifting = 1001, register content <u>after</u> shifting = 0100)

 You must clearly label the D flip-flop(s) and MUX(s) inputs and outputs.



Note: It is possible to have any of the following connected to inputs 2 and 3 of the MUX that is connected to D_3 :

$$\bar{Q}_3 \oplus \bar{Q}_2 \oplus \bar{Q}_1$$

$$\bar{Q}_3 \oplus Q_2 \oplus Q_1$$

$$Q_3 \oplus \bar{Q}_2 \oplus Q_1$$

$$Q_3 \oplus Q_2 \oplus \bar{Q}_1$$

Question 6.**(10 Points)**

Consider the following state transition table for a synchronous sequential circuit that detects five consecutive 1's. The circuit has a single input X , a single output Z , and three state variables Y_0 , Y_1 , and Y_2 . The states are encoded using binary codes **001**, **010**, **011**, **100**, and **101**.

PS	$(Y_2 \ Y_1 \ Y_0)^{t+1}$		Z	
$(Y_2 \ Y_1 \ Y_0)^t$	X = 0	X = 1	X = 0	X = 1
0 0 1	0 0 1	0 1 0	0	0
0 1 0	0 0 1	0 1 1	0	0
0 1 1	0 0 1	1 0 0	0	0
1 0 0	0 0 1	1 0 1	0	0
1 0 1	0 0 1	1 0 1	0	1

You are required to implement the above circuit using a **ROM** device and a **register**. The circuit should be designed such that **any unused state should go to the initial state 001**.

- a. What is the minimum size of the register (i.e., number of D flip-flops)? [1 pt]


Three state variables \rightarrow 3 FFs

- b. What is the minimum size of the ROM (number of memory locations \times number of memory bits per location)? [2 pt]


of Locations = $2^4 = 16$ word

of Bits = 4

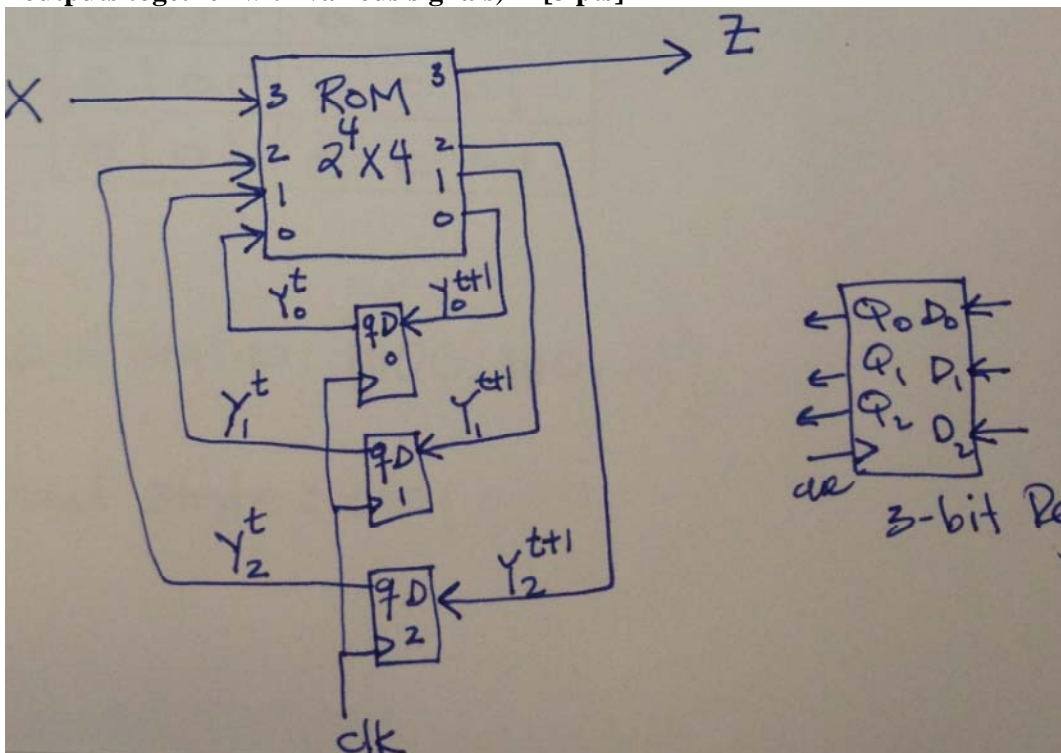- c. Draw the block diagram for such an implementation. (Label all components inputs and outputs together with various signals) [3 pts]



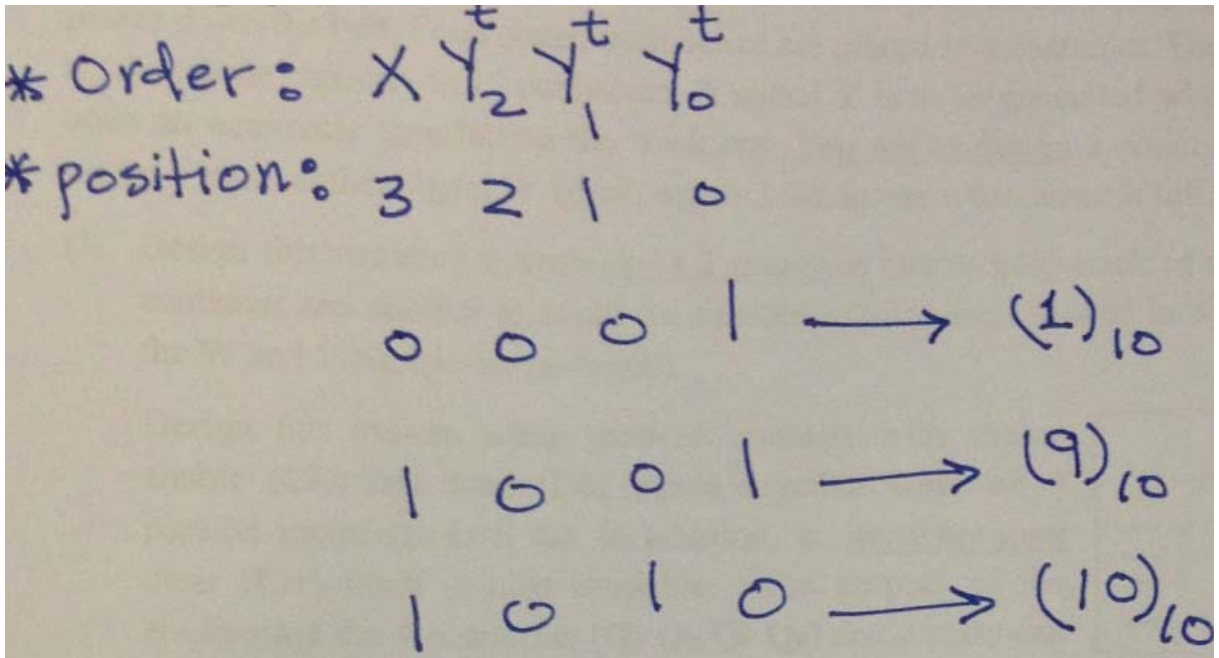- d. Starting in the initial state **001**, what is the sequence of ROM locations addresses that will be accessed as a result of applying an input sequence **X = 011** where **0** is applied first. [2 pts]



- e. Starting from address **0**, complete the following table to show the data stored in the first six memory locations in the ROM device [2 pts]

Binary Address	Binary Stored Data
$X Y_2^t Y_1^t Y_0^t$	$Z Y_2^{t+1} Y_1^{t+1} Y_0^{t+1}$
0 0 0 0	0 0 0 1
0 0 0 1	0 0 0 1
0 0 1 0	0 0 0 1
0 0 1 1	0 0 0 1
0 1 0 0	0 0 0 1
0 1 0 1	0 0 0 1


Note: Unused states are states {000, 110, 111}

Question 7.**(15 Points)**


In an assembly line a conveyer belt has a sensor that generates a signal **X** whenever a cartoon box passes down the belt. Each dozen such boxes are placed in a container. The containers are loaded in trucks whose capacity is 15 containers. A signal **Y** is to be generated whenever the truck is full to open an automatic gate letting the truck out. You are to design a counting system that generates signal **Y** and another signal **W** which equals **1** whenever a container is full.

 - (I) Design this counting system using 2 counters; one to keep track of the number of boxes in a container and another to count the number of containers loaded in a truck. Clearly show how the **W** and **Y** signals are generated.

Design this system using **mod-16** counters with count-able (**CE**) and load (**Ld**) inputs together with the 4 parallel inputs (**I₃ I₂ I₁ I₀**). In addition, an asynchronous clear (**Clr**) input is also available. The outputs of the counter are the 4 count bits (**Q₃ Q₂ Q₁ Q₀**) and a carry-out signal **C_{out}** which equals **1** when $Q_3Q_2Q_1Q_0 = 1111$.



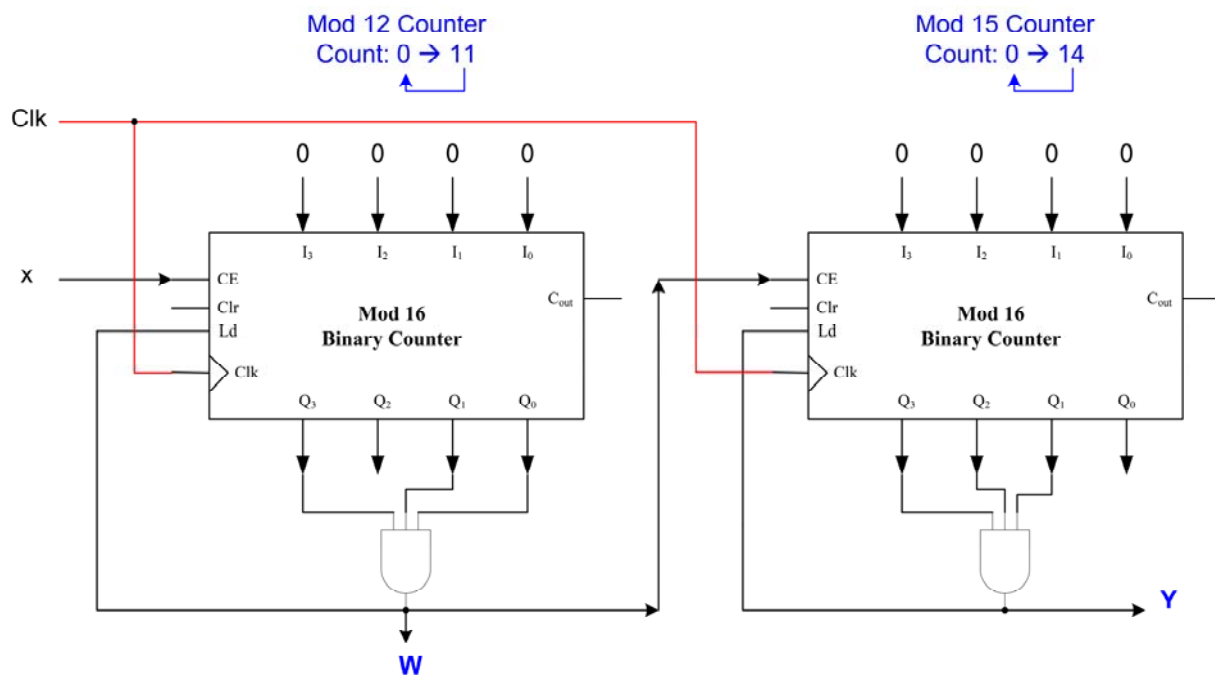Draw the complete block diagram of the counting system showing all logic components needed / used by the system **(6 Pts)**




- (II) Modify the counting system you designed in part (I) to make it self-resetting, i.e. whenever the system falls in any unused state, the count is automatically reset to zero. (3 Pts)

Unused states for the mod 12 counter correspond to counts: $Q_3Q_2Q_1Q_0 = 1100 \rightarrow 1111$ which correspond to a Boolean expression of unused-1 = Q_3Q_2


Unused states for the mod 15 counter correspond to the single count: $Q_3Q_2Q_1Q_0 = 1111$ which correspond to a Boolean expression of unused-1 = $Q_3Q_2Q_1Q_0$

Once the unused state is detected, the generated signal can be used to asynchronously clear the counter.

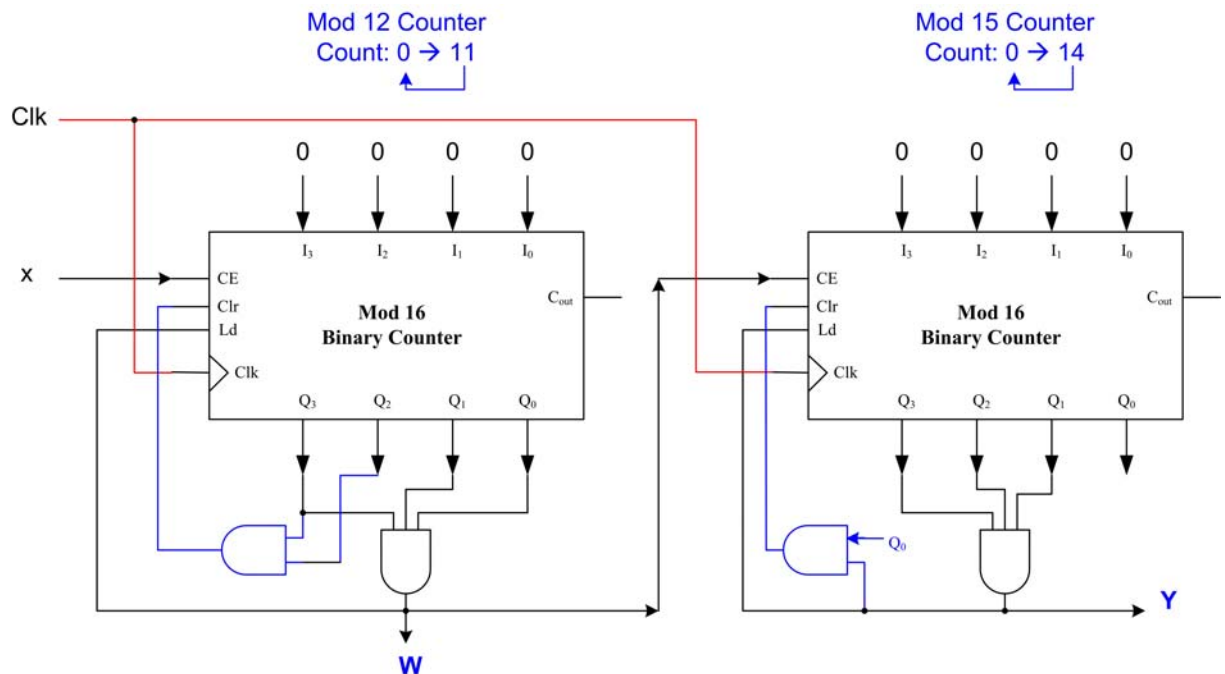The self-resetting logic is shown in blue.



 (III) The carton boxes are 75 cm long, and are placed 100 cm apart on the conveyer belt. Signal **X** maintains a value of **1** until the full length of the box passes beyond the sensor. Given that the belt moves at a speed of 5 meters/sec;




a. Plot the *waveform* of signal **X** (value of X versus time).

(2 Pts)

$$\text{Signal X} = 1 \text{ for a period of } = \frac{0.75 \text{ meters}}{5 \text{ meters/sec}} = 0.15 \text{ seconds}$$
 
$$\text{Signal X} = 0 \text{ for a period of } = \frac{1 \text{ meters}}{5 \text{ meters/sec}} = 0.2 \text{ seconds}$$



b. Neglecting propagation, setup and hold delays, determine the maximum possible clock frequency. What happens if a higher frequency is used? (2 Pts)

No more than one clock pulse may be received during the period when X=1, otherwise one box may count more than once. Thus, the minimum clock period = Period of X=1

$$T_{\text{CLK}}(\text{min}) = 0.15 \text{ sec} \rightarrow \text{Maximum frequency } f_{\text{max}} = 1/0.15 = 6.66 \text{ Hz}$$

c. Neglecting propagation, setup and hold delays, determine the minimum possible clock frequency. What happens if a lower frequency is used? (2 Pts)

At least one clock pulse should be received for each X pulse, otherwise a box may pass without being counted at all.

$$T_{\text{CLK}}(\text{max}) = 0.35 \text{ sec} \rightarrow \text{minimum frequency } f_{\text{min}} = 1/0.35 = 2.86 \text{ Hz}$$

Thus the clock frequency f should satisfy: $2.86 \text{ Hz} \leq f \leq 6.66 \text{ Hz}$