
 


COE 202, Term 162
Digital Logic Design
HW# 5

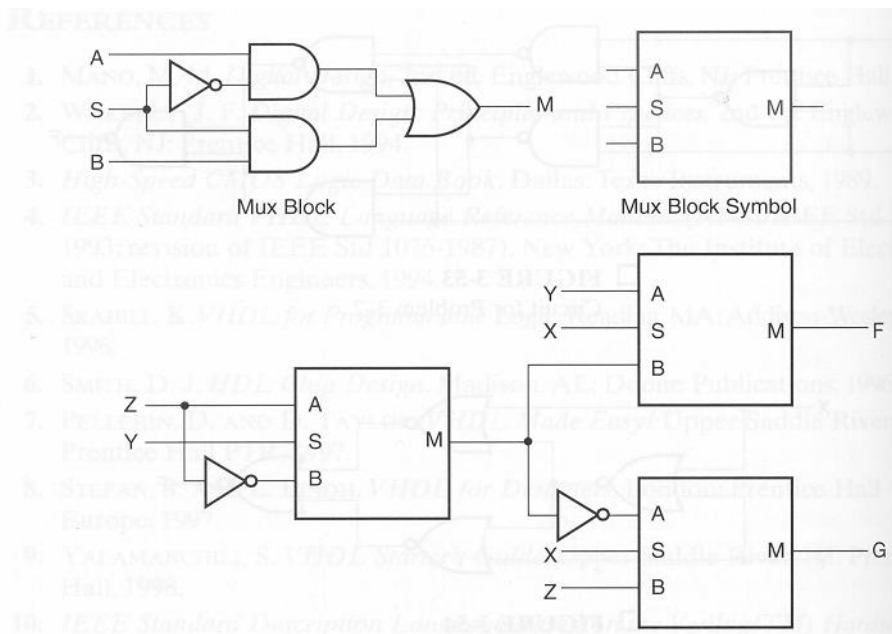
Q.1. Obtain the truth table for the circuit shown below. Draw an equivalent circuit for F with fewer NAND gates.



Q.2. Find simplified Boolean equations for the outputs F and G of the hierarchical circuit given below.



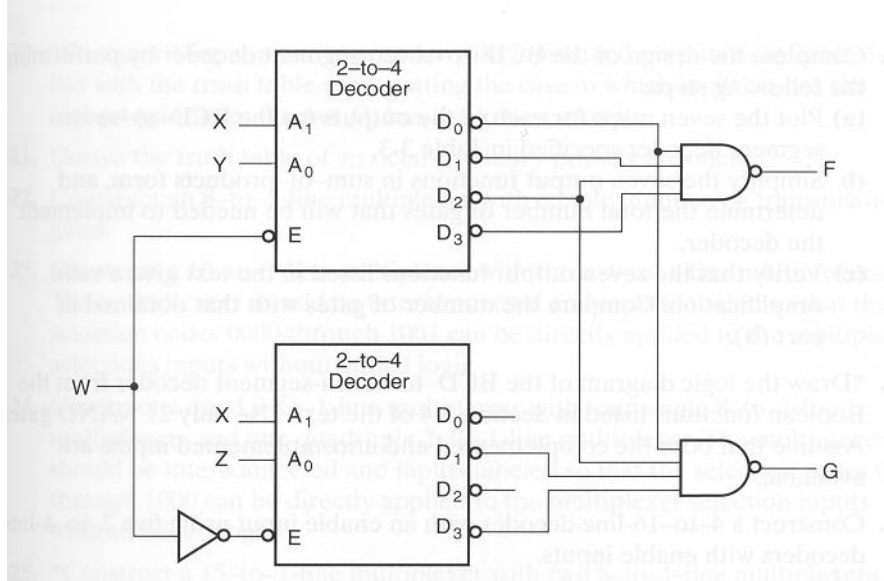Q.3. Find the truth table for the outputs F and G of the hierarchical circuit shown below.



Q.4. Construct a 5-to-32 line decoder with four 3-to-8 line decoders with enable input and one 2-to-4 line decoder.

Q.5. A Combinational circuit is defined by the following three Boolean functions:

$$F_1(X, Y, Z) = X'Y' + XYZ'$$

$$F_2(X, Y, Z) = X' + Z$$

$$F_3(X, Y, Z) = XY + X'Y'$$

(i) Design the circuit with a 3x8 decoder, four 2-input OR gates, and an inverter.

(ii) Design the circuit with two 4x1 MUXs, one 2-input OR gate, and an inverter.

Q.6. Design a 4-input priority encoder with four inputs and three outputs including the valid bit but with the truth table representing the case in which input D₀ has the highest priority and input D₃ has the lowest priority.

Q.7. Construct a quad 9-to-1 line multiplexer with four single 8-to-1 line multiplexers and one quadruple 2-to-1 line multiplexer. The multiplexers should be interconnected and inputs labeled so that the selection codes 0000 through 1000 can be directly applied to the multiplexer selection inputs without added logic.

- Q.8.** Implement the following Boolean function $F(A, B, C, D) = \sum m(4, 6, 7, 8, 12, 15)$ with:
- (i) An 8x1 MUX. Assume that the inputs A, B, and C are used for the select lines.
 - (ii) A 4x1 MUX and external gates. Assume that the inputs A and B are used for the select lines.
- Q.9.** Design a Combinational circuit that accepts a 3-bit number and generates as output a binary number equal to the square of the input number.
- Q.10.** It is required to design a Combinational circuit that compares two n-bit numbers to see if they are equal or not. Design a circuit that has three inputs and one output, that can be used for each of the n bits, such that the circuit is connected in cascade by carry-like signals. One of the inputs to each cell is a carry input, and the single output is a carry output.
- Q.11.** Design three versions of the combinational circuit whose input is a 4-bit number and whose output is the 2's complement of the input number such that:
- (i) The circuit is a simplified two-level circuit, plus inverters as needed for the input variables.
 - (ii) The circuit is made up of four identical two-input, two output cells, one for each bit. The cells are connected in cascade, with lines similar to a carry between them. The value applied to the rightmost carry bit is 0.
 - (iii) The circuit is redesigned with carry lookahead-like logic in order to speed up the circuit in part (ii) for use in larger circuits with 4n input bits.