 



**COE 202, Term 102**  
**Fundamentals of Computer Engineering**  
**HW# 5**

- Q.1.** Design a combinational circuit that detects an error in the representation of a decimal digit in BCD. In other words, obtain a logic diagram whose output is equal to 1 when the inputs contain any one of the six unused bit combinations in the BCD code.
- Q.2.** Implement a full-adder using a dual 4x1 multiplexer.
- Q.3.** It is required to design a 4-bit ripple-borrow subtractor to find the subtraction  $X-Y$  for the two unsigned numbers,  $X=X_3-X_0$ , and  $Y=Y_3-Y_0$ . Design a 1-bit full subtractor and show how it can be used to construct the 4-bit subtractor.
- Q.4.** Design two simplified combinational circuits that generate the 9's complement of (a) a BCD digit and (b) an excess-3 digit. Then compare the gate and literal count of the two circuits. Assume in both cases that input combinations not corresponding to decimal digits give don't care outputs.
- Q.5.** Construct a BDC adder-subtractor using a BCD adder and the 9's complement designed in Q3, as well as other logic or functional blocks as necessary. Use block diagrams for the components, showing only inputs and outputs where possible.
- Q.6.** The D-latch shown below can be constructed with only four NAND gates. This can be done by removing the inverter and connecting the output of the upper NAND gate (connected to the D input) to the input of the lower NAND gate (Connected to D'). Use manual or computer-based logic simulation to verify that the new circuit is functionally the same as the original one.



**Q.7.** Obtain the logic diagram of the D-latch give in Q6, using NOR gates only.

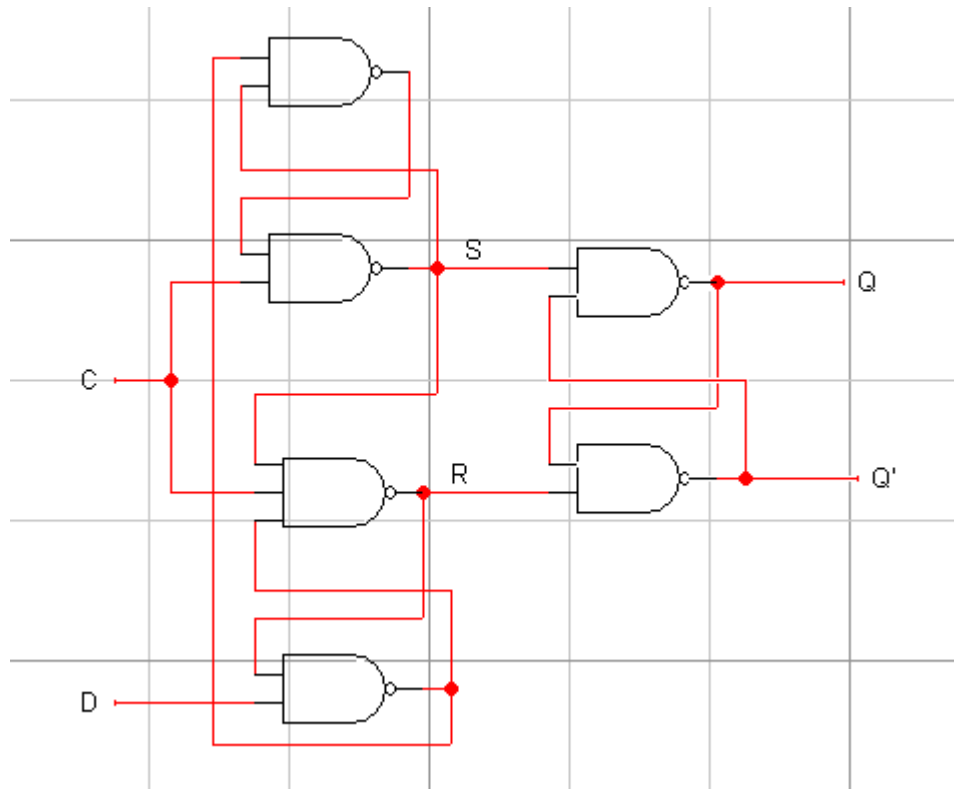**Q.8.** A popular alternative design for positive-edge-triggered D flip-flop is shown below. Simulate the circuit to determine that its functional behavior is identical to that of a D flip-flop.



**Q.9.** Show the design of the following flip-flops using SR latches and external gates:

- (i) A negative-edge triggered D-FF.
- (ii) A negative edge-triggered JK-FF.
- (iii) A positive-edge triggered T-FF.

**Q.10.** A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:


$$D_A = X \oplus Y + X A \qquad D_B = X \oplus B + X A \qquad Z = B$$

(i) Draw the logic diagram of the circuit.


(ii) Derive the state table.

(iii) Derive the state diagram.

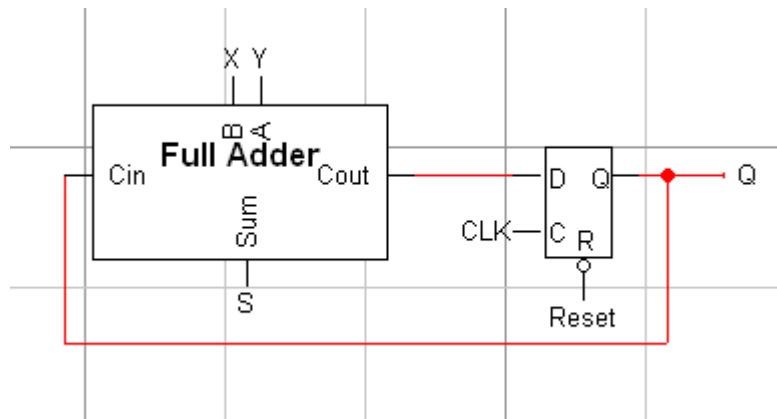**Q.11.** A sequential circuit has one flip-flop Q, two inputs X and Y, and one output S. The circuit consists of a full adder circuit connected to a D flip-flop, as shown below. Derive the state table and state diagram of the sequential circuit.



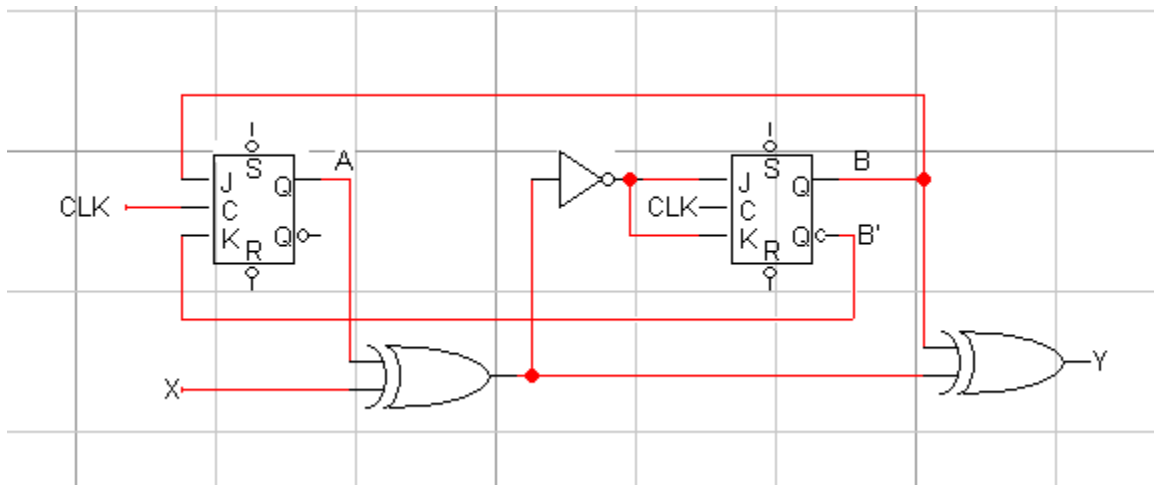**Q.12.** A sequential circuit has two JK flip-flops, one input X, and one output Y. The logic diagram of the circuit is shown below. Derive the state table and state diagram of the circuit.




HW#5

Q1 The output is 1 if the BCD code is in the range 1010 - 1111.


	$A_3A_2$	00	01	11	10
$A_1A_0$	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	1

$$E = A_3 A_2 + A_3 A_1$$


$$= A_3 (A_2 + A_1)$$

 

Q2 Full adder

 

Q3

 

$b_i$	$x_i$	$y_i$	$b_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

$b_i$	$x_i y_i$	00	01	11	10
0		0	1	0	0
1		1	0	1	0

$$b_{i+1} = \bar{x}_i y_i + b_i \bar{x}_i + b_i y_i$$



$$= \bar{x}_i y_i + b_i (y_i + \bar{x}_i)$$

$$= \bar{x}_i y_i + b_i (y_i \oplus \bar{x}_i)$$

$$= \bar{x}_i y_i + b_i (y_i \oplus x_i)$$

$b_i$	$x_i y_i$	00	01	11	10
0		0	1	0	1
1		1	0	1	0

$$S_i = x_i \oplus y_i \oplus b_i$$

  

Q4 9's complement

(a) BCD digit

Digit	$x_3$	$x_2$	$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0
2	0	0	1	0	0	1	1	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	0	0
6	0	1	1	0	0	0	1	1
7	0	1	1	1	0	0	1	0
8	1	0	0	0	0	0	0	1
9	1	0	0	0	0	0	0	0

$$y_0 = \bar{x}_0, \quad y_1 = x_1$$


$x_3 x_2$	$x_1 x_0$	00	01	11	10
00	0	0	1	1	1
01	1	1	0	0	0
11	X	X	X	X	X
10	0	0	X	X	

$x_3 x_2$	$x_1 x_0$	00	01	11	10
00	1	1	0	0	0
01	0	0	0	0	0
11	X	X	X	X	X
10	0	0	X	X	

$$y_2 = x_2 \bar{x}_1 + \bar{x}_2 x_1$$

$$= x_2 \oplus x_1$$


$$y_3 = \bar{x}_3 \bar{x}_2 \bar{x}_1$$

 

(b) Excess-3 digit


Digit	$x_3$	$x_2$	$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	1	1	1	1	0	0
1	0	1	0	0	1	0	1	1
2	0	1	0	1	1	0	1	0
3	0	1	1	0	1	0	0	1
4	0	1	1	1	1	0	0	0
5	1	0	0	0	0	1	1	1
6	1	0	0	1	0	1	1	0
7	1	0	1	0	0	1	0	1
8	1	0	1	1	0	1	0	0
9	1	1	0	0	0	0	1	1
 
$$y_0 = \bar{x}_0, \quad y_1 = \bar{x}_1, \quad y_2 = \bar{x}_2, \quad y_3 = \bar{x}_3$$




(c) we can see that for the excess-3 code, the 9's complement circuit has 4 literals and 4 inverter gates. However, for the BCD code, the 9's complement circuit has 9 literals and one inverter, one NOR, and one XOR gate. This is the advantage of using the excess-3 code as the 9's complement is obtained by finding the 1's complement of the code.

Q5 BCD Adder - Subtractor

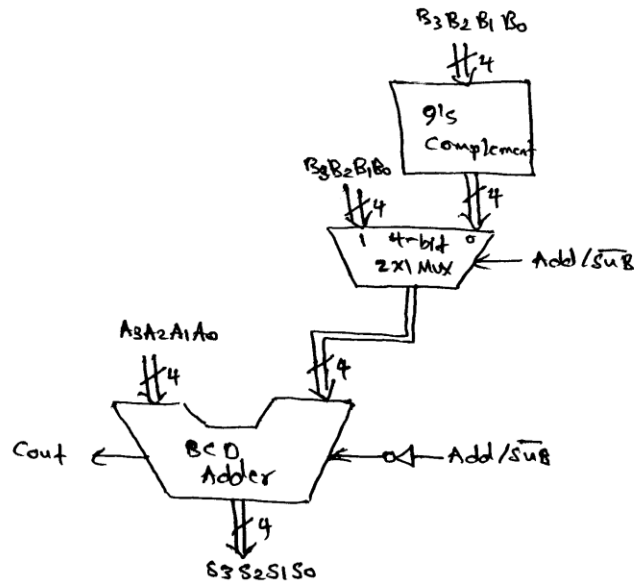


Q6 Modified D-latch


 





Q7 D latch with NOR gates only

 

  
Q8 Alternative positive-edge-triggered D flip-flop




Q9  
 (i) Negative-edge triggered D-FF

 

(ii) Negative-edge triggered JK-FF

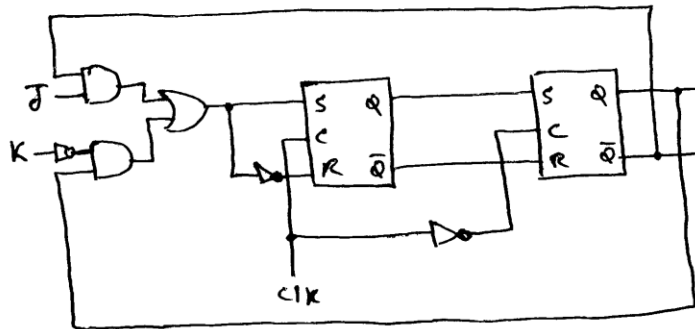


(iii) Positive-edge triggered T-FF

 

Q10

$$D_A = \bar{x}y + xA, \quad D_B = \bar{x}B + xA, \quad z = B$$


(a)

 

(b) State Table:

Current State AB	Next State				output Z
	xy=00 AB	xy=01 AB	xy=10 AB	xy=11 AB	
00	00	10	00	00	0
01	01	11	00	00	1
10	00	10	11	11	0
11	01	11	11	11	1

(c) State Diagram:

 

\* Note that this circuit has a Moore model.

\* Note that this circuit has several synchronizing sequence. For example, {00,11} synchronizes it to state 00.

Q11


$$D_2 = xy + xz + yz$$

$$S = x \oplus y \oplus z$$

State Table:

Current state z	Inputs x y		Next state z	output S
	x	y		
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

State Diagram:

 


This circuit is a mealy model.

Note that this circuit has synchronizing sequence. For example, {00} synchronizes the circuit to state 0. Also, {11} synchronizes it to the 1 state.

Q12  $\delta A = B$ ,  $K_A = \bar{B}$ ,  $\delta B = (A \oplus X)'$ ,  $K_B = (A \oplus X)$ ,  $Y = A \oplus B \oplus X$

Current State		Input X	Next State		FFs Inputs				output
A	B		A	B	$\delta A$	$K_A$	$\delta B$	$K_B$	Y
0	0	0	0	1	0	1	1	1	0
0	0	1	0	0	0	1	0	0	1
0	1	0	1	0	1	0	1	1	1
0	1	1	1	1	1	0	0	0	0
1	0	0	0	0	0	1	0	0	1
1	0	1	0	1	0	1	1	1	0
1	1	0	1	1	1	0	0	0	0
1	1	1	1	0	1	0	1	1	1

State Diagram:

 

This circuit is a mealy model.  
Notice that this circuit has no synchronizing sequence.