

Name:

Id#

COE 202, Term 141  
Digital Logic Design

Quiz# 2

Date: Thursday, Oct. 16


**Q1** Use Boolean algebra to solve the following questions. Show clearly all your steps.

a. Reduce  $F = \overline{W}X\overline{Z} + XW + \overline{W}X\overline{Y}Z + X\overline{W}YZ$  to 1 literal

b. Reduce  $F = (x + y)(x + \overline{y}) + xyz + \overline{x}y + xy\overline{z}$  to the sum of 2 literal

c. Given  $F = Y + \overline{X}Z + X\overline{Y}$ , Express  $\overline{F}$  as a single minterm

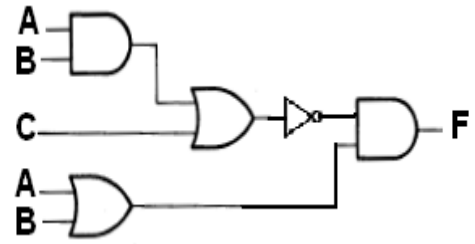d. Express F in the logic diagram shown as a function of the input variables.  
Do not do any logic manipulations.



**Q2.** Given the Boolean function  $F(X, Y, Z) = (X + Y)(X + Z)(\bar{X} + \bar{Z})$ :

- a. Express F as a **sum-of-minterms**,  $F = \sum m$ .
- b. Find the **algebraic product-of-Maxterms** expression for F.

**Q3.** Given  $F(A, B, C) = \sum m(0, 3, 5, 7)$  and  $G(A, B, C) = \prod M(1, 2, 4, 7)$ , express the function  $F + \bar{G}$  as a sum-of-minterms.